

# **IC Design of Power Management Circuits (IV)**

**Wing-Hung Ki**

**Integrated Power Electronics Laboratory**

**ECE Dept., HKUST**

**Clear Water Bay, Hong Kong**

**[www.ee.ust.hk/~eeki](http://www.ee.ust.hk/~eeki)**

**International Symposium on Integrated Circuits  
Singapore, Dec. 14, 2009**

# Part IV

## Bandgap References

# Content (1)

## Bandgap Reference Fundamentals:

PTAT Loop,  $V_{PTAT}$ ,  $V_{BE}$ ,  $V_{BG}$ ,  $V_{REF}$

Tempco, Line and Load Regulation, PSR

Positive and Negative Feedback Loops, Stability

Symmetrical Matching in Bipolar and CMOS Transistors

## Simplest Bandgap References:

Basic BGR: Basic Bandgap Reference

in [Meijer 76]

Basic SM BGR: Basic Symmetrically Matched BGR

[industry]

PCS BGR: Peak Current Source BGR

[Cheng 05]

## Classic Bandgap References:

Widlar BGR

[Widlar 71]

Brokaw BGR

[Brokaw 74]

in [Meijer 76]: referenced, but not proposed, in [Meijer 76].

[industry]: circuit not published but used in the industry.

## Content (2)

### CMOS Bandgap References with Op Amp:

Vertical PNPs for CMOS BGRs

OP BGR: Op Amp Based BGR

CM BGR: Op Amp Based BGR with Current Mirror

FR BGR: BGR with Folded Resistors

SFR BGR: BGR with Symmetrical Folded Resistors

FRD BGR: BGR with Folded Resistor Dividers

[Song 83]

[Kuijk 73]

[Gregorian 81]

[Neuteboom97]

[Banba 99]

[Leung 02]

### CMOS Bandgap References without Op Amp:

4T BGR: BGR with 4T Current-Voltage Mirror (CVM)

4T SM BGR: BGR with 4T SM CVM

8T SM BGR: BGR with 8T SM CVM

in [Gray 01]

[industry]

[Lam 09]

### Design Issues:

Start Up

Trimming

Organization of References in IC System

# I-V Characteristic of NPN

The I-V characteristic of a short-base npn transistor is [Sze 81]

$$I_c = I_s (e^{V_{BE}/nV_T} - 1)$$
$$= qn_i^2 A \frac{D_n}{N_A W_B} (e^{V_{BE}/nV_T} - 1)$$

where  $I_c$ : collector current

$I_s$ : reverse saturation current

$V_{BE}$ : base-emitter voltage

$V_T$ : thermal voltage =  $kT/q$

$k$ : Boltzmann's constant ( $=1.38 \times 10^{-23}$  J/K)

$T$ : absolute temperature (Kelvin, K)

$q$ : electronic charge ( $=1.6 \times 10^{-19}$  C)

$n$ : non-ideality factor


$n_i$ : intrinsic carrier concentration

$A$ : area of base

$D_n$ : diffusion constant of electron (minority carrier) in the base

$N_A$ : donor (majority carrier) doping concentration in the base

 $W_B$ : effective base width (to replace diffusion length)



# Temperature Dependence of I-V Curve

We investigate the temperature dependence of the transistor. With Einstein's relation:

$$\frac{D_p}{\mu_p} = \frac{D_n}{\mu_n} = \frac{kT}{q}$$

we have

$$\begin{aligned} I_s &= C_1 T n_i^2 \bar{\mu}_n \\ n_i^2 &= C_2 T^3 e^{-V_{Go}/nV_T} \\ \mu_n &= C_3 T^{-\eta} \end{aligned}$$

and gives

$$I_s = CT^\gamma e^{-V_{Go}/nV_T} \quad (C = C_1 C_2 C_3, \gamma = 4 - \eta)$$

where  $\mu_n$ : (average, effective) mobility of electron  
 $V_{Go}$ : silicon bandgap voltage at 0K (= -273°C) [Gray 01] gives  
 $V_{Go} = 1.205V$  with no explanation; while [Sze 81] gives  
 $V_{Go} = 1.17V$ , and  $V_G(300K) = 1.11V$  using experimental data.

# Temperature Dependence of $V_{BE}$

The temperature dependence of the collector current is quite complicated but could be expressed as [Gray 01]

$$I_c = DT^\chi$$

and gives

$$\begin{aligned} V_{BE} &= nV_T \ln\left(\frac{I_c}{I_s}\right) \\ &= nV_T \ln\left(\frac{DT^\chi}{CT^\gamma e^{-V_{Go}/nV_T}}\right) \\ &= V_{Go} - nV_T \ln(ET^{\gamma-\chi}) \quad (E = C/D) \\ &= V_{Go} - nV_T [(\gamma - \chi) \ln(T) + \ln(E)] \end{aligned}$$

Note: (1)  $V_{BE}$  is lower than  $V_{Go}$

(2) Temperature coefficient (TC) of  $V_{BE}$  ( $\partial V_{BE}/\partial T$ ) is negative

## Realizing $V_{\text{REF}}$

The thermal voltage at  $T = 300\text{K}$  ( $27^\circ\text{C}$ ) is

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 25.88\text{mV}$$

The TC of  $V_T$  at 300K is positive:

$$\begin{aligned} \frac{\partial V_T}{\partial T} &= \frac{k}{q} = \frac{V_T}{T} \\ &= +86.25 \times 10^{-6} \text{ V} / ^\circ\text{C} \end{aligned}$$

From previous page, we learn that TC of  $V_{\text{BE}}$  is negative. If we design a circuit with a voltage proportional to  $V_T$ , then we have

$$\begin{aligned} V_{\text{REF}} &= V_{\text{BE}} + M V_T \\ &= V_{\text{Go}} - n V_T (\gamma - \chi) \ln(T) + V_T [M - n \ln(E)] \end{aligned}$$

We need to determine the condition for  $V_{\text{REF}}$  to have zero TC.



## Condition for Zero-TC of $V_{\text{REF}}$

The condition for zero TC of  $V_{\text{REF}}$  at a predefined temperature  $T_o$  is

$$\left. \frac{dV_{\text{REF}}}{dT} \right|_{T_o} = 0$$

$$\Rightarrow -nV_{T_o}(\gamma - \chi) \frac{1}{T_o} - \frac{nV_{T_o}(\gamma - \chi)}{T_o} \ln(T_o) + \frac{V_{T_o}}{T_o} [M - n \ln(E)] = 0$$

$$\Rightarrow M - n \ln(E) = n(\gamma - \chi) [1 + \ln(T_o)]$$

$$\therefore V_{\text{REF}} = V_{G0} + nV_T(\gamma - \chi) \left( 1 - \ln\left(\frac{T}{T_o}\right) \right)$$

As the reference voltage is close to  $V_{G0}$ , so it is labeled the **bandgap reference voltage**:

$$\begin{aligned} V_{\text{BG}} &= V_{\text{BE}} + MV_T \\ &= V_{G0} + nV_T(\gamma - \chi) \left( 1 - \ln\left(\frac{T}{T_o}\right) \right) \end{aligned}$$

# Temperature Dependence of $V_{BG}$


For  $T = T_0 + \Delta T$  and  $\ln(1 + \delta) \approx \delta - \frac{1}{2}\delta^2$ , we have

$$V_T = V_{T_0} \left( 1 + \frac{\Delta T}{T_0} \right)$$
$$\ln\left(\frac{T}{T_0}\right) = \ln\left(1 + \frac{\Delta T}{T_0}\right) \approx \frac{\Delta T}{T_0} - \frac{1}{2} \frac{\Delta T^2}{T_0^2}$$

then

$$V_{BG} = V_{G0} + nV_{T_0} (\gamma - \chi) \left( 1 - \frac{1}{2} \frac{\Delta T^2}{T_0^2} \right)$$

 Hence,  $V_{BG}$  peaks at  $V_{BG0} = V_{BG}(T_0)$ , and  $V_{BG}(T) < V_{BG}(T_0)$ :



# Direct Design of $V_{BG}$

A direct consideration of a zero-TC voltage reference without resorting to semiconductor physics is to recognize that

$$\frac{dV_{BE}}{dT} = -2\text{mV} / ^\circ\text{C} \sim -2.2\text{mV} / ^\circ\text{C}$$


while the thermal voltage has a positive TC:

$$\frac{dV_T}{dT} = \frac{k}{q} = \frac{V_T}{T} = +86.25\mu\text{V} / ^\circ\text{C}$$

The bandgap voltage is then generated by

$$V_{BG} = V_{BE} + MV_T$$

 with  $M = 23.2$  for  $dV_{BE}/dT = -2\text{mV}/^\circ\text{C}$ .




# TC of Voltage References

The IC industry defines TC of  $V_{REF}$  as:

$$TC = \frac{|V_{REF,max} - V_{REF,min}|}{T_2 - T_1} \quad \text{in mV / } ^\circ\text{C}$$
$$= \frac{|V_{REF,max} - V_{REF,min}| / V_{REF,ave}}{T_2 - T_1} \quad \text{in ppm / } ^\circ\text{C}$$

 Moreover, due to simulation and fabrication variations, the measured zero TC point may not be at exactly the midpoint of the temperature range:



## TC of BGR

For the ideal I-V curve with the temperature range of  $2\Delta T$ , the TC of  $V_{BG}$  is given by

$$TC = \frac{1}{2} n V_{T_0} (\gamma - \chi) \frac{\Delta T^2}{T_0^2} \frac{1}{2\Delta T}$$

Let  $n(\gamma - \chi) = 2$ , and  $T_0 = 300K$  ( $27^\circ C$ ), then

$$V_{BG} = 1.205 + 2 \times 25.88m \approx 1.26V$$

If the temperature range is from  $250K$  ( $-23^\circ C$ ) to  $350K$  ( $77^\circ C$ ), then  $T_0 = 300K$  ( $27^\circ C$ ),  $\Delta T = 50^\circ C$ ,  $T_2 - T_1 = 100^\circ C$ , and

$$\begin{aligned} TC &= \frac{1}{2} \times 2 \times 25.88m \times \frac{50^2}{300^2} \times \frac{1}{100} \\ &\approx 7.2\mu V / ^\circ C \\ &\approx 6ppm / ^\circ C \end{aligned}$$

In actual design, the TC figures would be (much) worse.

# Line Regulation

Line regulation is the change of  $V_{REF}$  w.r.t. the change in  $V_{dd}$ :

$$\begin{aligned}\text{line reg.} &= \frac{\Delta V_{REF}}{\Delta V_{dd}} && \text{in mV / V} \\ &= \frac{\Delta V_{REF} / V_{REF}}{\Delta V_{dd}} && \text{in \% / V}\end{aligned}$$

Transistor circuits are non-linear circuits for large signal changes, and hand analysis is impossible. It could be obtained by simulation. In datasheets, line regulation is usually measured:

- Find  $V_{dd}(\text{min})$  such that the voltage reference is barely operative
- Measure points range from  $V_{dd}(\text{min}) + 0.2\text{V}$  to  $V_{dd}(\text{max})$
- Compute line regulation

# Power Supply Rejection

For a good voltage reference (also for bandgap reference and linear regulator), the output voltage should be a weak function w.r.t. the supply voltage. Hence, a small signal parameter, the power supply rejection, gives good indication of line regulation.

**Power supply rejection (PSR)** is the small signal change of  $V_{BG}$  w.r.t. the small signal change in  $V_{dd}$ .

In transfer function form: 
$$PSR = \frac{V_{bg}}{V_{dd}}$$

In dB: 
$$PSR = 20 \times \log \left| \frac{V_{dd}}{V_{bg}} \right|$$

Usually  $|v_{bg}/v_{dd}| < 1$ , but we customarily give a positive PSR in dB.

Note: Line reg.  $\approx PSR \times \Delta V_{dd}$

# Load Regulation and Output Impedance

Load regulation is the change of  $V_{\text{REF}}$  w.r.t. the change in  $I_o$ :

$$\begin{aligned}\text{load reg.} &= \frac{\Delta V_{\text{REF}}}{\Delta I_o} && \text{in mV / mA} \\ &= \frac{\Delta V_{\text{REF}} / V_{\text{REF}}}{\Delta I_o} && \text{in \% / mA}\end{aligned}$$

In datasheets, load regulation is usually measured. Moreover, many BGRs cannot drive resistive loads, and load regulation is not included.

In the small signal limit, load regulation is the output impedance:

$$R_{o(\text{REF})} = \frac{dV_{\text{REF}}}{dI_o} \quad \text{in } \Omega$$



# Stability inferred from Line and Load Transients

For a feedback system, stability is usually determined by computing or measuring the loop gain and the **gain and phase margins**.

For a circuit, and especially an integrated circuit, however, due to loading effect and that loop-breaking points may not be accessible, stability is inferred by simulating or measuring the **line transient** and/or **load transient**.

If the circuit is stable and has adequate phase margin, line and load transients will show first order responses.

If the circuit is stable but has a phase margin less than  $70^\circ$ , line and load transients will show minor ringing.

If the circuit is unstable, line and load transient will show serious ringing/oscillation.

# Voltage References Criteria

A good voltage reference should have:

- (1) Low TC over a wide range of temperature
- (2) Low line regulation and good power supply rejection (PSR)
- (3) Good stability

Other considerations:

- (1) Low load regulation (if applicable)
- (2) Minimum  $V_{dd}$  for operation
- (3) Consume little power
- (4) Small area for resistors
- (5) Small area for compensation capacitor (if applicable)
- (6) Low noise
- (7) Long term stability

# PTAT Current Generator

A commonly used PTAT (proportional to absolute temperature) current generator is discussed in [Kessel 71] as shown below.

Now,

$$V_{BE1} = V_T \ln \frac{I_1}{NI_s} \quad V_{BE2} = V_T \ln \frac{I_2}{I_s}$$

Ignore early effect, then

$$I_2 = I_1$$


and

$$\Delta V_{BE} = V_{BE2} - V_{BE1} = V_T \ln(N)$$

$I_1$  (and  $I_2$ ) is a PTAT current:

$$I_1 = \frac{V_T}{R_1} \ln(N)$$

 (If TC of R is smaller than TC of  $V_T$ .)




# Basic BGR: Schematic

The simplest bandgap reference (BGR) consists of 4 transistors and 2 resistors. Positive TC is generated by the PTAT circuit consists of  $Q_1$ ,  $R_1$  and  $Q_2$  ( $n=1$  and large  $\beta$ ) [Meijer 76]\*. The reference voltage is

$$\begin{aligned} V_{BG} &= V_{BE2} + I_2 R_2 \\ &= V_{BE2} + \frac{R_2}{R_1} \ln(N) V_T \end{aligned}$$

Clearly,  $V_{BE2}$  has a  $-ve$  TC, and  $V_T$  has a  $+ve$  TC. Note that the TCs of  $R_1$  and  $R_2$  cancel each other. Also, the basic BGR, and all other BGRs, requires a start-up circuit (to be discussed later).

 \*The basic BGR is referenced, not proposed, in [Meijer 76].



## Basic BGR: Zero TC Condition

To achieve zero TC for  $V_{BG}$  at  $T_o$ , we set

$$\left. \frac{dV_{BG}}{dT} \right|_{T_o} = 0 \Rightarrow \frac{dV_{BE2}}{dT} + \frac{R_2}{R_1} \ln(N) \frac{V_{T_o}}{T_o} = 0$$

$R_1$  and  $R_2$  has the same TC, and  $(R_2/R_1) \times \ln(N)$  is independent of temp. In practice, TC of  $V_{BE2}$  is obtained by characterizing the process, and

$$\frac{dV_{BE}}{dT} \approx -2\text{mV} / ^\circ\text{C} \quad \text{to} \quad -2.2\text{mV} / ^\circ\text{C}$$


The transistor ratio  $N$  is usually taken as 4 or 8, and  $I_1$  is determined by the application, usually ranges from  $10\mu\text{A}$  to  $100\mu\text{A}$ . Let TC of  $V_{BE}$  be  $-2\text{mV}/^\circ\text{C}$  (from measurement), and  $T_o = 300\text{K}$ , then

$$\frac{R_2}{R_1} \ln(N) = \frac{2\text{m} \times T_o}{V_T} = \frac{2\text{m} \times q}{k} = \frac{3.2 \times 10^{-22}}{1.38 \times 10^{-23}} \approx 23.2$$


# Basic BGR: Matching Consideration

Common centroid layout for  $Q_1$  and  $Q_2$  for better matching:

$$Q_1:Q_2 = 4:1$$

 

$$Q_1:Q_2 = 8:1$$

 

Take  $N=8$ ,  $\Delta V_{BE} = V_T \ln(N) = 53.8\text{mV}$  at  $T=300\text{K}$ . For  $I_1=5\mu\text{A}$ ,

$$R_1 = \frac{V_T}{I_1} \ln(N) = 10.76\text{k}\Omega$$

$$R_2 = \frac{2m \times T_o \times R_1}{V_T \ln(N)} = 2m \times T_o \times I_1 = 120\text{k}\Omega$$

N.B. Some designs use  $N > 100$  to generate a large  $\Delta V_{BE}$  for better (lower) sensitivity due to process variations.

# Process and Simulation

Process: TSMC 0.18 $\mu$  deep n-well CMOS

NMOS:  $V_{tn}=0.44V$

PMOS:  $|V_{tp}|=-0.44V$

nnp:  $V_{BE}(4.7\mu A)=0.70V$

pnnp:  $V_{EB}(4.7\mu A)=0.64V$


Conditions:  $N=8$ ,  $I_1 \approx 4.6\mu A$  @25°C,  $R_1=10.8k\Omega$ ,  $R_2=91.6k\Omega$

Notes:

- (1) All voltage references in this talk are simulated using the same 0.18 $\mu$  CMOS process that also supports bipolar transistors.
- (2) With  $N=8$ ,  $R_2$  should be  $11.16 \times R_1 = 120.5k\Omega$ , but as the non-ideality factor  $n \neq 1$ ,  $R_2$  needed is smaller.
- (3) Current mirrors are simulated using PMOS transistors.
- (4) I thank Mr. Chenchang Zhan for assisting in all Spice simulations.
 
## Basic BGR: TC + Line Reg. Simulation

Instead of cutting and pasting the simulation results, they are redrawn using PowerPoint as shown below. Note that line regulation causes a larger error than the temperature dependence.





 
# Cross-Biased 4T Cell


The loop gain of the basic BGR is independent of  $R_2$ . Moreover, for  $N = 1$  and  $R_1 = 0\Omega$ ,  $T = -1$ , and the circuit oscillates.

Although the circuit oscillates, this cross-biased 4T cell, when properly connected, can be considered as a current mirror as well as a voltage mirror: current conveyer [Smith 68], or current-voltage mirror (CVM) [Lam 08]. More on this later.




UNSTABLE  
by  
themselves!

 But could  
be useful if  
properly  
connected.


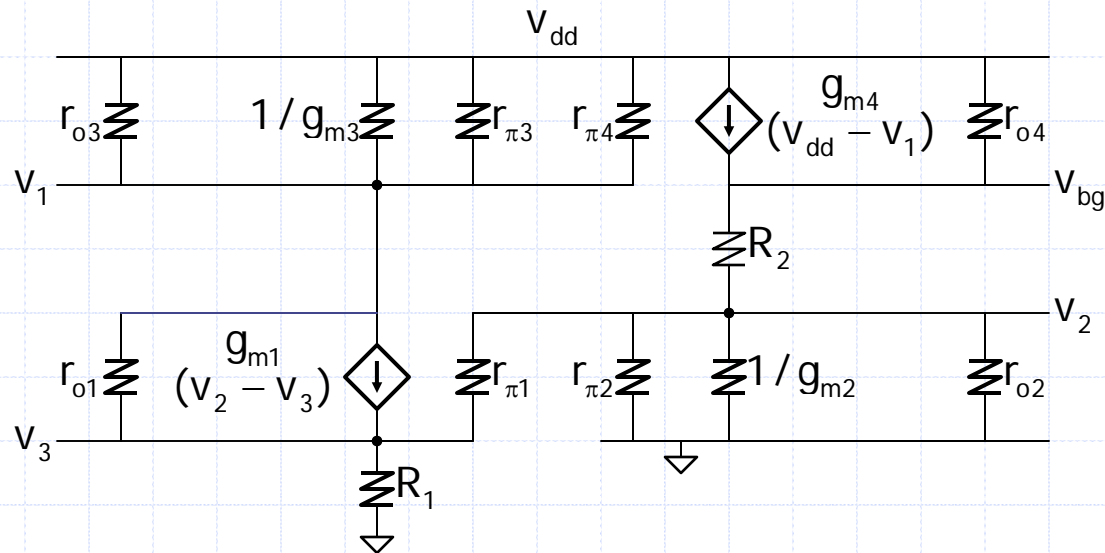
# Basic BGR: PSR Analysis

Small signal model for computing PSR of the basic BGR:




The computation is not trivial, but using appropriate approximations, it could be shown that, for  $r_{on}=r_{o1,2}$ ,  $r_{op}=r_{o3,4}$ ,

$$PSR = \frac{v_{bg}}{v_{dd}} = \left( 1 + \frac{R_2}{R_1} \ln(N) \right) \left( \frac{r_{on}}{r_{op} + r_{on}} + \frac{1}{\ln(N)} \right) \frac{1}{g_m (r_{op} || r_{on})}$$
 
# Basic BGR: Line Transient

Assume on-chip application such that  $C_{\text{Load}} = 10\text{pF}$ . The basic BGR is stable with a larger  $C_{\text{Load}}$ .



## Basic BGR: Performance Summary

Parameter	Computation	Simulation BSIM 3 ( $\beta_n=20$ )	Simulation Level 1 ( $\beta_n=80$ )
$R_2$ ( $R_1=10.8\text{k}\Omega$ )	120.5k $\Omega$	91.6k $\Omega$	108.3k $\Omega$
$V_{dd}(\text{min})=V_{BG}+0.2\text{V}$	1.45V	1.5V	1.5V
$V_{BG}$ ( $V_{dd}=1.7\text{V}$ )		1.118V	1.118V
TC	6ppm/ $^{\circ}\text{C}$	49ppm/ $^{\circ}\text{C}$	8ppm/ $^{\circ}\text{C}$
Loop gain	-0.324	-0.349	-0.324
PSR	32.7dB	33.6dB	32.4dB
Line regulation	23mV/V	22mV/V	25mV/V

N.B.

- (1)  $R_2$  is smaller than computed because  $n$  (ideality factor) is not 1.
- (2) BSIM3 simulation using parasitic  $Q_1$  and  $Q_2$  gives a much larger TC than predicted in pp.13. By substituting  $Q_1$  and  $Q_2$  with Level 1 npn with  $\beta_n=80$ , TC simulation is close to prediction.

# Symmetrical Matching of Bipolar Transistors

When a pair of bipolar transistors  $Q_1$  and  $Q_2$  of the same type are matched, the area ratio is designed to be the same as the intended current ratio. However, their collector-emitter voltages may be different and their collector currents are different due to early effect.

If  $Q_1$  and  $Q_2$  are forced (by an additional circuit) to have essentially the same  $V_C$ ,  $V_B$  and  $V_E$ , then they are called **symmetrically matched (SM)** [Lam 07b].

High performance BGRs inevitably employ symmetrical matching to improve PSR, although not explicitly stated [Brokaw 74].

# Basic SM BGR

For the basic BGR, line regulation and PSR could be improved by reducing the early effect of  $Q_1$  and  $Q_2$ . The  $Q_5$  and  $Q_6$  branch is added, forcing  $Q_1$  and  $Q_2$  to be symmetrically matched. By adding  $R_2$  at the collector of  $Q_3$ ,  $Q_3$  and  $Q_4$  are symmetrically matched.


The reference voltage is

$$V_{BG} = V_{BE5} + \frac{R_2}{R_1} \ln(N) V_T$$

The loop gain at breaking at  $V_2$  is

$$T = -\frac{V_{2o}}{V_{2i}} = \ln(N) \times g_m (r_{op} \parallel r_{on})$$

 
where all transistors have the same transconductance  $g_m$ , all npn have the same  $r_{on}$ , and all pnp have the same  $r_{op}$ . This  $T$  is -ve feedback.


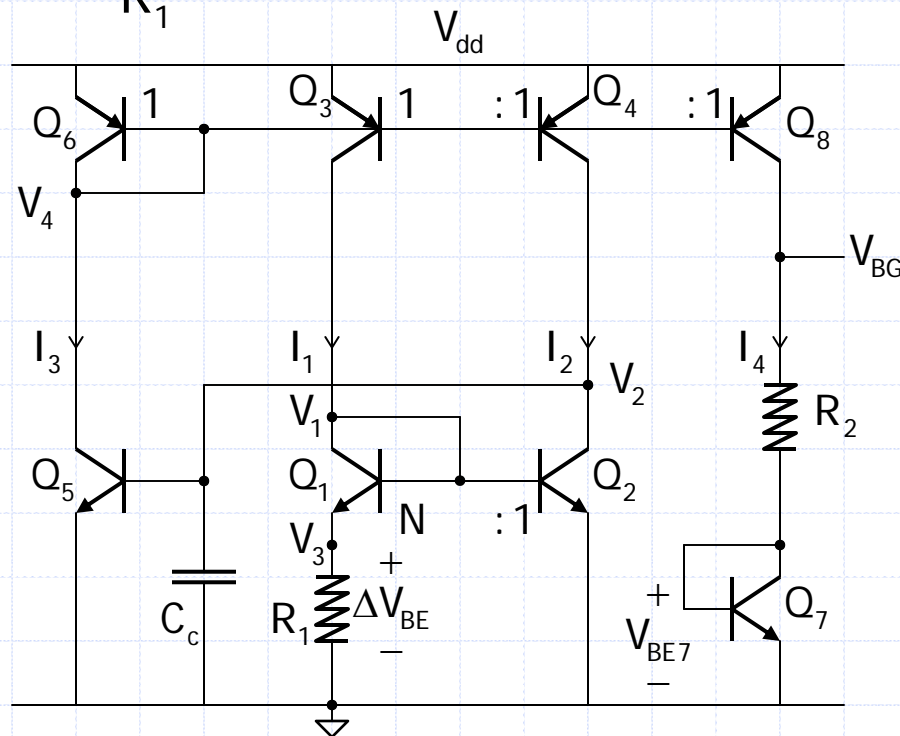
## Basic SM BGR (2)

To save a large  $R_2$ , a fourth branch ( $Q_7$  and  $Q_8$ ) could be added, and

$$V_{BG} = V_{BE7} + \frac{R_2}{R_1} \ln(N) V_T$$



N.B. Both basic SM BGRs are used in the industry but not discussed in the literature.

## Basic SM BGR: Performance Summary

Parameter	Computation	Simulation BSIM 3 ( $\beta_n=20$ )	Simulation Level 1 ( $\beta_n=80$ )
$R_2$ ( $R_1=10.8\text{k}\Omega$ )	120.5k $\Omega$	115.4k $\Omega$	105.7k $\Omega$
$V_{dd}(\text{min})$	1.45V	1.5V	1.3V
$V_{BG}$ ( $V_{dd}=1.7\text{V}$ )		1.3305V	1.3305V
TC	6ppm/ $^{\circ}\text{C}$	13.3ppm/ $^{\circ}\text{C}$	5.9ppm/ $^{\circ}\text{C}$
Loop gain	64.5dB	60.9dB	64.1dB
PSR		69dB	60dB
Line regulation		-0.36mV/V	-0.83mV/V

N.B. TC performance of the basic SM BGR is closer to prediction even for BSIM3 simulation using parasitic  $Q_1$  and  $Q_2$ .



## Op-Amp Based BGR (OP BGR)

The op-amp based bandgap was first discussed in [Kuijk 73] using Widlar current source [Widlar 65] with  $I_1 \neq I_2$ . For  $I_1 = I_2$ ,  $Q_1$  and  $Q_2$  will have different sizes (N:1). The op-amp A(s) forces  $I_1 = I_2$ , and  $I_1$  is a PTAT current:


$$V_{BE2} - V_{BE1} = V_T \ln(N) = I_1 R_1$$

$$V_{BG} = V_{BE2} + I_1 R_2$$

$$= V_{BE2} + \frac{R_2}{R_1} \ln(N) V_T$$


This  $V_{BG}$  relation is the same as that of the basic BGR. However, the total resistance is

$$R_T = R_1 + 2R_2.$$

 
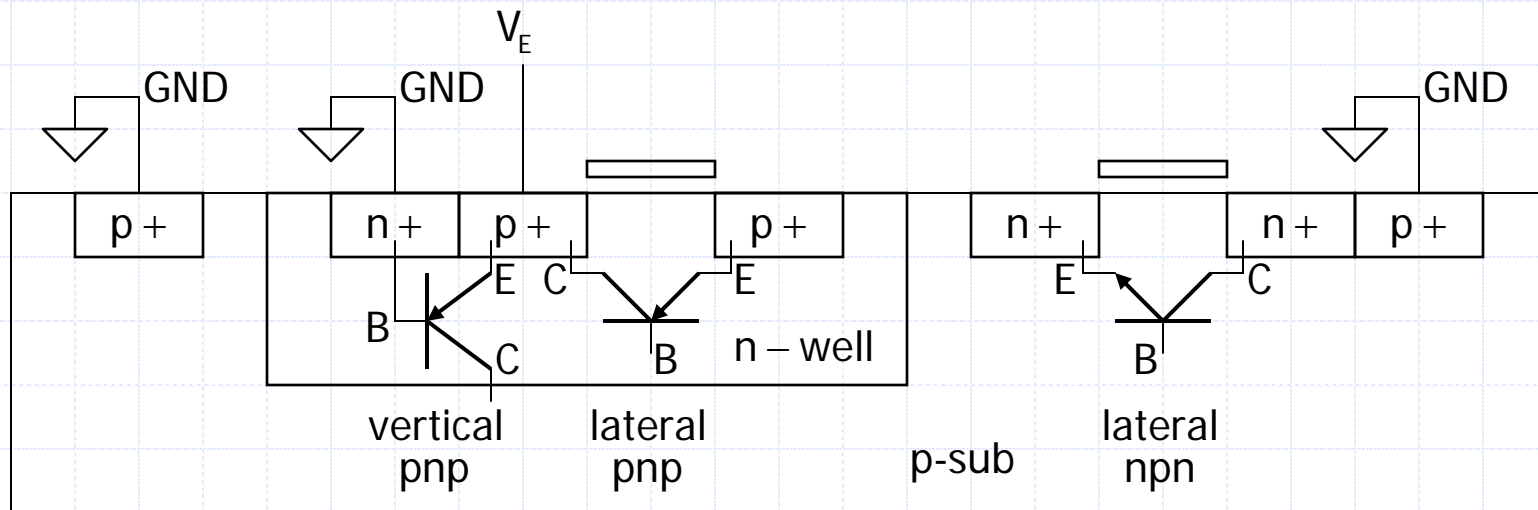
# BJTs in Digital CMOS Process



In a digital CMOS n-well process, parasitic lateral pnp, lateral npn and vertical pnp transistors could be identified. Vertical pnp transistors are more commonly used for their lower base resistance than lateral transistors. However, the collector, which is the p-sub, is restricted to be connected to ground.



Parasitic vertical pnp transistors were used in [Song 83].
  
## Op-Amp Based BGR (OP BGR)

For a standard CMOS digital process, BGR usually uses parasitic vertical pnp transistors. By drawing the CMOS op-amp based BGR (OP BGR) as shown on the right, two feedback loops, one negative and one positive, can easily be identified.



This BGR can drive resistive load if EA is properly designed.


# OP BGR: –ve and +ve Feedback Loops

Negative feedback loop:

$$T_- = \frac{1 + g_{m1}R_1}{1 + g_{m1}(R_1 + R_2)} \times A(s)$$

Positive feedback loop:
 
$$T_+ = \frac{-1}{1 + g_{m1}R_2} \times A(s)$$



For stability, we need  $|T_-| > |T_+|$ , and this criterion is satisfied by the above two relations.

The above  $T_-$  and  $T_+$  ignore parasitic capacitors of the transistors and resistors. By accounting for all parasitics, we require  $|T_-(j\omega)| > |T_+(j\omega)|$  for all frequencies.

## OP BGR: System Loop Gain

By breaking the loop at the output of the op-amp  $V_a$ , the system loop gain  $T(s)$  is given by


$$\begin{aligned} T &= T_- - T_+ \\ &= \left( \frac{1 + g_{m1}R_1}{1 + g_{m1}(R_1 + R_2)} - \frac{1}{1 + g_{m1}R_2} \right) \times A(s) \end{aligned}$$

Stability of a system is determined by the system loop gain, however, parasitic capacitors complicate the loop gain expression, and may not be too useful in compensation consideration:

⇒ Considering  $T_-(s)$  and  $T_+(s)$  for stability is more direct.

An example is shown in designing the current-mirror (CM) BGR.

Let the gate overdrive voltage be  $V_{gsn} - V_{tn} = |V_{gsp}| - |V_{tp}| = V_{ov}$ .

 


For NMOS input, we need

$$V_{EB2} > V_{tn} + 2V_{ov}$$

$V_{EB2}$  ranges from 0.5V to 0.7V

$$\Rightarrow V_{tn} < 0.2V$$

⇒ too tough to be satisfied

 

For PMOS input, we need

$$V_{dd} > V_{EB2} + |V_{tp}| + 2V_{ov}$$


For  $V_{EB}=0.64V$ ,  $|V_{tp}|=0.44V$ ,

$$V_{OV} = 0.15V$$

$$\Rightarrow V_{dd}(\min) = 1.38V.$$

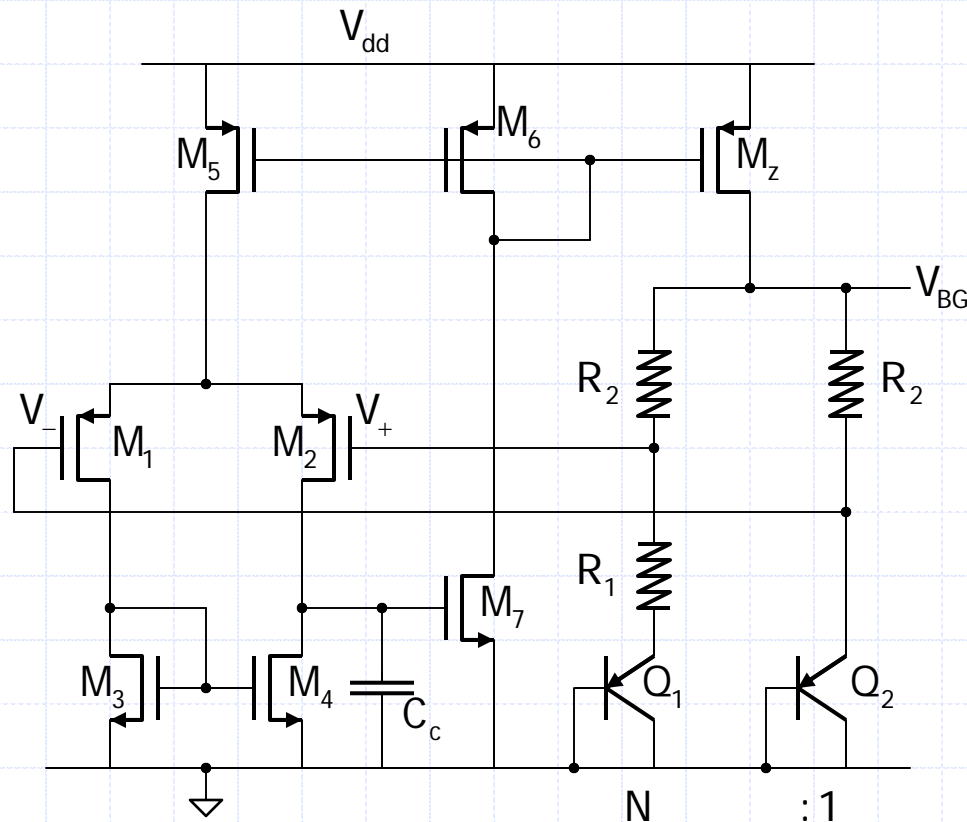
## OP BGR: Example

The OP BGR could be implemented by a 2-stage op-amp with a self-biasing scheme, and it resembles the CM BGR to be discussed in terms of feedback connections. Note that a start-up circuit is needed.


 
## OP BGR: Offset Error

For a bipolar op-amp, the offset voltage could be as low as 1mV, while for a CMOS op-amp, the offset voltage could be a few mV.



By accounting for  $V_{os}$ , it can be shown that [Song 83]


$$V_{BG} = V_{EB2} + \frac{R_2}{R_1} \ln(N) V_T - \left(1 + \frac{R_2}{R_1}\right) V_{os}$$





## $T_+$ and $T_-$ of CM BGR

Note that  $V_{d1}$  and  $V_{d2}$  generate the same reference voltage, but the reference output should be taken at  $V_{d2}$ , because with the filtering capacitor  $C_{OUT}$ , the positive feedback loop then has an even lower gain at high frequencies, satisfying  $|T_-(j\omega)| > |T_+(j\omega)|$ .

 

With a PMOS input stage, and

$$V_{EB2} = 0.64V$$

$$|V_{tp}| = 0.44V$$



$$V_{ov} = 0.15V$$

The minimum  $V_{dd}$  is thus

$$V_{dd}(\min) = V_{BE2} + |V_{tp}| + 2V_{ov} = 1.38V$$



## CM BGR: Line Transient with cap. at $V_{d1}$

If  $C_{OUT}$  is connected at  $V_{d1}$ , then  $|T_+(j\omega)| > |T_-(j\omega)|$  at high frequencies, making the BGR unstable.

  


## CM BGR: Line Transient with cap. at $V_{d2}$

If  $C_{OUT}$  is connected at  $V_{d2}$ , then  $|T_+(j\omega)| < |T_-(j\omega)|$  for all frequencies, and the BGR is stable.

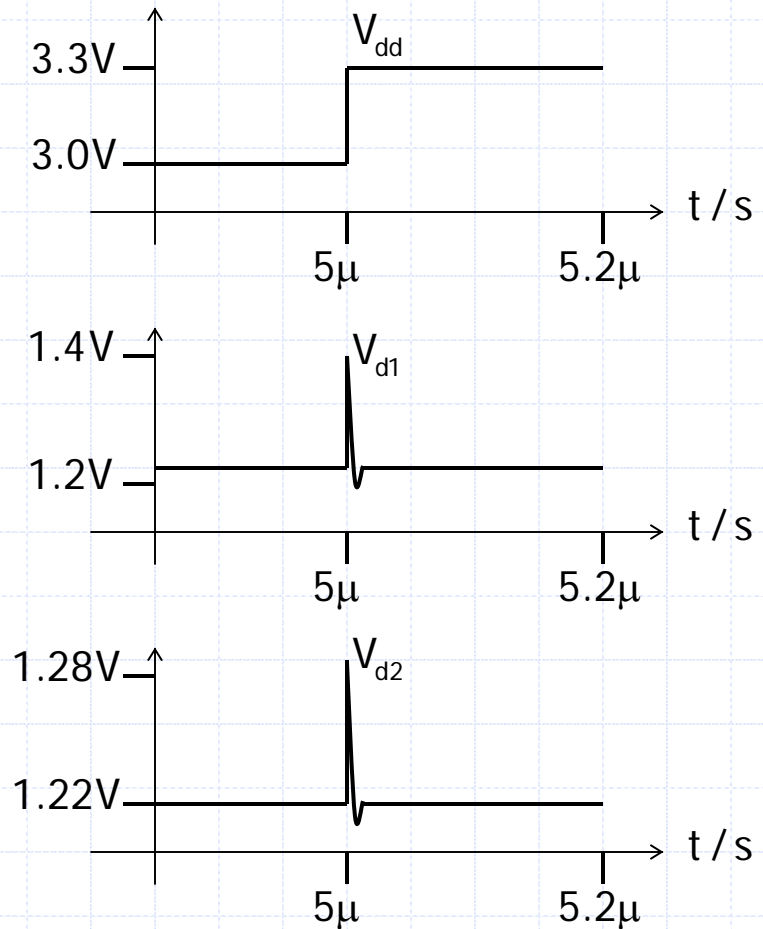 
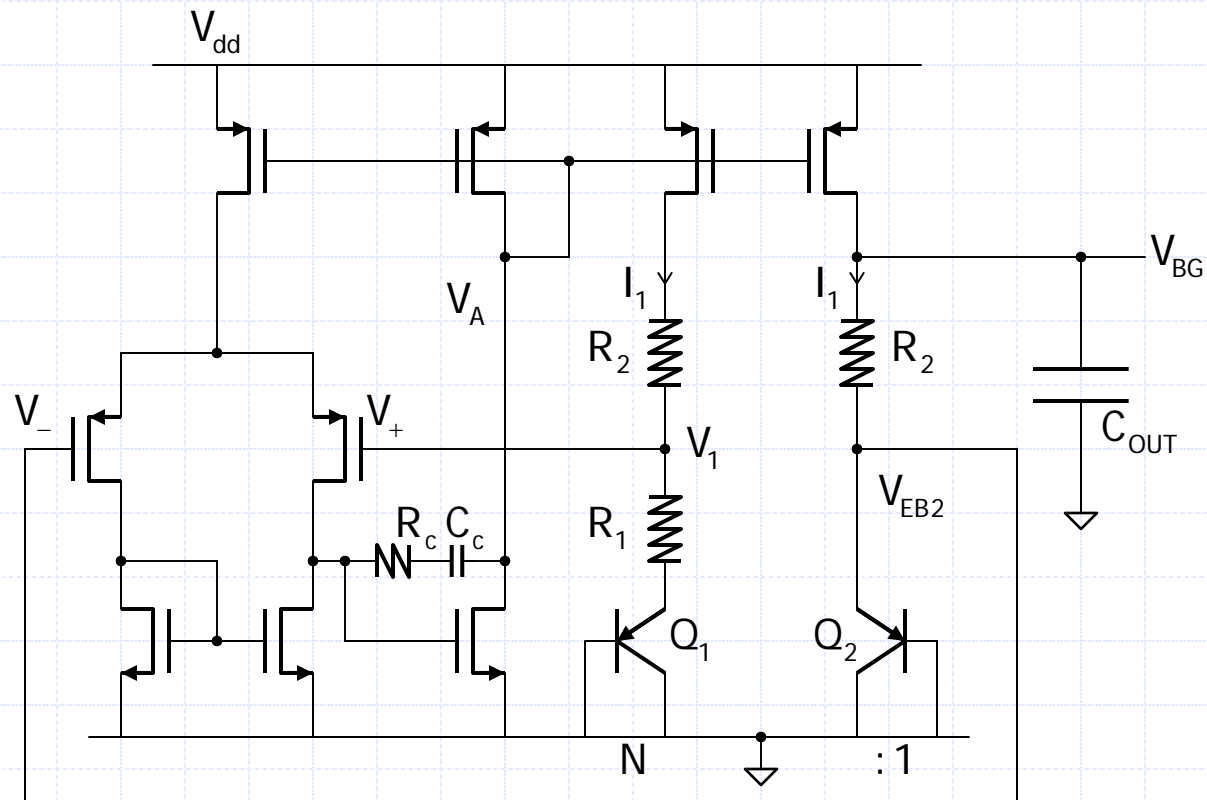
# CM BGR with PMOS Input

A 2-stage op amp could be used, and biased by the PTAT circuit.



# CM BGR: Performance Summary

Parameter	Computation	Simulation BSIM 3
$R_1$	12k $\Omega$	12k $\Omega$
$R_2$	133.9k $\Omega$	123.1k $\Omega$
$R_T$	279.8k $\Omega$	258.2k $\Omega$
$I_{pnp}$	4.75 $\mu$ A	4.75 $\mu$ A
$I_{op}$	9.5 $\mu$ A	9.5 $\mu$ A
$I_{total}$	19 $\mu$ A	19 $\mu$ A
$C_c$		200fF
$V_{dd}(\text{min})$	1.38V	1.5V
$V_{BG} (V_{dd}=1.7V)$		1.2757V
TC	6ppm/ $^{\circ}$ C	7.26ppm/ $^{\circ}$ C
PSR		79dB
Line regulation		+0.12mV/V

# BGR with Folded Resistor: FR BGR

In [Neuteboom 97], the resistors  $R_2$  is folded down to decrease the requirement of  $V_{dd}$ , using a special process. With  $I_1=I_2=I_3$ :


$$I_3 = \frac{V_T \ln(N)}{R_1} = \frac{V_{REF}}{R_2} + \frac{V_{REF} - V_{EB3}}{R_3}$$

$$\Rightarrow \frac{V_{REF}}{R_2} + \frac{V_{REF}}{R_3} = \frac{V_{EB3}}{R_3} + \frac{V_T \ln(N)}{R_1}$$

$$\Rightarrow V_{REF} = \frac{R_2}{R_2 + R_3} \left( V_{EB3} + \frac{R_3}{R_1} \ln(N) V_T \right)$$

For  $R_2 = R_3$ , then  $R_T = R_1 + 2R_2$ , and
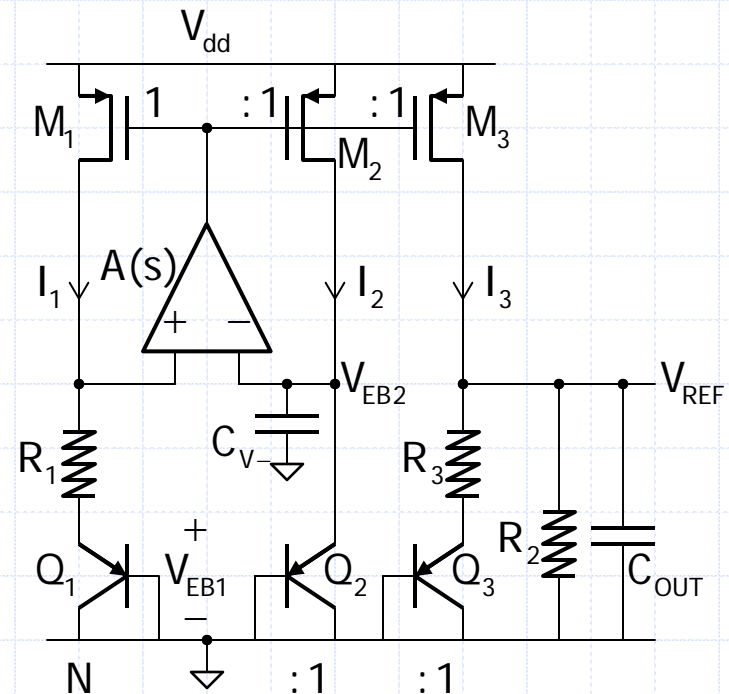
$$V_{REF} = \frac{1}{2} \left( V_{EB3} + \frac{R_2}{R_1} \ln(N) V_T \right)$$



Using a normal process,  $V_{dd(min)}$  is still  $V_{EB2} + |V_{tp}| + 2V_{ov}$ .

# BGR with Symmetrical Folded Resistors: SFR BGR

In [Banba 99], both branches of  $R_2$  are folded down to generate a zero-TC current  $I_3$ . With  $I_1 = I_2 = I_3$ :


$$I_1 = \frac{V_{EB2}}{R_2} + I_{R_1}$$

$$\Rightarrow I_1 = \frac{V_{EB2}}{R_2} + \frac{V_T \ln(N)}{R_1}$$

$$\Rightarrow V_{REF} = \frac{R_3}{R_2} \left( V_{EB2} + \frac{R_2}{R_1} \ln(N) V_T \right)$$

For  $R_3 = R_2/2$ ,  $R_T = R_1 + 2\frac{1}{2}R_2$ , and
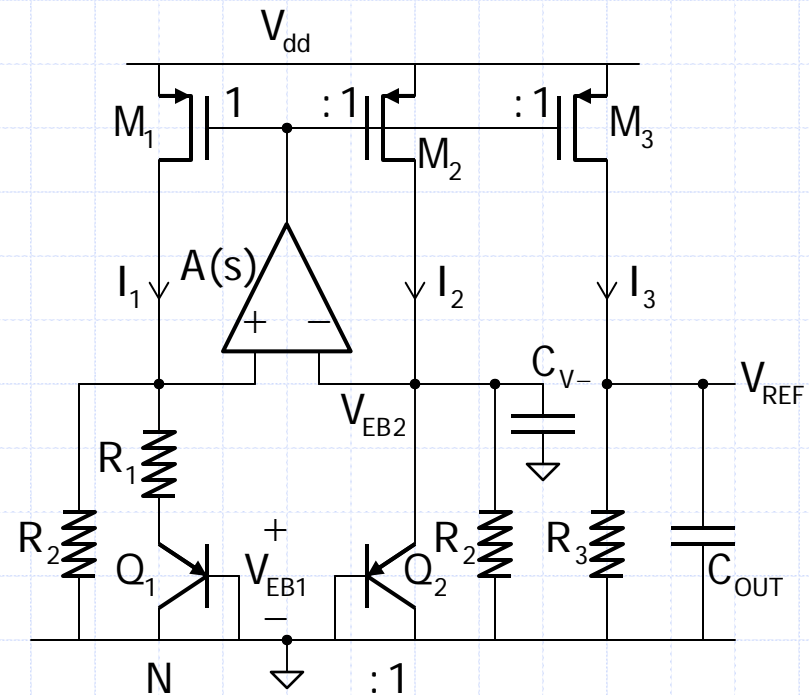
$$V_{REF} = \frac{1}{2} \left( V_{EB2} + \frac{R_2}{R_1} \ln(N) V_T \right)$$





# FR BGR and SFR BGR with Sub-1V Operation

In [Neuteboom 97], the  $0.8\mu$  process has  $|V_{tp}| = -0.7V$  and  $V_{tn} = 0.5V$ . Due to low  $V_{tn}$ , the op amp has an NMOS input stage, and

$$V_{dd}(\min) = V_{REF} + V_{ov}$$

For  $V_{REF} = 670mV$ , the BGR works at  $V_{dd} = 0.9V$  or lower.

In [Banba 99], the  $0.4\mu$  n-well process has  $|V_{tp}| = -1V$ ,  $V_{tn} = 0.7V$ , and native NMOS with  $V_{tn(native)} = -0.2V$ . The op amp uses a native NMOS input stage, and


$$V_{dd}(\min) = V_{REF} + V_{ov}$$

For  $V_{REF} = 515mV$ , the simulated lowest  $V_{dd}$  is  $0.84V$ . However, all measurements in [Banba 99] used  $V_{dd}$  are larger than  $2.4V$ .

# BGR with Folded Resistor Dividers: FRD BGR

By using resistor dividers for  $R_2$  in [Banba 99], the  $V_{dd}$  requirement can truly be reduced [Leung 02], without using low  $V_{tn}$  for NMOS. With  $b = R_{2b}/(R_{2a} + R_{2b})$ , then

$$V_{dd}(\min) = bV_{EB2} + |V_{tp}| + 2V_{ov}$$

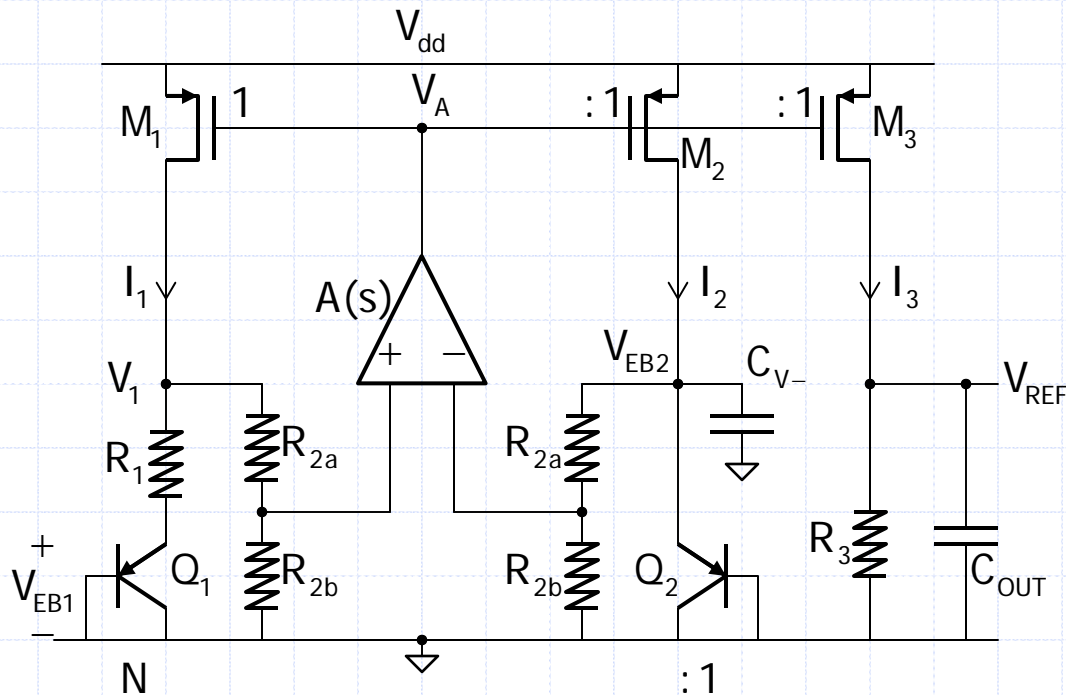

# SFR/FRD BGR: Performance Summary

Parameter	SFR BGR	FDR BGR
$R_1$	25k $\Omega$	25k $\Omega$
$R_2$	269.4k $\Omega$	268.5k $\Omega$ (b=0.6)
$R_3$	126k $\Omega$	125.5k $\Omega$
$R_T$	689.8k $\Omega$	687.5k $\Omega$
$I_{pnp}$	4.75 $\mu$ A	4.75 $\mu$ A
$C_{VBE2}$	5pF	5pF
$C_c / R_c$	60fF / 12k $\Omega$	60fF / 12k $\Omega$
$I_{total}$	24.25 $\mu$ A	24.25 $\mu$ A
$V_{dd}(\text{min})$	1.4V	1.2V
$V_{BG}$	0.6015V	0.6003V
TC	4.32ppm/ $^{\circ}$ C ( $V_{dd}=1.8V$ )	6.1ppm/ $^{\circ}$ C ( $V_{dd}=1.5V$ )
PSR	84.7dB	96.5dB
Line reg.	-0.12mV/V	-0.12mV/V


# Cross-Biased 4T Cell

PTAT loop is realized by forcing  $V_{EB1} + I_1 R_1 (=V_y) = V_{EB2} (=V_x)$ . The previous BGRs use an op-amp, but we may use a "voltage mirror" instead. The cross-biased 4T cell with the PMOS side connected to  $V_{dd}$  is such a voltage mirror.

A positive feedback loop is identified and the diode-connection must be at  $R_x$  with  $R_x < R_y$  to maintain stability.

The loop gain is
 
$$T = -\frac{V_{1o}}{V_{1i}} = -\frac{1 + g_{mn}R_x}{1 + g_{mn}R_y}$$



# BGR with 4T Current-Voltage Mirror

The 4T current-voltage mirror (CVM) forces  $V_y = V_x$ , and  $Q_1$ ,  $R_1$  and  $Q_2$  forms a PTAT loop with

$$I_1 = I_2 = \frac{V_T}{R_1} \ln(N)$$

The reference voltage is thus


$$V_{BG} = V_{EBZ} + \frac{R_2}{R_1} \ln(N) \times V_T$$

The loop gain of the 4T BGR is

$$T = -\frac{V_{1o}}{V_{1i}} = -\frac{1 + g_{mn} R_x}{1 + g_{mn} (R_1 + R_x)}$$


where  $R_x = 1/g_{mq}$ , with  $g_{mq}$  the transconductance of all pnp transistors, and
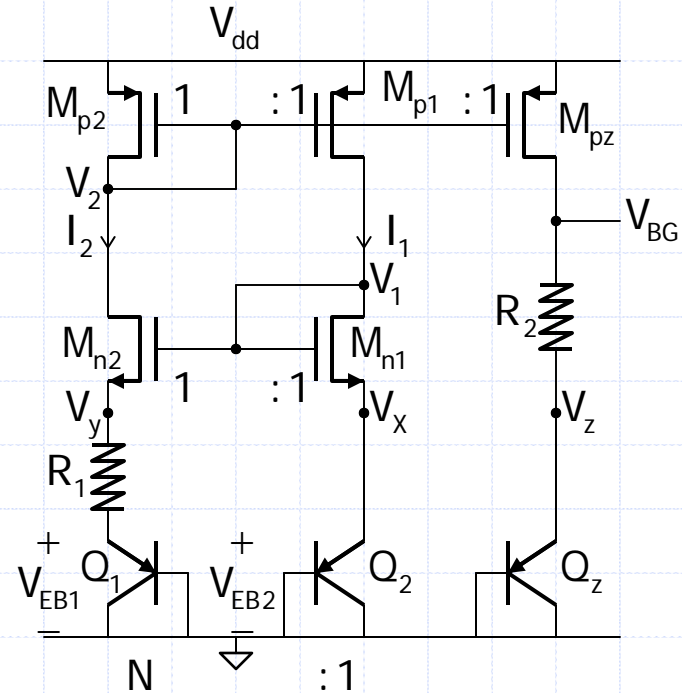
$$V_{dd(min)} = V_{EB2} + V_{tn} + 2V_{ov}$$


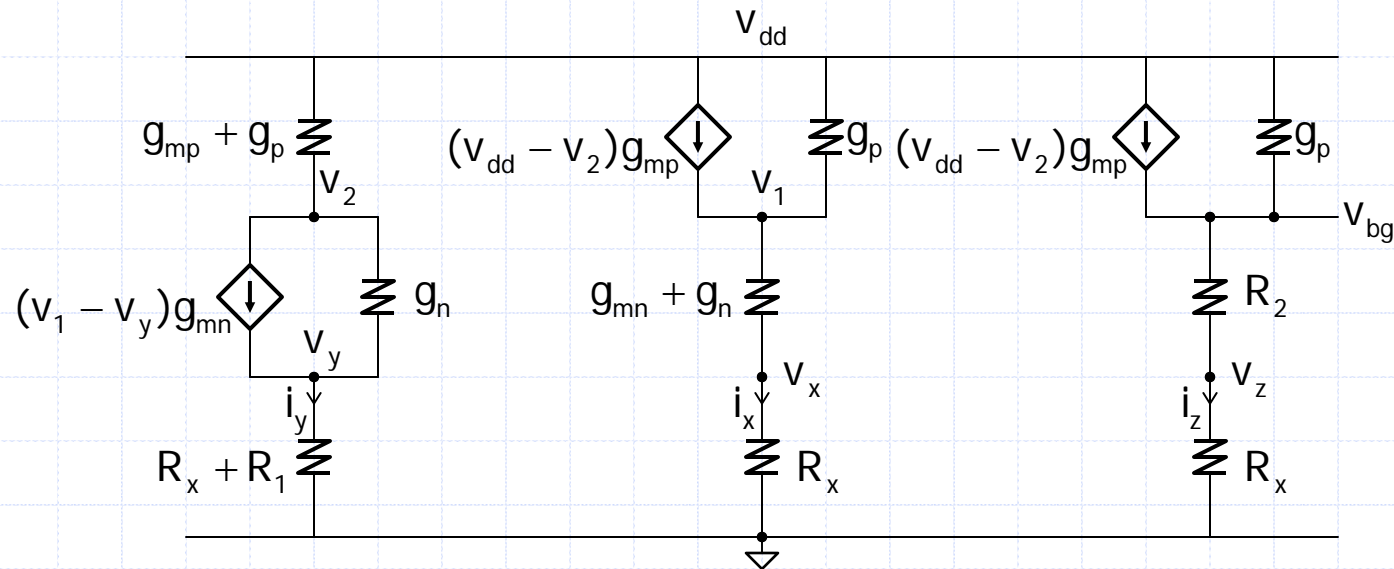
# 4T BGR: PSR Analysis

Small signal model for computing PSR of the 4T BGR:




With appropriate approximation, and  $r_{dsp}=1/g_p$ ,  $r_{dsn}=1/g_n$ , we arrive at

$$PSR = \frac{V_{bg}}{V_{dd}} = \frac{1 + r_{dsp}/r_{dsn} + g_{mn}(R_x + R_1)}{g_{mn}R_1} \frac{(R_x + R_2)}{r_{dsp}}$$
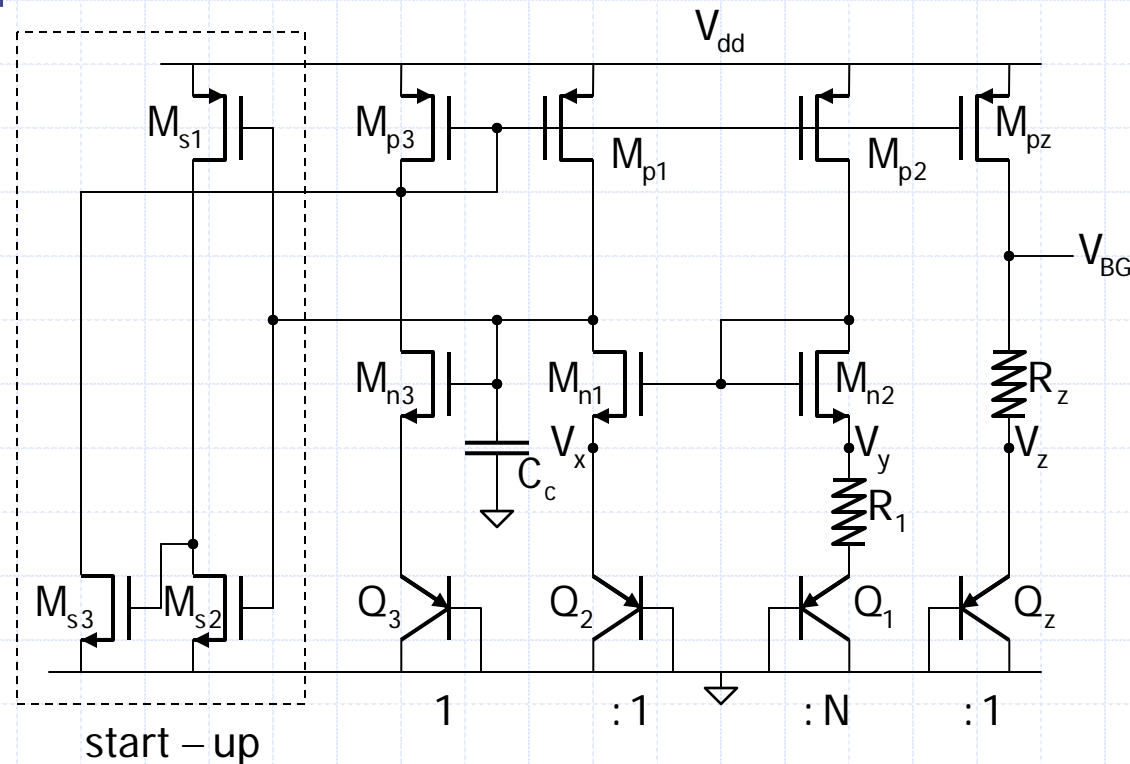
## 4T SM BGR


By adding the  $M_{n3}$  and  $M_{p3}$  branch,  $M_{n1}$  and  $M_{n2}$  are symmetrically matched. The diode-connection of NMOS is at  $Q_1$  rather than at  $Q_2$  to give negative feedback, and  $C_c$  is added for compensation [industry].



[industry]: circuit not published but used in the industry.
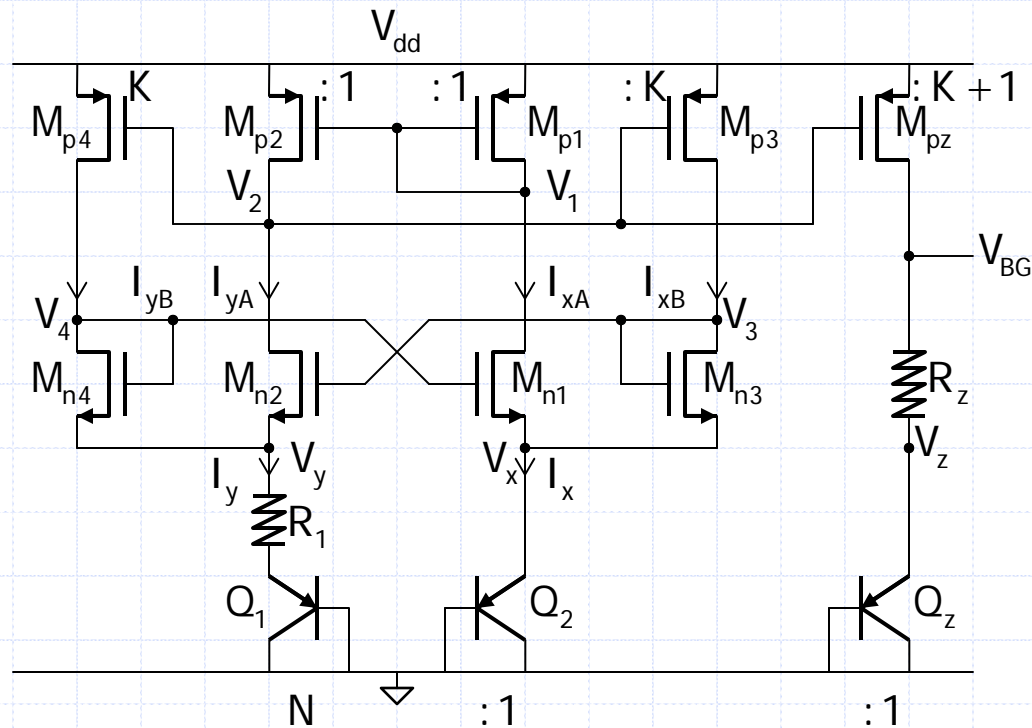
# 8T SM BGR

Another way to achieve symmetrical matching is to use an 8T SM CVM [Taylor 99]. A modified version is shown below [Lam 08]. For stability, we require  $K > 1$ , and a suggested value is  $K = 4$ .





## 8T SM BGR: Operation

When the PTAT loop is activated, the current  $I_X$  flows in  $Q_2$  is equal to  $I_{XA} + I_{XB}$ .

The W/L ratio of  $M_{p1}$  and  $M_{p3}$  is 1:K, and  $I_{XB}$  is approximately equal to  $K \times I_{XA}$  ( $M_{p1}$  and  $M_{p3}$  are not symmetrically matched).

To provide the correct gate drive for  $M_{p3}$ , the feedback action of the SM CVM drives  $V_2$  to be essentially equal to  $V_1$ , such that the X branch is symmetrically matched to the Y branch.

Now, with  $V_{SG}$  of  $M_{p1}$  being equal to  $V_{SG}$  of  $M_{p2}$ ,  $M_{p1}$  is then symmetrically matched to  $M_{p2}$ .


Arguing in a similar fashion, we conclude that all transistor pairs ( $M_{n1}, M_{n2}$ ), ( $M_{p1}, M_{p2}$ ), ( $M_{n3}, M_{n4}$ ) and ( $M_{p3}, M_{p4}$ ) are symmetrically matched and thus  $V_Y = V_X$ .

## 4T/8T BGRs: Performance Summary

Parameter	4T BGR	4T SM BGR	8T SM BGR
$R_1$	12k $\Omega$	12k $\Omega$	12k $\Omega$
$R_2$ ( $R_1=12\text{k}\Omega$ )	113.3k $\Omega$	123.9k $\Omega$	124.1k $\Omega$
$I_{\text{pnp}}$	4.5 $\mu\text{A}$	4.5 $\mu\text{A}$	4.5 $\mu\text{A}$
$C_c$	-	5pF	-
pnp	N+2	N+3	N+2
$I_{\text{total}}$	13.5 $\mu\text{A}$	18 $\mu\text{A}$	13.5 $\mu\text{A}$
$V_{\text{dd}}(\text{min})$	1.7V	1.8V	1.8V
$V_{\text{BG}}$ ( $V_{\text{dd}}=2\text{V}$ )	1.2142V	1.2815V	1.2701V
TC	11.9ppm/ $^{\circ}\text{C}$	5.44ppm/ $^{\circ}\text{C}$	6.1ppm/ $^{\circ}\text{C}$
PSR	20dB	50.3dB	44.1dB
Line reg.	42.1mV/V	-4.9mV/V	-5.8mV/V

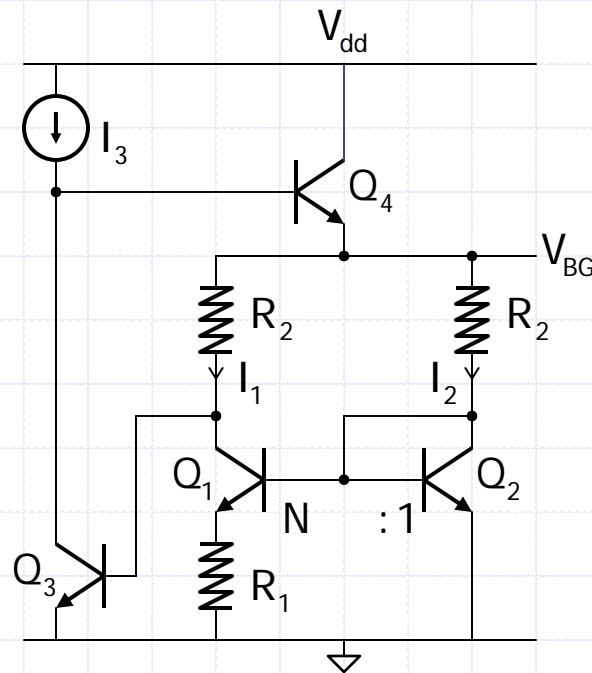
# Modified Widlar BGR

Widlar's original BGR [Widlar 71] has minor matching difficulties. A modified version with better matching is shown below [Gilbert 96].



 
# Brokaw BGR (1)

The Brokaw BGR is a popular topology for BJT process [Brokaw 74], and its CMOS variant is discussed in [Vittoz 79].


 
$$V_{BG} = V_{BE2} + 2 \frac{R_2}{R_1} \ln(N) V_T$$



$$V_{REF} = \left( 1 + \frac{R_A}{R_B} \right) V_{BG}$$


To compensate for base current error, set

$$R_3 = \frac{R_1}{R_2} \frac{R_A R_B}{R_A + R_B}$$
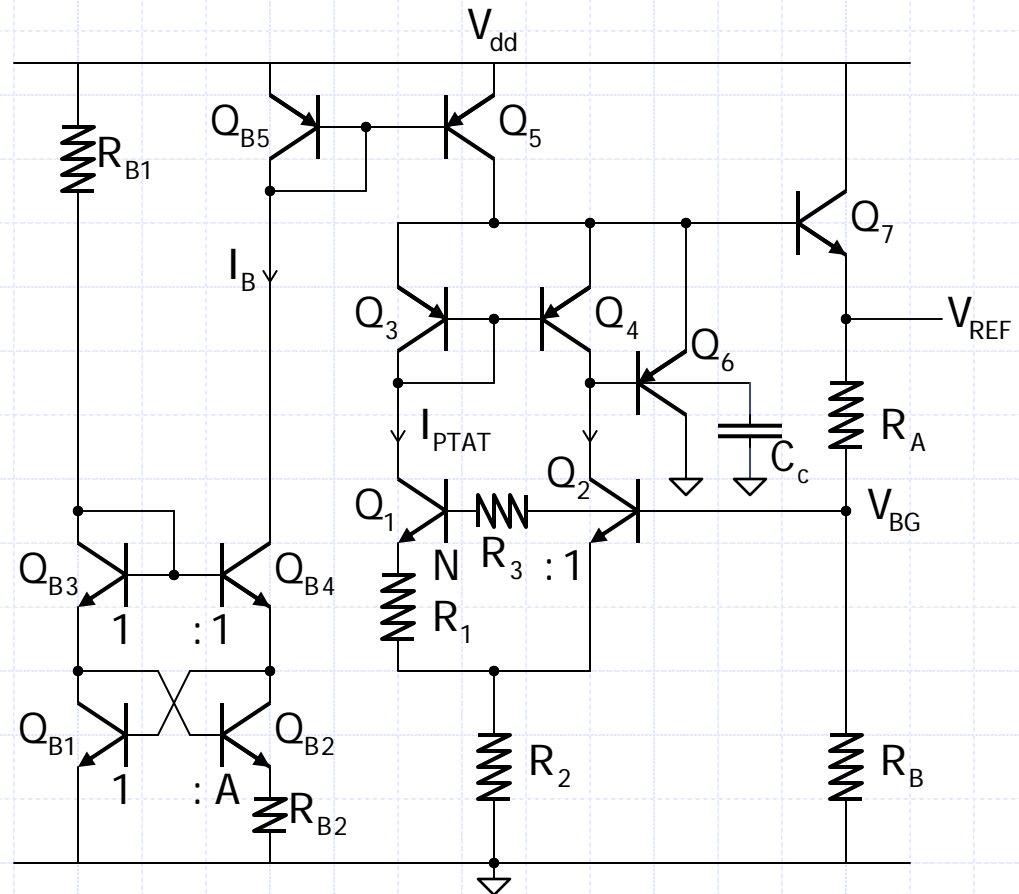
## Brokaw BGR (2)

To achieve symmetrical matching between  $Q_3$  and  $Q_4$ ,  $Q_6$  is added [Brokaw 74].

$Q_{B1}$ ,  $Q_{B2}$  and  $R_{B2}$  forms a PTAT loop to produce  $I_B$ , a PTAT current.  $Q_{B3}$  and  $Q_{B4}$  are used to minimize base current error.  $I_B$  is at least 3 times of  $I_{PTAT}$ , to supply enough base current to  $Q_7$  to drive resistive load.




# Start-Up Consideration

The basic BGR has two stable operation points:

- (1) Normal mode with  $V_{BG} \approx 1.2V$ ; and
- (2) Shutdown mode with  $V_1 = V_{dd}$  and  $V_2 = 0$ .

A start-up circuit should

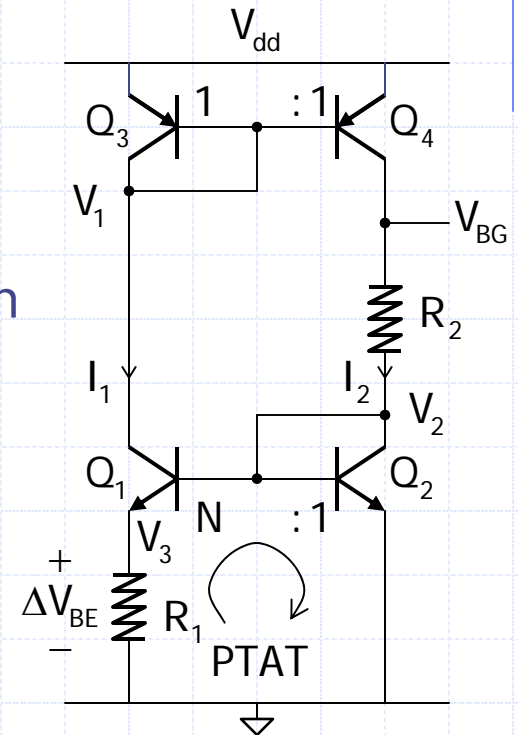- (1) automatically steer the BGR from the shutdown mode to the normal mode;
- (2) disconnect from the BGR when it is working in the normal mode; and
- (3) consume very little power.




# Basic BGR with CMOS Start-Up

Consider the  $0.18\mu$  CMOS process that supports bipolar transistors.



When BGR is shut down,  $V_1 = V_{dd}$ ,  $M_{s1}$  is off and  $M_{s2}$  is on, such that  $V_s$  is low, turning on  $M_{s3}$  that pumps current to  $Q_2$ .  $Q_1$  mirrors current to turn on  $M_3$ , and  $M_4$  mirrors current and the BGR works properly.

 $M_{s1}$  should be turned on hard by  $V_1$ , trying to source large current that puts itself into the linear region with a very small  $V_{sd1}$ , such that  $M_{s3}$  is shut off and isolated from the BGR.


  
# CMOS Start-Up Schemes

A start-up circuit is used to jumpstart the main circuit, and  $V_1$  and  $V_2$  are the normal operating voltages of the main circuit. The basic BGR may only use the P-startup circuit. Note that  $V_2$  is only 0.6V (at 27°C) and may be too low to turn on  $M_{s2}$  of the N-startup circuit.



Both the P-startup and the N-startup circuits consume quiescent current, and  $M_{s2}$  (P-startup) and  $M_{s1}$  (N-startup) should be made long.



# Trimming for Zero-TC

Consider the Brokaw BGR. The simulated BGR has zero-TC, giving, say,  $V_{BG}=1.263V$  at  $25^{\circ}C$ , and  $R_A$  and  $R_B$  are adjusted to give, say,  $V_{REF}=2.50V$ . Due to inaccurate modeling and process variations, the fabricated BGR will have a different  $V_{REF}$  and large TC.

A very accurate  $V_{REF}$  will need to trim for both zero-TC and accurate initial value. The zero-TC point is determined by  $R_1:R_2$ , while the initial accuracy of  $V_{REF}$  (at room temp.) is determined by  $R_A:R_B$ .

Trimming individual BGR for zero-TC is too time consuming. In practice, the zero-TC point is determined by fabricating and measuring the BGRs a few times using the same vendor and process. After finding the “optimal” ratio of  $R_1:R_2$ , this is then fixed for mass production and individual BGR will only be trimmed for initial accuracy.

# Trimming for Initial Accuracy

For  $V_{REF} = 2.50V \pm 1\%$  over  $T$  and  $V_{dd}$ , the initial accuracy should be  $V_{REF} = 2.50V \pm 0.25\%$  by trimming  $R_B$ . The LSB of 0.25% is 6.25mV, and for 4-bit trimming, the trimming range is  $\approx \pm 50mV$ .



Let  $I_{REF} = 5\mu A$ , such that  $R_A = 247.4k\Omega$  and  $R_B = 252.6k\Omega \pm 10k\Omega$ .  $R_B$  is divided into  $R_{B1} = 242.6k\Omega$  and  $R_{B2} = 18.75k\Omega$ .  $R_{B2}$  consists of 4 smaller resistors of 1.25k $\Omega$  (LSB), 2.5k $\Omega$ , 5k $\Omega$  and 10k $\Omega$  (MSB) that are connected in parallel with poly fuses ( $\approx 100\Omega$ ).

If the fabricated BGR behaves as designed, only 1 fuse (MSB fuse) is needed to be blown open. Otherwise, the BGR could still be trimmed up and down  $+43.75mV/-50mV$ .
  
# Trimming Circuit

Trimming is usually done during wafer testing. A poly fuse of around  $100\Omega$  needs 60mA to be blown open.


For  $R_{LSB} \gg R_{poly}$ : blow fuse to trim up.


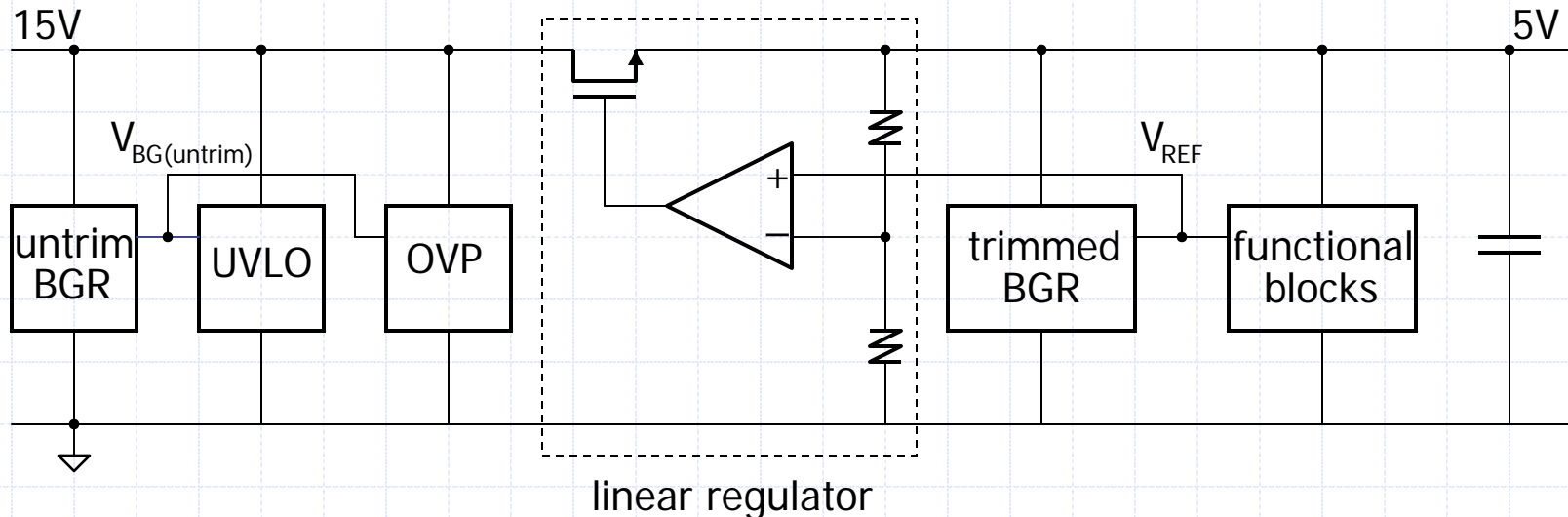
# Organization of BGRs in IC Systems

For a low-voltage system, e.g.,  $V_{dd}=5V$ , there is usually only one trimmed voltage reference.

For a system with  $V_{dd}=15V$ , there are usually two voltage references, one trimmed for accuracy, and a second one untrimmed and could work at very low voltage for start-up, UVLO (under voltage lockout) and OVP (over voltage protection).



# References: Books/Thesis

## Books / Book Chapters / Thesis:

- [Gilbert 96] B. Gilbert, "Monolithic voltage and current references: Theme and Variations," in [Huijsing 96], 1996.
- [Gray 01] P. Gray, P. Hurst, S. Lewis and R. Meyer, *Analysis and Design of Analog Integrated Circuits*, 4<sup>th</sup> Ed., Wiley, 2001.
- [Huijsing 96] J. H. Huijsing, R. van de Plassche and W. Sansen, *Analog Circuit Design*, Kulwer, 1996.
- [Johns 97] D. Johns and K. Martin, *Analog Integrated Circuit Design*, Wiley, 1997.
- [Lam 08] Y. H. Lam, *Differential Common-Gate Techniques for High Performance Power Management Integrated Circuits*, PhD Thesis, HKUST, Jan. 14, 2008.
- [Meijer 96] G. Meijer, "Concepts for bandgap references and voltage measurement systems," in [Huijsing 96], 1996.
- [Razavi 01] B. Razavi, *Design of Analog CMOS Integrated Circuits*, McGraw Hill, 2001.
- [R-Mora 02] G. A. Rincon-Mora, *Voltage References*, IEEE Press, 2002.
- [Sansen 06] W. Sansen, *Analog Design Essentials*, Springer, 2006.
- [Sze 81] S. M. Sze, *Physics of Semiconductor Devices*, 2<sup>nd</sup> Ed., Wiley, 1981.

# References: Current Sources

## Current Sources and Circuits:

- [Frederiksen 72] T. M. Frederiksen, "Constant current source," *US Patent 3,659,121*, Apr. 25, 1972.
- [Lam 07] Y. H. Lam, W. H. Ki and C. Y. Tsui, "Symmetrically matched voltage mirrors and applications therefor," *US Patent 7,215,187*, May 8, 2007.
- [Kessel 71] T. van Kessel and R. van der Plaasche, "Integrated linear basic circuits," *Philips Tech. Rev.*, pp.1-12, 1971.
- [Smith 68] K. C. Smith and A. Sedra, "The current conveyor: a new circuit building block," *Proc. of the IEEE.*, pp.1368-1369, 1968.
- [Widlar 65] R. J. Widlar, "Some circuit design techniques for linear integrated circuits," *IEEE Trans. Circ. Theory*, pp.586-590, 1965.

# IC References: BGR (1)

## Bandgap References:

- [Banba 99] H. Banba *et. al.*, "A CMOS bandgap reference circuit with sub-1-V operation," *IEEE J. on Solid-State Circ.*, pp.670-674, May 1999.
- [Brokaw 74] A. P. Brokaw, "A simple three-terminal IC bandgap reference," *IEEE J. on Solid-State Circ.*, pp.388-393, Dec. 1974.
- [Cheng 05] M. H. Cheng and Z. W. Wu, "Low-power low-voltage reference using peaking current mirror circuit," *Elect. Lett.*, pp.572-573, May 2005.
- [Gregorian 81] R. Gregorian, G. A. Wegner and W. Nicholson Jr., "An integrated single-chip PCM voice codec with filters," *IEEE J. Solid-State Circ.*, pp.322-333, Aug. 1981.
- [Kuijk 73] K. E. Kuijk, "A precision reference voltage source," *IEEE J. on Solid-State Circ.*, pp.222-226, June 1973.
- [Lam 09] Y. H. Lam and W. H. Ki, "CMOS bandgap references with self-biased symmetrically matched current-voltage mirror and extension of sub-1V design," *IEEE Trans. on VLSI Syst.*, accepted for publication.
- [Leung 02] K. N. Leung and P. Mok, "A sub-1-V 15-ppm/°C CMOS bandgap voltage reference without requiring low threshold voltage device," *IEEE J. on Solid-State Circ.*, pp.526-530, Apr. 2002.
- [Meijer 76] G. Meijer and J. B. Verhoeff, "An integrated bandgap reference," *IEEE J. on Solid-State Circ.*, pp.403-406, June 1976.



# IC References: BGR (2)

## Bandgap References (cont.):

- [Mok 04] P. Mok and K. N. Leung, "Design considerations of recent advanced low-voltage low-temperature-coefficient CMOS bandgap voltage reference," *IEEE Custom IC Conf.*, pp.635-642, Sept. 2004.
- [Neuteboom 97] H. Neuteboom, B. Kup and M. Janssens, "A DSP-based hearing instrument IC," *IEEE J. Solid-State Circuits*, pp. 1790-1806, Nov. 1997.
- [Song 83] B. S. Song and P. R. Gray, "A precision curvature-compensated CMOS bandgap reference," *IEEE J. on Solid-State Circ.*, pp.634-643, Dec. 1983.
- [Taylor 99] C. R. Taylor, "Current source, reference voltage generator, method of defining a PTAT current source, and method of providing a temperature compensated reference voltage," US Patent No. 5,936,392, Aug. 10, 1999.
- [Vittoz 79] E. A. Vittoz and O. Neyroud, "A low-voltage CMOS bandgap reference," *IEEE J. on Solid-State Circ.*, pp.573-577, June 1979.
- [Widlar 71] R. J. Widlar, "New developments in IC voltage regulators," *IEEE J. on Solid-State Circ.*, pp.2-7, Feb. 1971.



# **IC Design of Power Management Circuits (V)**

**Wing-Hung Ki**

**Integrated Power Electronics Laboratory**

**ECE Dept., HKUST**

**Clear Water Bay, Hong Kong**

**[www.ee.ust.hk/~eeki](http://www.ee.ust.hk/~eeki)**

**International Symposium on Integrated Circuits  
Singapore, Dec. 14, 2009**

## **Part V**

# **Development of Integrated Charge Pumps**

# Foreword

The first AC-DC switched-capacitor power converters (charge pumps) were invented in the 1930's, while DC-DC charge pumps found many applications in recent years. After seventy years of research and development, the study is still not systematic and not standardized. My study on AC-DC and DC-DC charge pumps suggests the following four areas of attention:

Analysis

Topology

Gate Control

Regulation

A comprehensive review of the development of charge pumps would definitely include the works from all over the world. However, due to limited time, I could only concentrate on the research efforts at HKUST, and in particular, my own research. I hope I could write up a better account in the future.

# Content

AC-DC and DC-DC Charge Pumps  
Step-Up, Step-Down, and Inverting Charge Pumps  
Single-Branch and Dual-Branch Charge Pumps

Linear (Dickson) Charge Pumps  
Fibonacci (Ueno) Charge Pumps  
Exponential Charge Pumps  
2N-X Charge Pumps

2-Phase Charge Pumps  
    Gate Control Strategies  
    ANTZ Topological Tree  
Multi-Phase Charge Pumps

Regulated Charge Pumps

# Switched-Capacitor Power Converters

Qn.

What is a switched-capacitor power converter (SCPC)?

Ans:

An SCPC converts an input power source to an output voltage that supplies power to a load, with power transfer components that consists of **only switches and capacitors**.

Currently, there are more step-up SCPCs than step-down SCPCs, and hence an SCPC is better known as a **Charge Pump (QP)**.

# Classification of Charge Pumps

A major classification of charge pumps is according to input:

- AC-DC charge pumps
- DC-DC charge pumps

In this talk, the focus is on DC-DC charge pumps. In particular, integrated step-up charge pumps.

# Classifications of DC-DC Charge Pumps

According to output vs input (with  $V_s > 0$ ):

$V_o > V_s$ : step-up charge pumps

$V_o < V_s$ : step-down charge pumps

$V_o < 0$ : inverting charge pumps

According to conversion ratio:

Linear charge pumps (Dickson charge pumps)

Fibonacci charge pumps (Ueno charge pumps)

Exponential charge pumps ( $2^N$  charge pumps)

2N-X charge pumps

According to ripple-reduction:

Single-branch charge pumps

Dual-branch charge pumps

According to phases:

2-phase charge pumps

Multi-phase charge pumps



# Step-Up Charge Pump

A **voltage doubler** (2X charge pump) is shown below.

Clock phases  $\phi_1$  and  $\phi_2$  are **non-overlapping** with appropriate voltages to switch on and off the switches **completely**.

When  $\phi_1=1$ ,  $C_1$  is charged to  $V_{dd}$ .

 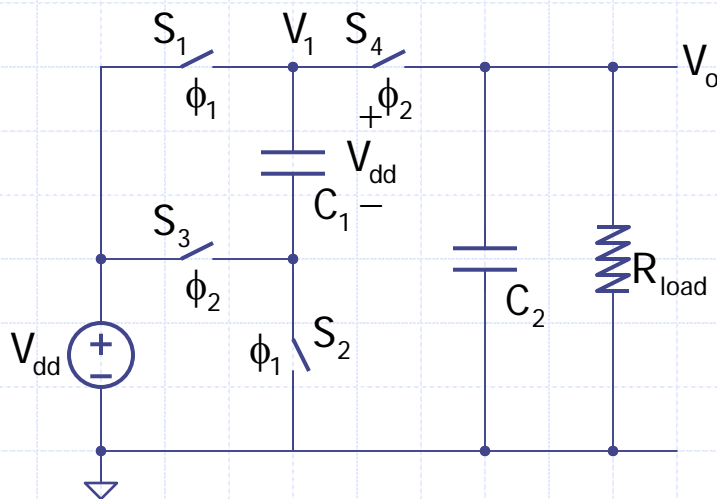When  $\phi_2=1$ ,  $C_1$  sits on top of  $V_{dd}$ , and charges  $V_1$  towards  $2V_{dd}$ .






# Step-Down Charge Pump

A **voltage divider** (divided by 2) is shown below.

When  $\phi_1=1$ ,  $C_1$  and  $C_2$  are charged in series to  $V_{dd}/2$ .

 When  $\phi_2=1$ ,  $C_1$  and  $C_2$  are connected in parallel to charge  $V_o$  towards  $V_{dd}/2$ .




# Inverting Charge Pump

An **inverting charge pump** is obtained by charging a capacitor in one direction and discharging it in the reverse direction.

When  $\phi_1=1$ ,  $C_1$  is charged to  $V_{dd}$ .

 When  $\phi_2=1$ , the “positive” plate of  $C_1$  is connected to ground, and the “negative” plate charges  $V_o$  towards  $-V_{dd}$ .



# Linear Charge Pump

Principle of operation (with ideal switches):


$\phi_1=1$ , ( $\phi_2=0$ ),  $C_1$  is charged to  $V_{dd}$ .

$\phi_2=1$ , top of  $C_1$  ( $V_1$ ) is pushed to  $2V_{dd}$ , charging  $C_2$  to  $2V_{dd}$ .

$\phi_1=1$  again, top of  $C_2$  ( $V_2$ ) pushed to  $2V_{dd}$ , charging  $C_3$  to  $3V_{dd}$ .

Similarly,  $V_o=V_5$  is then  $5V_{dd}$ .

 For  $N$  flying capacitors, the conversion ratio  $M = V_o/V_{dd}$  is  $N+1$ , and a linear charge pump (LQP) is obtained.




# Dickson Charge Pump

The first **integrated charge pump** is a linear charge pump presented in [Dickson 76], and is commonly known as **Dickson charge pump**.

Accounting for the diode drop  $V_d$ :

$$V_o = (N+1) \times (V_{dd} - V_d).$$

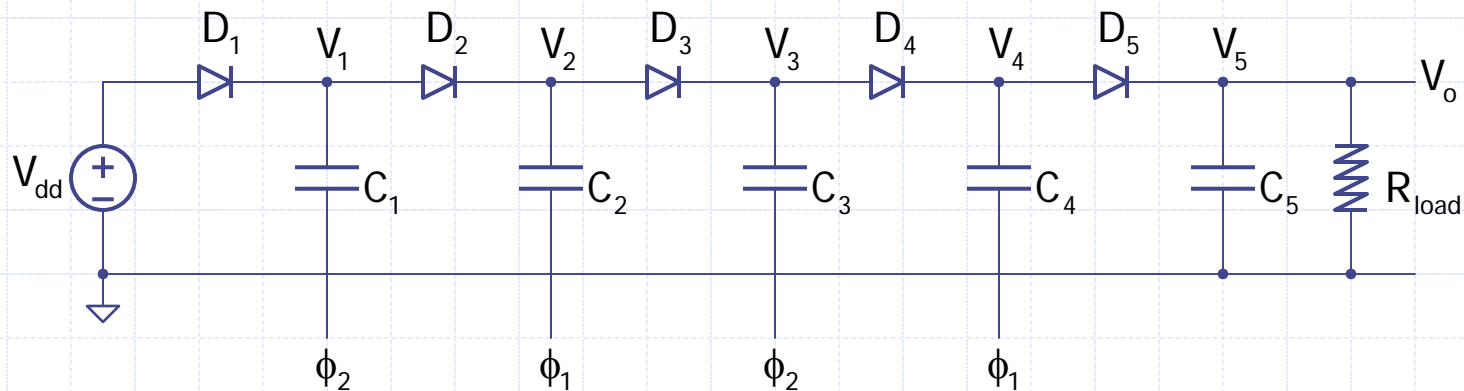


# LQP with Diode-Connected Transistors

In [Dickson 76], in fact, diode-connected transistors are used, and

$$V_o = (N+1) \times (V_{dd} - V_{tn(k)}).$$

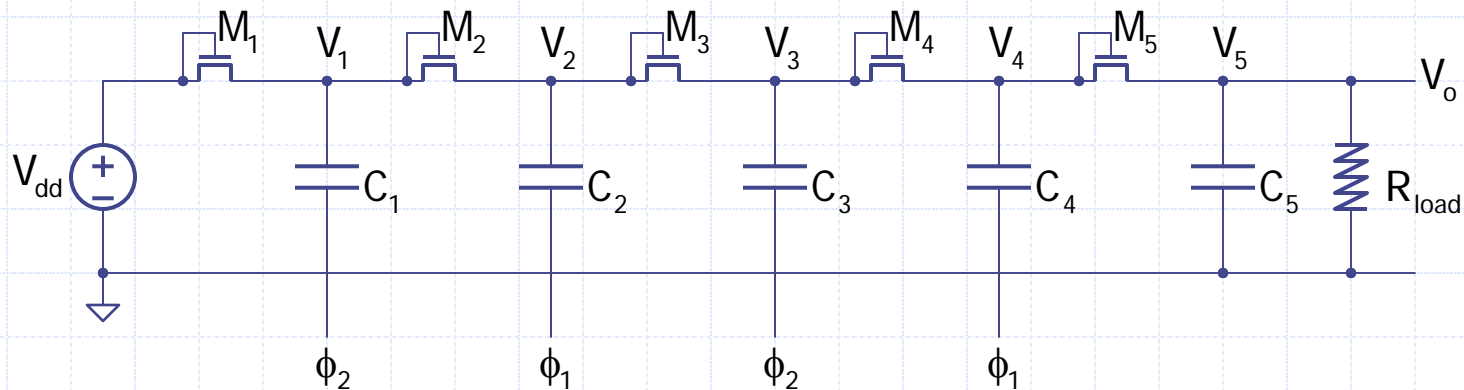For an n-well process, the p substrate (p-sub) has to be connected to GND, and high stage switches  $M_k$  ( $k > 1$ ) have body effect, and  $V_{tn(k+1)} > V_{tn(k)}$ . Eventually,  $V_{tn(k)} > V_{dd}$ , and adding more stages could not increase the conversion ratio.




# ON and OFF Conditions of a MOSFET


Qn. Can we design a charge pump with no loss due to  $V_d$  or  $V_{tn}$ ?

Ans. Surely we can, but first we need to determine the conditions for turning on and off an MOS (power) switch completely [Su 05].

ON

 

OFF

 

Assume  $V_{dd} > V_{tn}$ ,  $|V_{tp}|$ , and let  $V_{gk}$  be the gate voltage of  $S_k$ .


$S_k$  is NMOS: turned on if  $V_{gk} > (k+1)V_{dd}$ ; turned off if  $V_{gk} < (k-1)V_{dd}$ .

$S_k$  is PMOS: turned on if  $V_{gk} < (k-1)V_{dd}$ ; turned off if  $V_{gk} > (k+1)V_{dd}$ .

 
# Gate Control Schemes

In [Su 05], a systematic study of gate control for both NMOS and PMOS power switches is presented. For the 5X LQP,  $S_5$  has to be PMOS, and gate control circuits for PMOS are shown below.

**First-level gate control:** uses a PN pair to control the gate of  $M_k$ .



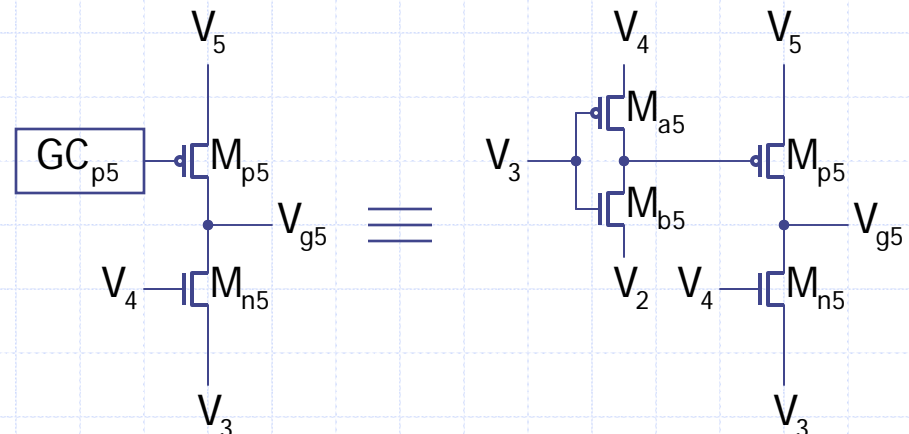**Second-level gate control:** treats  $M_{pk}$  (or  $M_{nk}$ ) as  $M_k$ , and generates  $GC_{pk}$  to drive  $M_k$  with a larger gate drive.



# Gate Control Candidates


	$(V_{Hk}, V_{pk})$	$(V_{nk}, V_{Lk})$
$GC_1$	$(V_1, \phi_2), (V_1, V_{dd}), (V_3, V_2), (V_5, V_4)$	$(V_{dd}, \phi_1), (\phi_2, \phi_1), (\phi_2, 0)$
$GC_2$	$(V_2, V_1), (V_4, V_3)$	$(V_1, V_{dd}), (V_1, \phi_2), (V_{dd}, \phi_2), (\phi_1, \phi_2), (\phi_1, 0)$
$GC_3$	$(V_3, V_2), (V_5, V_4)$	$(V_2, V_1), (V_{dd}, \phi_1), (\phi_2, \phi_1), (\phi_2, 0)$
$GC_4$	$(V_4, V_3)$	$(V_3, V_2), (V_1, V_{dd}), (V_1, \phi_2), (V_{dd}, \phi_2), (\phi_1, \phi_2), (\phi_1, 0)$
$GC_5$	$(V_5, V_4)$	$(V_4, V_3), (V_2, V_1), (V_{dd}, \phi_1), (\phi_2, \phi_1), (\phi_2, 0)$


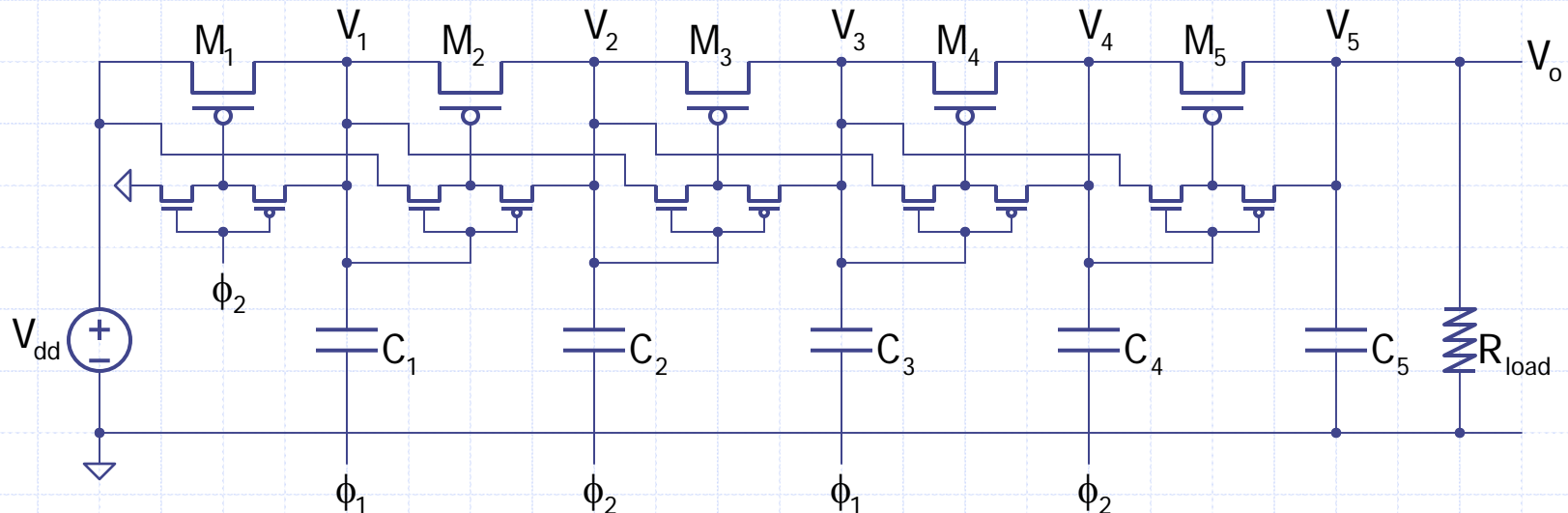
## 5X LQP w/o Drop Loss

The first LQP that completely eliminates (diode) drop loss is [Cheng 03] using the boldfaced options in the previous page. Only simulation was provided.

Implementation and measurement were finally realized in [Su 05] using the concept of **first-level gate control**. We labeled it LQP0.




# Improved 5X LQPs

The efficiency of **LQP0** could be improved by increasing the gate drives of some transistors to  $2V_{dd}$ :


**LQP1**: connect  $V_{L2}$  to  $\phi_2$  so gate drive of  $M_2$  is  $2V_{dd}$

**LQP2**: second-level gate control for  $M_5$

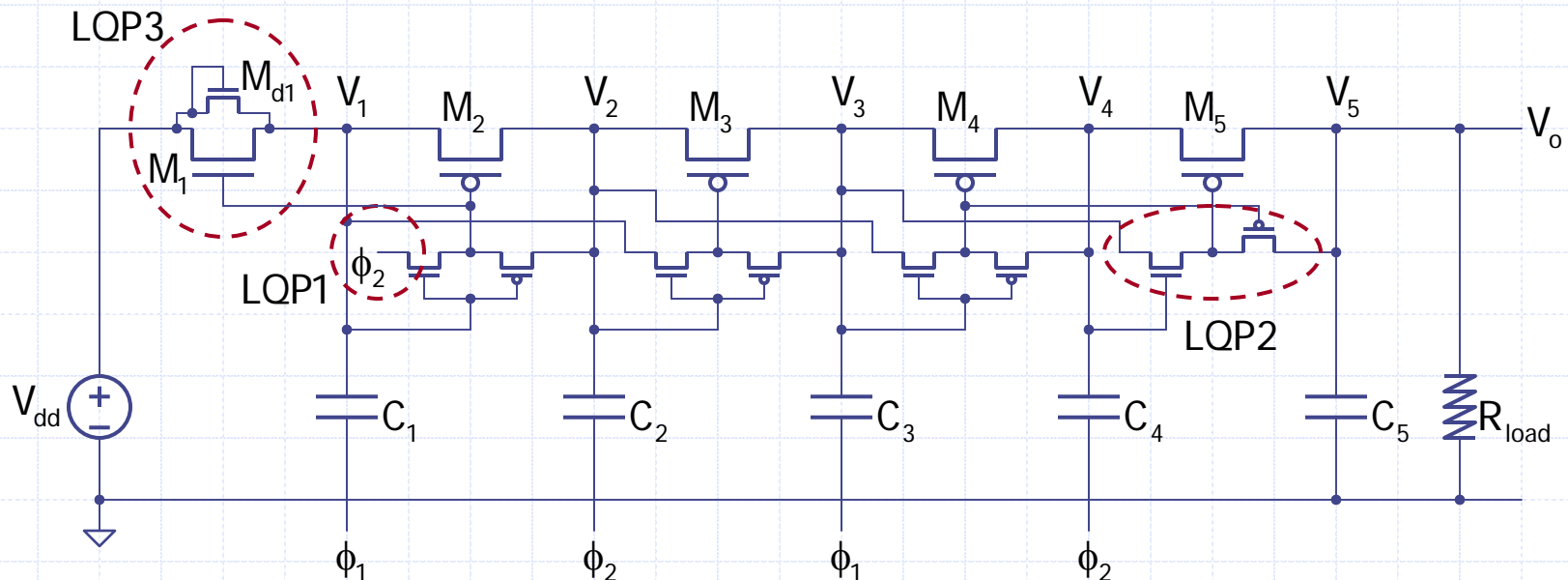
**LQP3**: change  $M_1$  to NMOS, but need  $M_{d1}$  for startup



# Performance Comparison of 5X LQPs

 

 $V_o$  vs  $V_{dd}$  for ideal and practical QPs




$V_o$  vs  $I_{load}$  for ideal and practical QPs
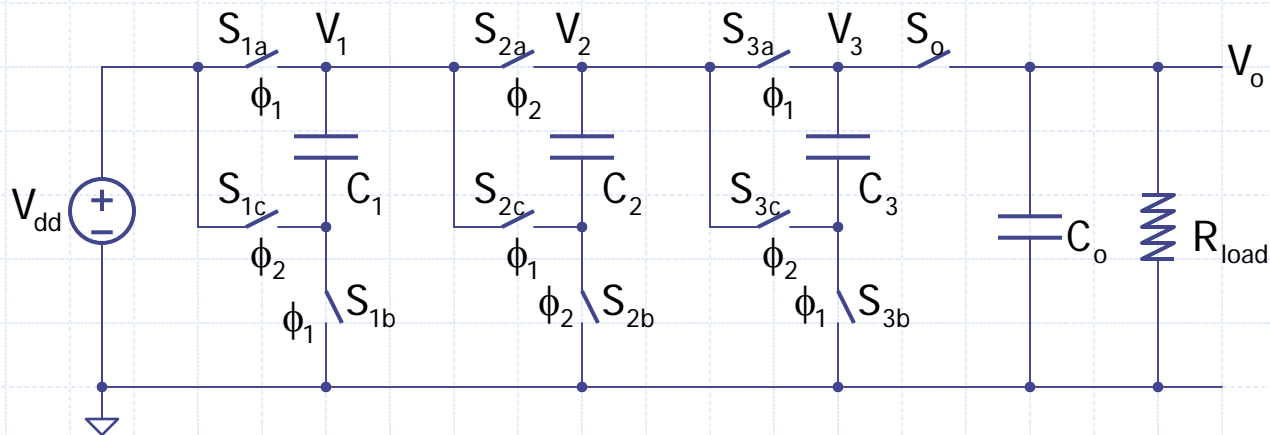
# Fibonacci Charge Pump

In [Ueno 91], a 2-phase charge pump is suggested that could realize a conversion ratio of 2, 3, 5, 8, 13, etc. that are Fibonacci numbers, and it could be referred as a **Fibonacci charge pump (FQP)**.

In [Makowski 97], it is shown, using graph theoretical concepts, that an FQP achieves the largest conversion ratio using the fewest capacitors among all 2-phase charge pumps.




# ANTZ Principle

Qn: How many 2-phase charge pumps could be realized given a specified number of flying capacitors?


Ans: To answer the above question, we need to formulate a systematic construction of charge pumps, the **ANTZ principle**: **All Negative Terminals** are connected to **Zero** (GND) during the charging phase [Su 07].

 It should be noted that all published charge pumps are abided by the ANTZ principle, and hence it is not a restrictive requirement.




# Charging and Pumping Scenarios

Consider a charge pump structure:

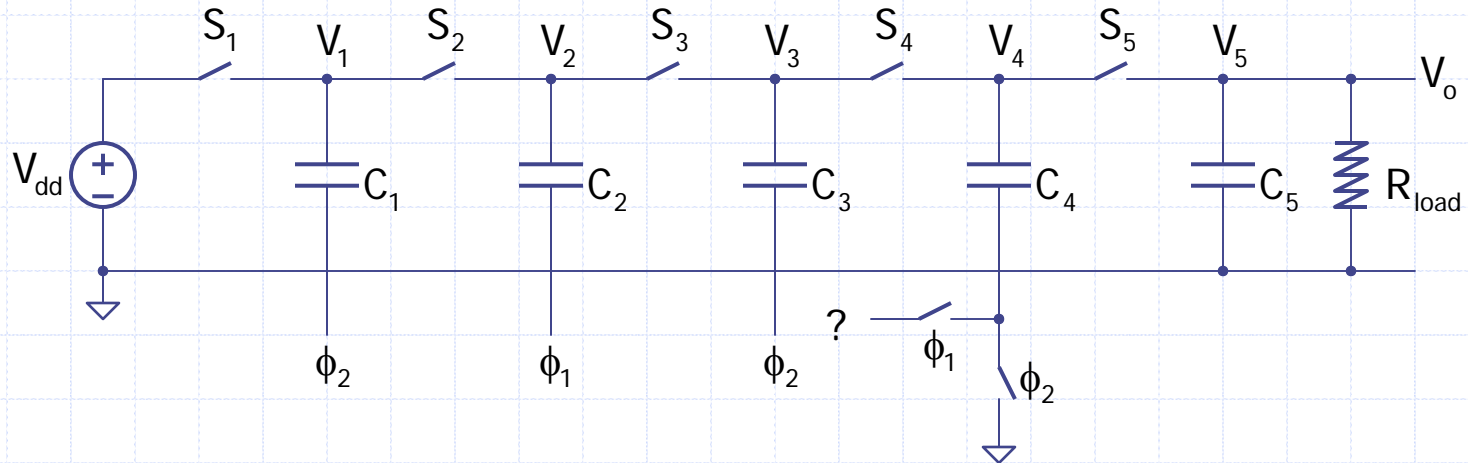

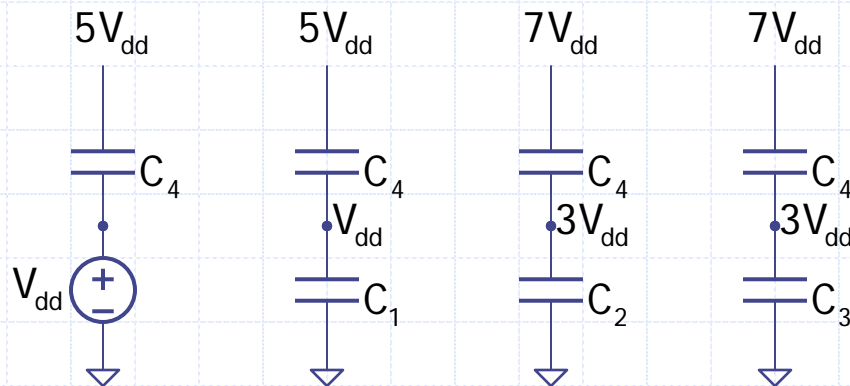After  $C_4$  is charged to  $4V_{dd}$  in  $\phi_2$ , it may be connected differently in  $\phi_1$ :



# ANTZ Tree Construction (1)

**Voltage Vector:**  $\mathbf{V}_p(C_x) = (V_p \text{ of } C_x \text{ in } \phi_1, V_p \text{ of } C_x \text{ in } \phi_2)$ , with  $V_p$  the potential of the positive terminal of  $C_x$ .

For the LQP in pp. 10,  $\mathbf{V}_p(C_3) = (3V_{dd}, 4V_{dd}) = (3, 4)$  for short.

Construct the **ANTZ tree** using voltage vectors.

**Level 0:** No capacitor but only  $V_{dd}$

$$\mathbf{V}_p(V_{dd}) = (1, 1)$$

**Level 1:** 1 capacitor  $C_1$

$$\mathbf{V}_p(C_1) = (1, 2) \text{ or } (2, 1)$$

Eliminate redundancy and the final assignment is

$$\mathbf{V}_p(C_1) = (1, 2)$$

## ANTZ Tree Construction (2)

Level 2:  $C_1$  and  $C_2$

To avoid redundancy,  $C_2$  should not assume (1, 2).

$C_2$  charged in  $\phi_1 \Rightarrow$  has to be connected in series with  $C_1$  and  $V_{dd}$  in  $\phi_2$ , and gives (1, 3).

$C_2$  charged in  $\phi_2 \Rightarrow$  (1) charged to  $V_{dd}$  by source and gives (2, 1)  
(2) charged to  $2V_{dd}$  by  $C_1$ , and gives (3, 2)

Hence, we have the following **vector paths** (starting from Level 1):

(1, 2)  $\rightarrow$  (1, 3)

(1, 2)  $\rightarrow$  (2, 1)

(1, 2)  $\rightarrow$  (3, 2)

Level 3 and Level 4 are constructed in a similarly fashion.



# 4-Capacitor ANTZ Tree

The 4-capacitor ANTZ tree has 59 configurations.

Level 0

(1,1)

Level 1

(1,2)

Level 2

(1,3)

(2,1)

(3,2)

(1,4)

(2,1)

(3,2)

(4,3)

(2,3)


(2,4)

(3,4)

(3,5)

(4,1)

(5,2)

 

# Charge Pumps from ANTZ Tree

5X Heap Charge Pump [Mihara 95]:

$$(1, 2) \rightarrow (1, 3) \rightarrow (1, 4) \rightarrow (1, 5)$$

3X Dual-Branch Charge Pump [Pellinconi 03]:

$$(1, 2) \rightarrow (2, 1) \rightarrow (2, 3) \rightarrow (3, 2)$$

2nX or 2<sup>n</sup>X (Exponential) Charge Pump (n=2) [Ying 03], [Ki 08]:

$$(1, 2) \rightarrow (2, 1) \rightarrow (2, 4) \rightarrow (4, 2)$$

5X Linear Charge Pump [Dickson 76]:

$$(1, 2) \rightarrow (3, 2) \rightarrow (3, 4) \rightarrow (5, 4)$$

8X Fibonacci Charge Pump [Ueno 91]:

$$(1, 2) \rightarrow (3, 2) \rightarrow (3, 5) \rightarrow (8, 5)$$

New 8X FQP [Su 07]:

$$(1, 2) \rightarrow (3, 2) \rightarrow (3, 5) \rightarrow (3, 8)$$


# Variable Conversion Ratio

Qn: What is the advantage of identifying all possible topologies?

Ans: The ANTZ tree helps to design charge pumps with a **variable conversion ratio**, by observing that adjacent topologies only differ by one connection.

For example, consider the vector paths:

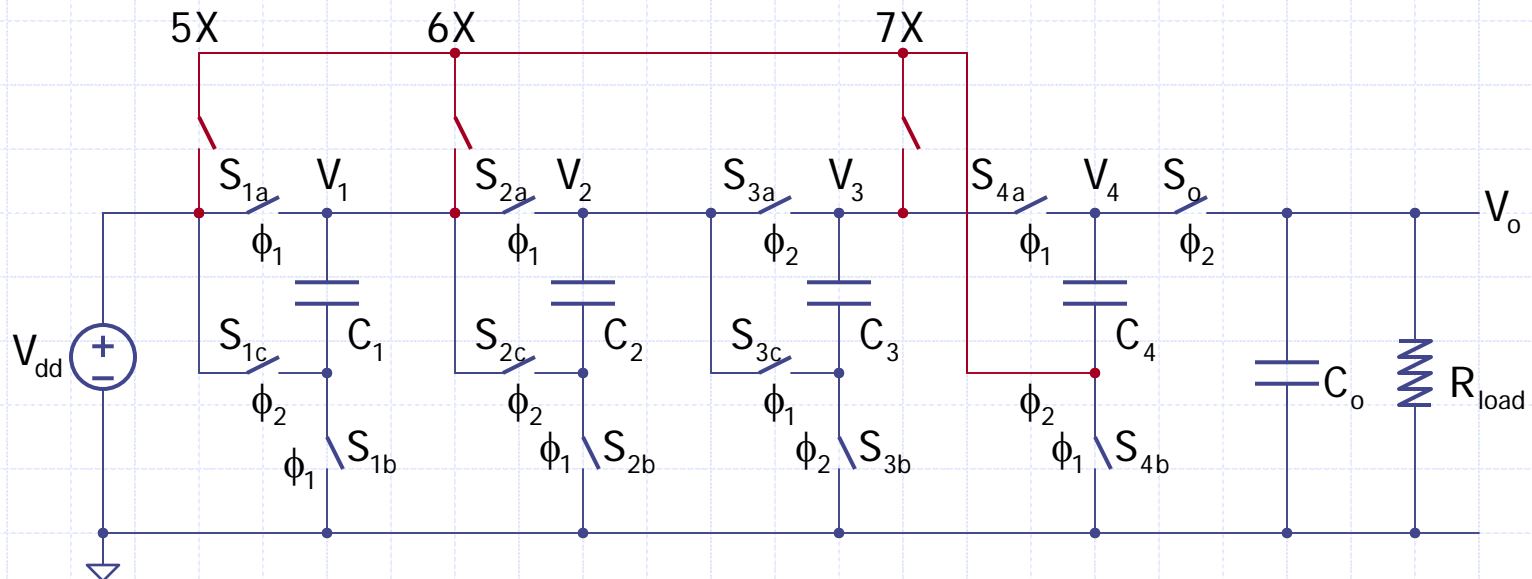$(1, 2) \rightarrow (1, 3) \rightarrow (4, 3) \rightarrow (4, 5) / (4, 6) / (4, 7)$





# Dual-Branch Charge Pumps

Using the same total capacitance, a dual-branch charge pump is more efficient than a single-branch charge pump [Ki 05]:


$$C_{ak} = C_{bk} = C_k/2$$

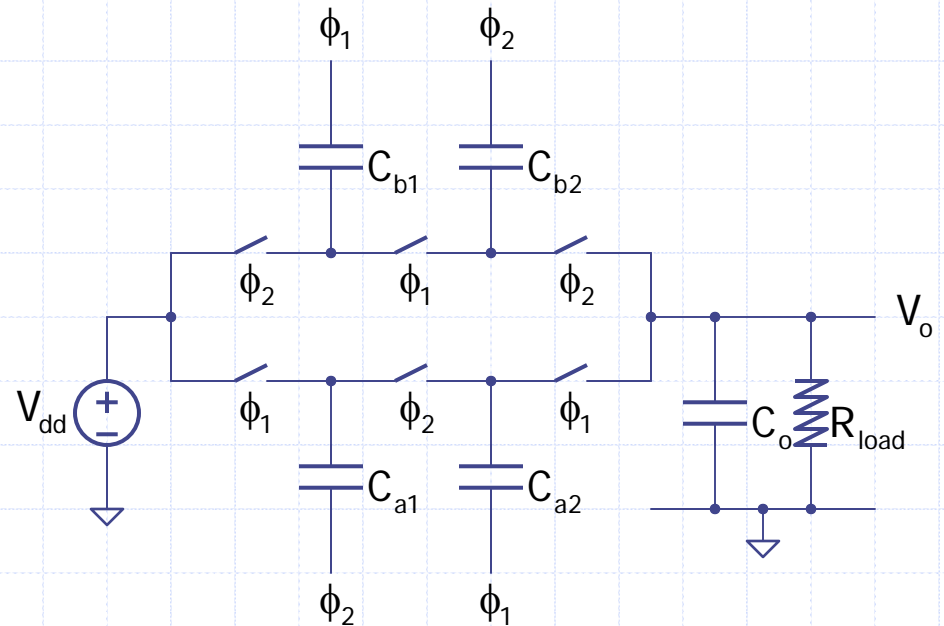 Hence, dual-branch charge pumps are more suitable for on-chip implementation.




# Cross-Coupled Voltage Doublers

Dual-branch charge pumps could make use of the opposite branch for gate drives, and typical examples are **cross-coupled voltage doublers** such as [Nakagome 91] and [Favrat 98] (they are equivalent).

 


[Nakagome 91]

 

[Favrat 98]
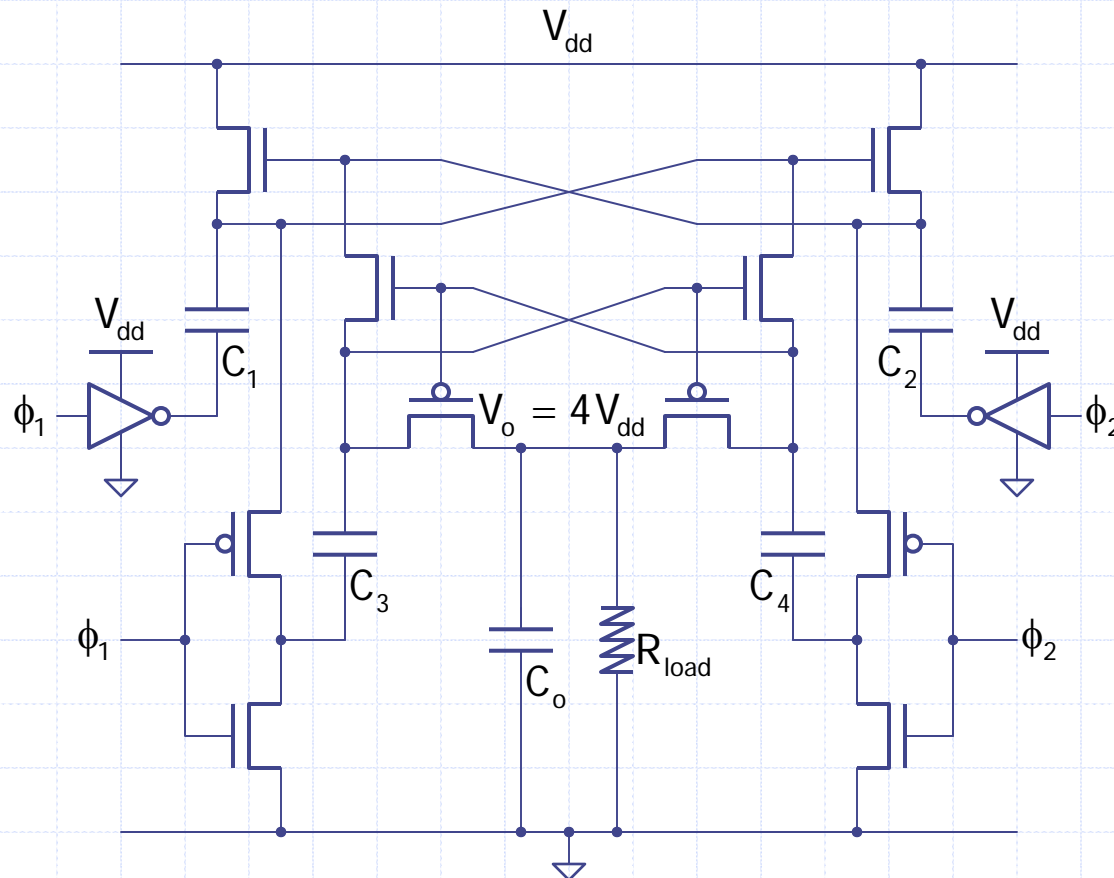
# Component-Efficient 2N-X Charge Pumps


A 4X charge pump could be constructed by cascading two 2X cross-coupled doublers, using 16 power switches. [Ying 02] suggests a 4X cross-coupled charge pump using only 14 power switches.


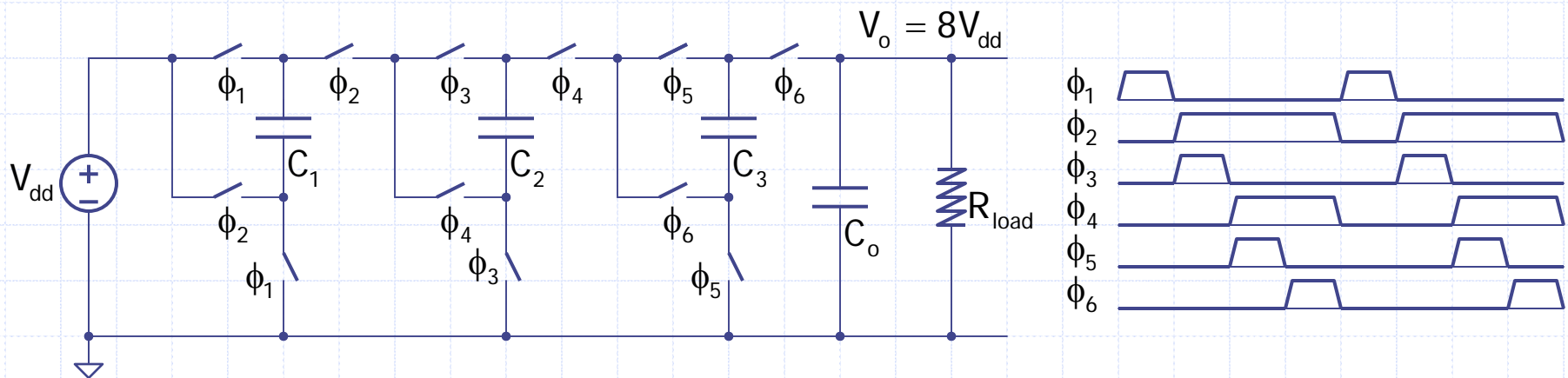
# 2N-Phase Exponential Charge Pump

Qn. Is it possible to design an exponential ( $2^N X$ ) charge pump?


Ans. Yes, [Starzyk 01] suggests a consecutive charging scheme that uses a  $2N$ -phase clock:  $C_1$  is charged in  $\phi_1$ , hold for a long  $\phi_2$ , within which  $C_2$  is charged in  $\phi_3$  and for a shorter  $\phi_4$ , but long enough for  $C_3$  to charge in  $\phi_5$  and pump in  $\phi_6$ .



# EQP with Cascade Doublers

A straightforward way is to cascade voltage doublers [Chang 04].  
However,

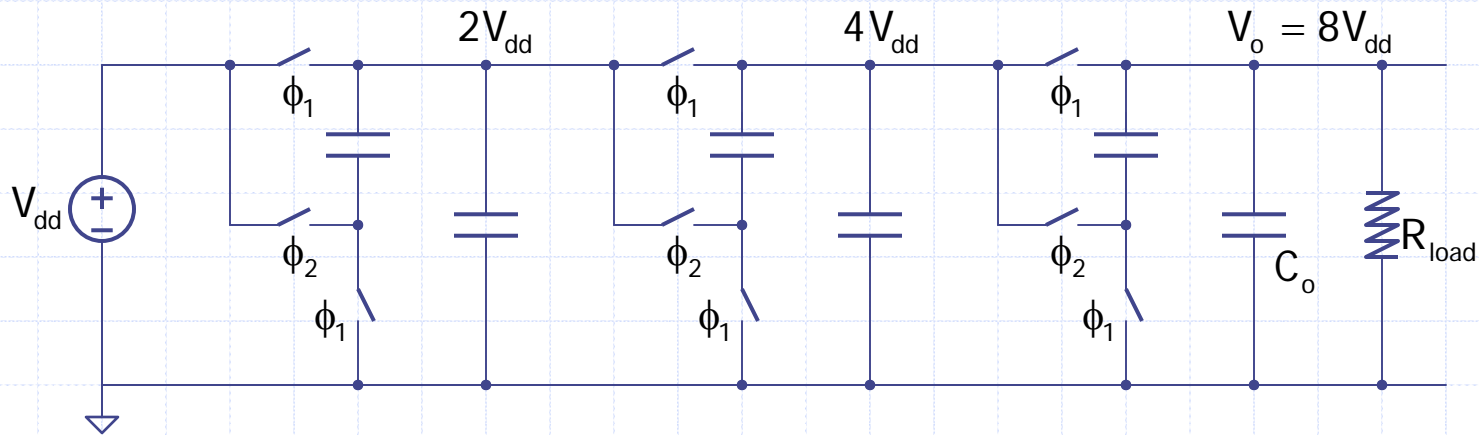
- (1) an N-stage charge pump needs  $2N$  capacitors; and
- (2) single-branch structure needs a larger total area than a dual-branch structure for the same efficiency.




 
# Cross-Coupled EQP

[Ki 08] suggests a cross-coupled dual-branch exponential charge pump:  $C_{a1}$  is charged to  $V_{dd}$  in  $\phi_1$ , pumped in  $\phi_2$ , and pushes up  $C_{a2}$  by  $2V_{dd}$  and charges  $C_{b2}$  to  $2V_{dd}$  at the same time.



# Properties of Cross-Coupled EQP

## Advantages:

- (1) Only a 2-phase clock is needed, and gate drive is simpler because dual branch operation provides node voltages to drive the other branch.
- (2) Dual branch operation charges the output in both phases, reducing the ripple, or equivalently, enhancing the efficiency as compared to single branch charge pumps.

## Disadvantages:

- (1) Need  $2N$  capacitors, and may not be good if off-chip capacitors are used.
- (2) Using cross-biased nodes for gate drives results in reversion loss.

# Multi-Phase Charge Pumps

Qn. Is it possible to design an exponential ( $2^N X$ ) charge pump using only  $N$  flying capacitors but using fewer than  $2N$  phases?

Ans. Yes, [Su 08b] suggests a systematic strategy to design multi-phase charge pumps, observing the **one voltage criteria**.


**One voltage criteria:** Each capacitor should be charged to only one voltage value that is a multiple of  $V_{dd}$  for all charging phases, and in the discharging phases, the lowering of the capacitor voltage is mainly due to the load current.

With the one voltage criteria, we demonstrate that a  $2^N X$  charge pump could be realized using  $N$  flying capacitors and only  $N+1$  phases.

# 3/4-Phase QPs with 3 Flying Capacitors

M	$\phi_1$	$\phi_2$	$\phi_3$	$\phi_4$
4 (a)				
5				
6				
7				

# Multi-Phase 7X and 8X Charge Pumps

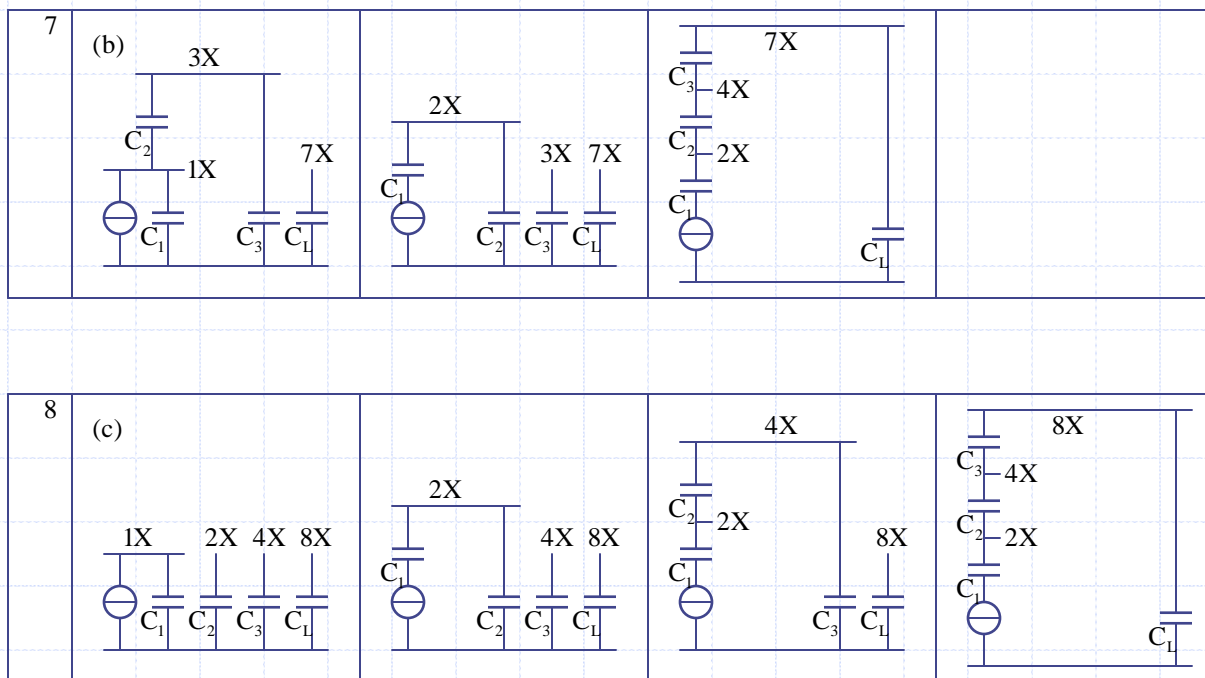


# Comparison of Exponential Charge Pumps

	Linear QP	Cascade 2X's	X-coupled EQP	Multi-phase
Caps	$2^N$	$2N$	$2N+1$	$N$
Clock	2-phase	$2N$ -phase	2-phase	$(N+1)$ -phase
Speed	very slow	fast	fast	medium
	single-branch	single-branch	dual-branch cross-coupled	single-branch
Area	large	medium	low	low
Eff.	poor	good	good	medium
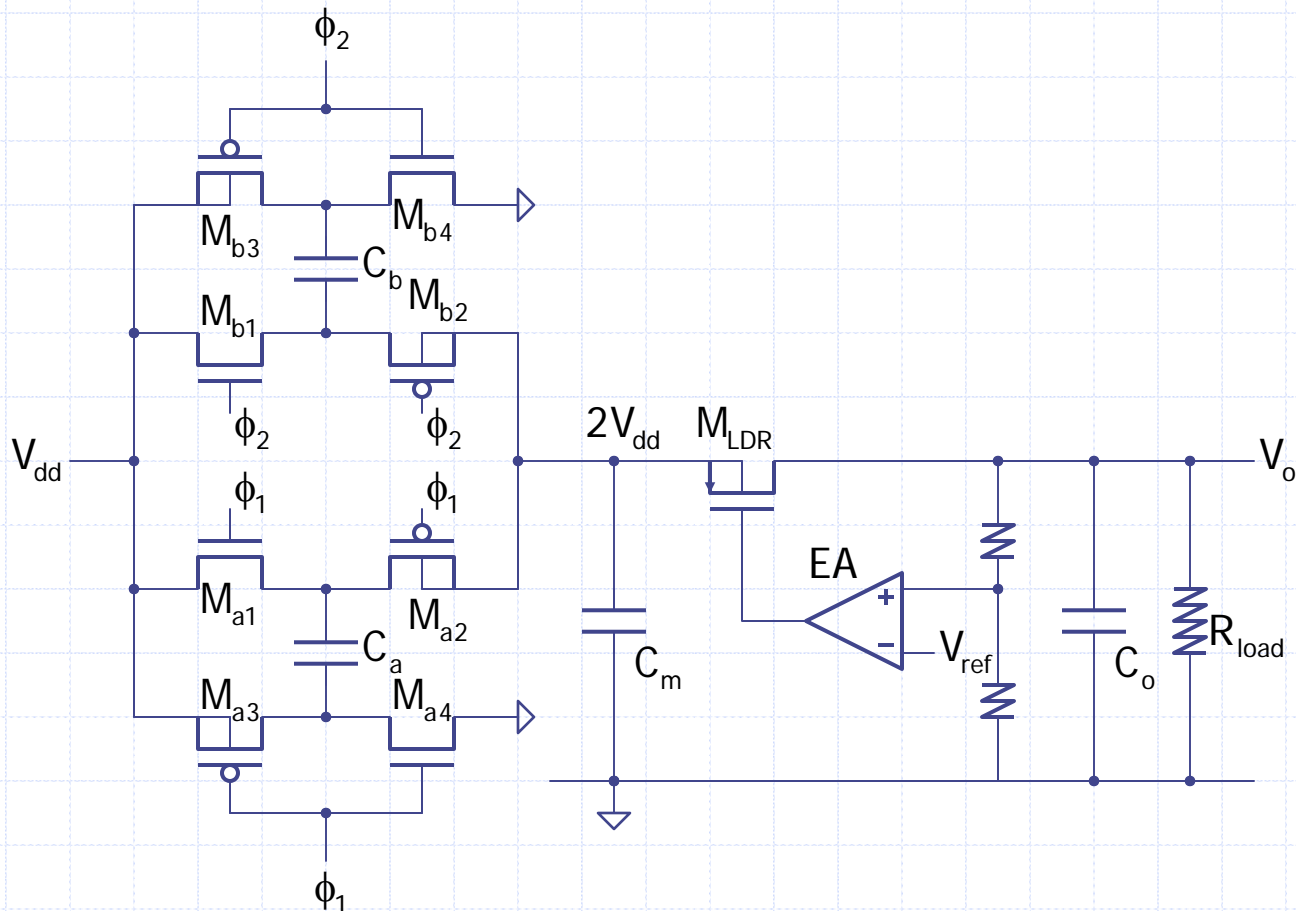
# Voltage Doubler + LDR


To achieve a regulated output voltage, a straightforward method is to cascade the charge pump with a low dropout regulator (LDR) to achieve a **regulated charge pump (RQP)**.



# RQP with Quasi Switches

In [Chung 98], the switches  $M_{a4}$  and  $M_{b4}$  are turned into controlled current sources (resistors), coined **quasi switches**, and charges  $C_a$  and  $C_b$  to  $V_1$  ([Chung 98] uses only single-branch) such that


$$V_o = V_{dd} + V_1$$

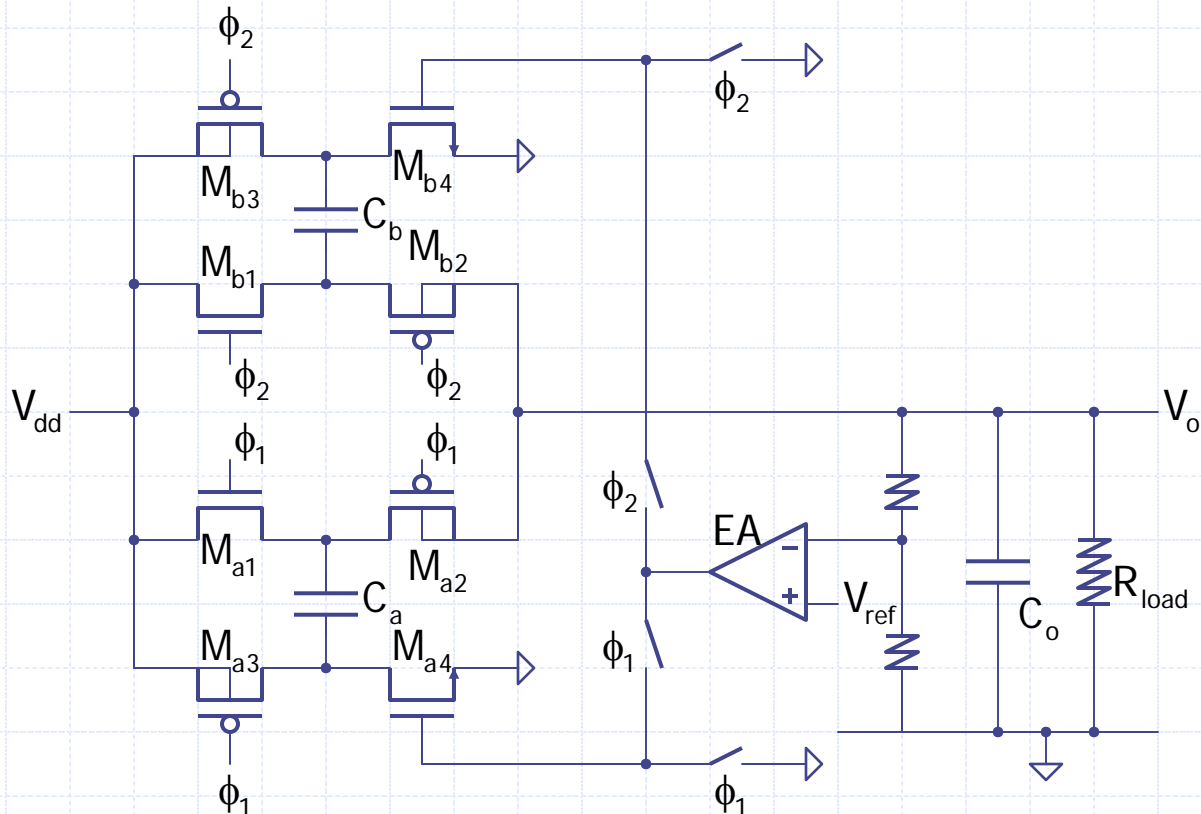



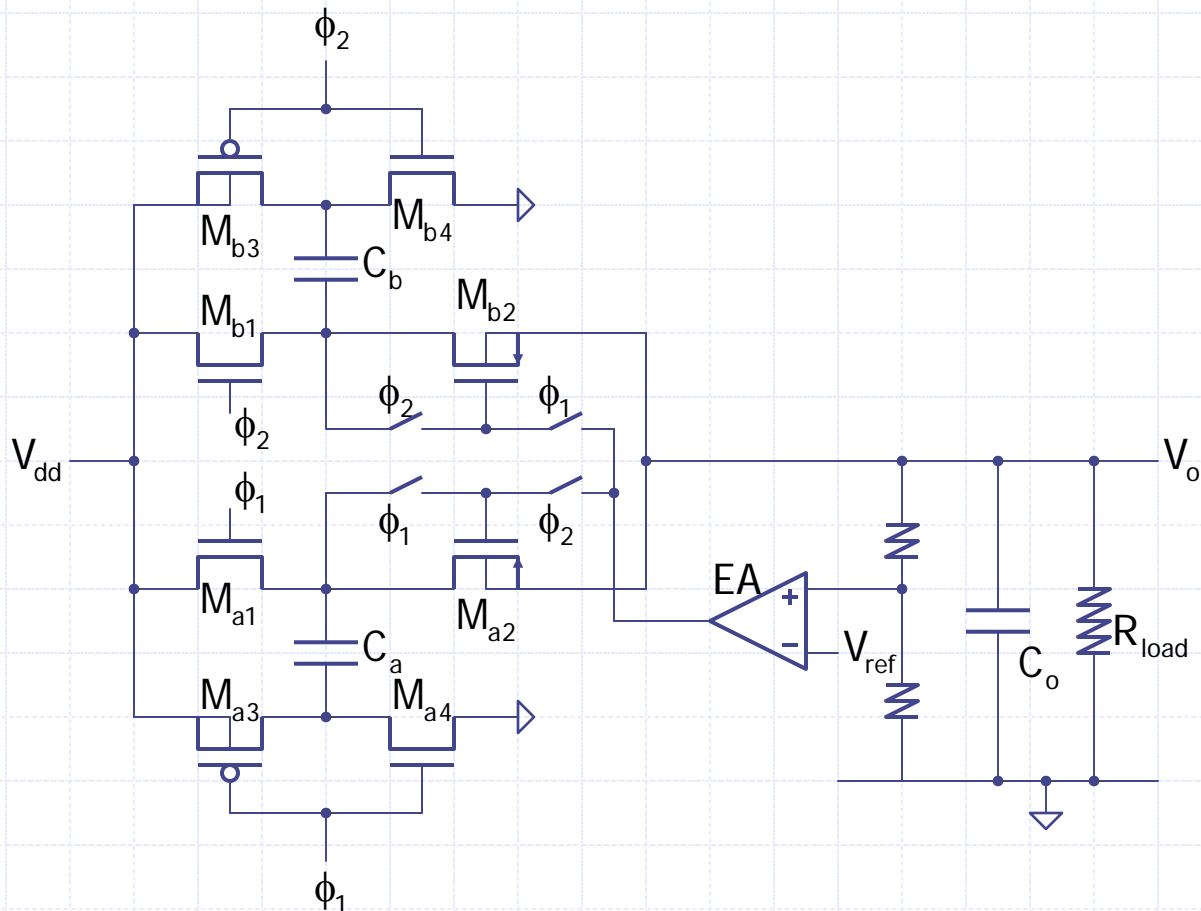
# Switching Low Dropout Regulator

The RQP with quasi-switches cannot achieve in-phase regulation, and the best is to combine  $M_{a2}$  ( $M_{b2}$ ) with  $M_{LDR}$ , and the scheme is coined **switching low dropout regulator (SLDR)** [Chen 01].




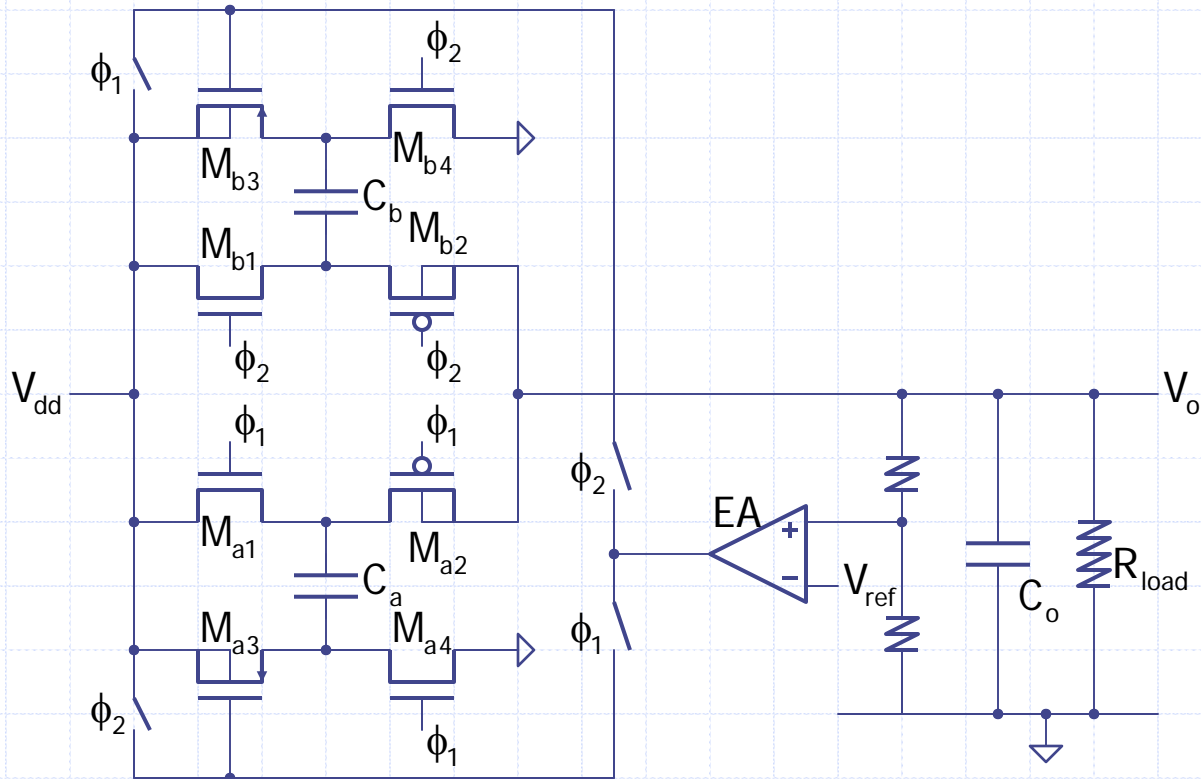An alternative way to achieve in-phase regulation is to incorporate  $M_{LDR}$  into  $M_{a3}$  ( $M_{b3}$ ), and the scheme is coined **pseudo-continuous regulation** [Lee 05].



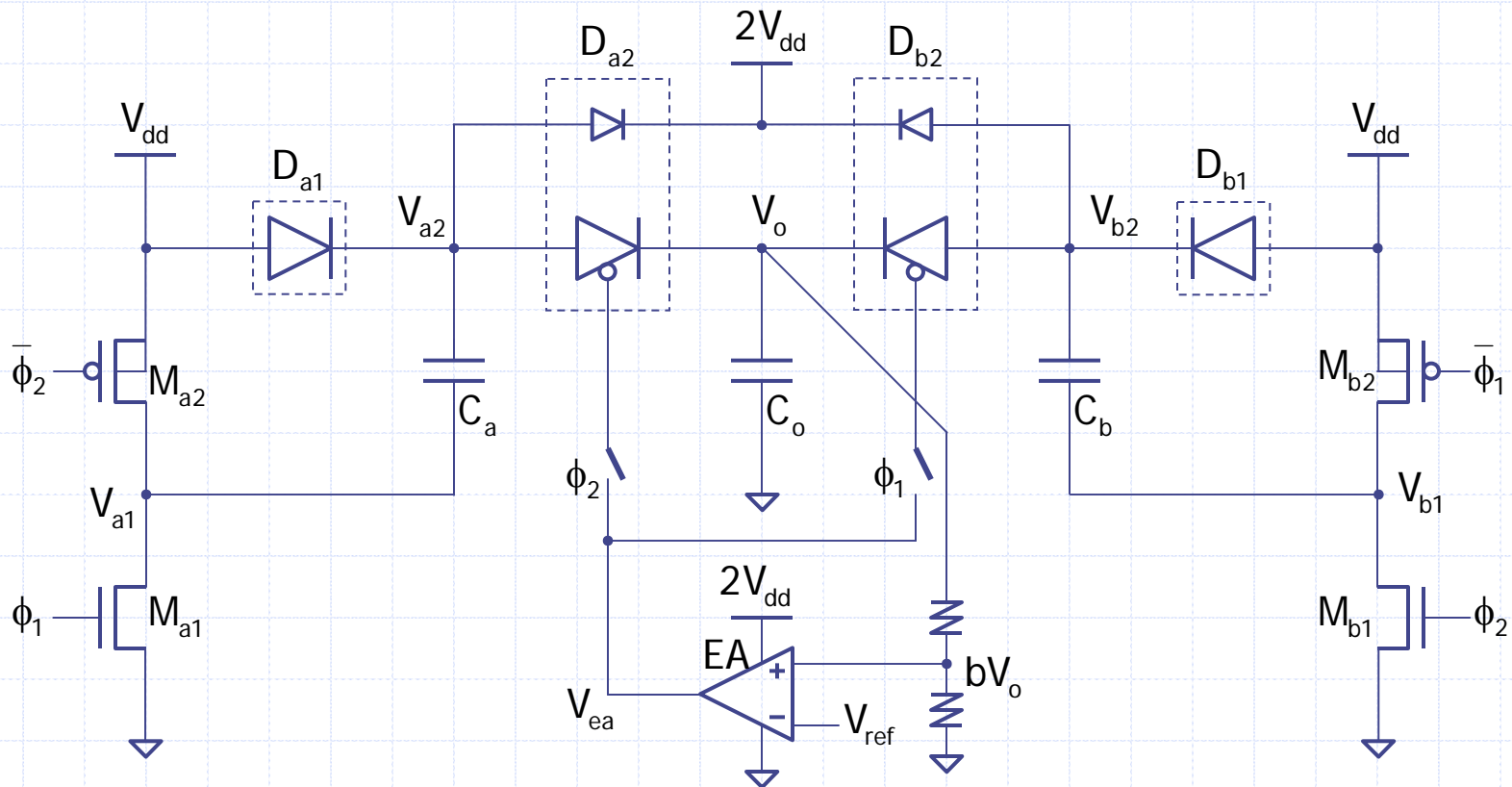
# RQP with Active Diodes

An alternative way of implementing the switching LDR is to use **active diodes**, i. e., using MOS transistors with control to replace the diodes [Lam 06a].



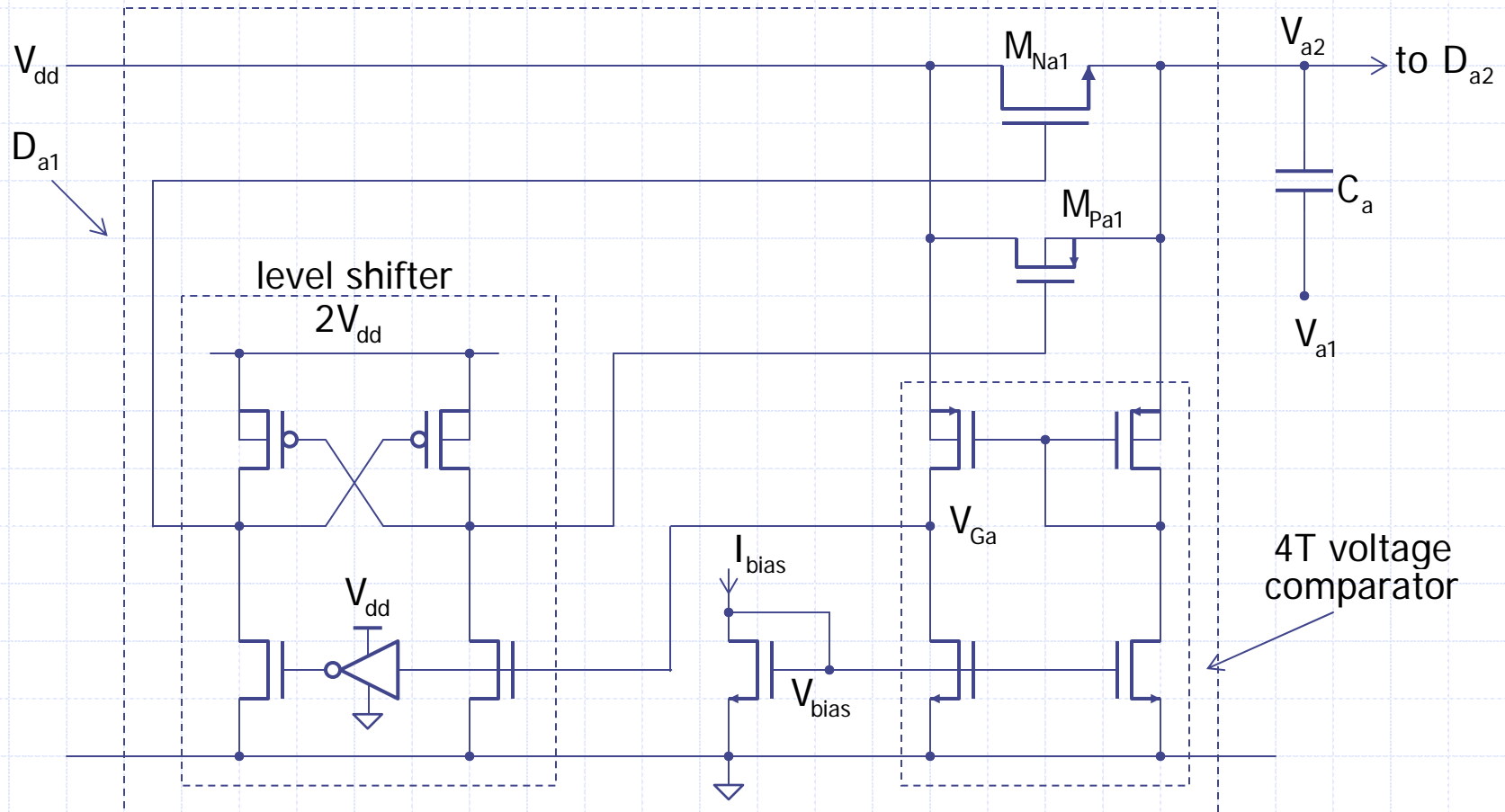
# Implementation of $D_{a1}$

An **active diode** is an MOS switch with a differential common gate comparator and level shifter [Lam 06a].


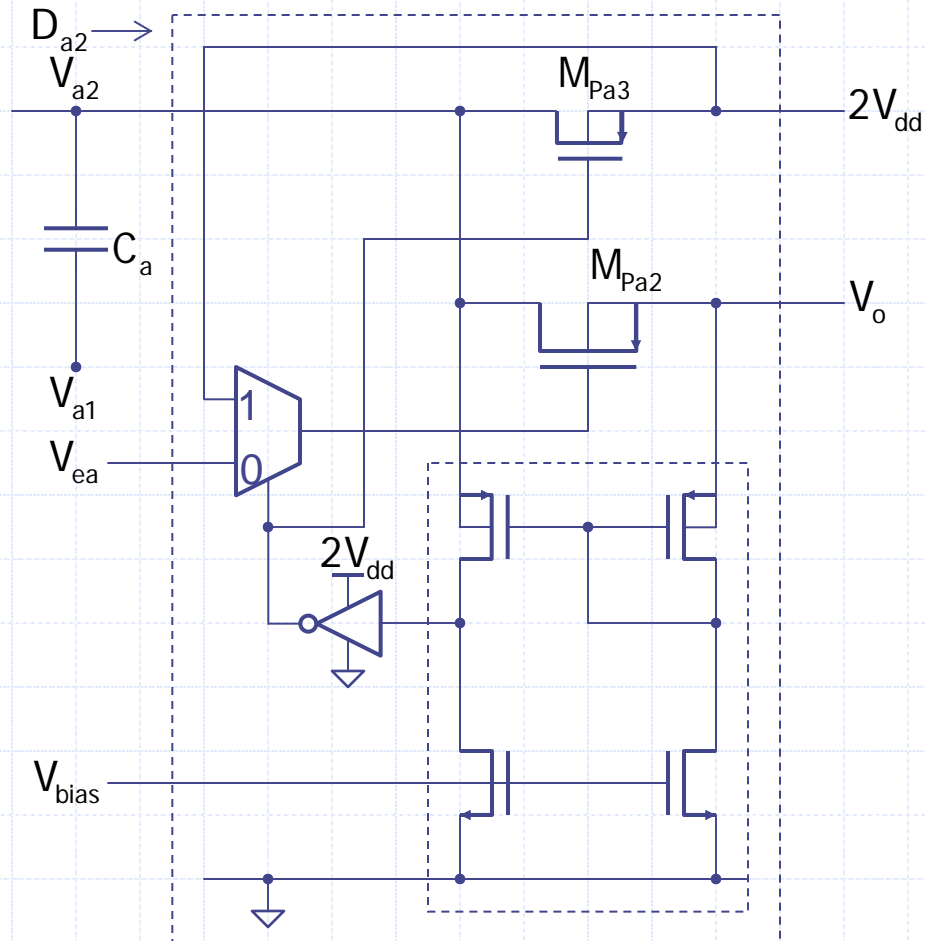
# Implementation of $D_{a2}$


Active diode  $D_{a2}$  ( $D_{b2}$ ) also serves as the **pass transistor** of the LDR.


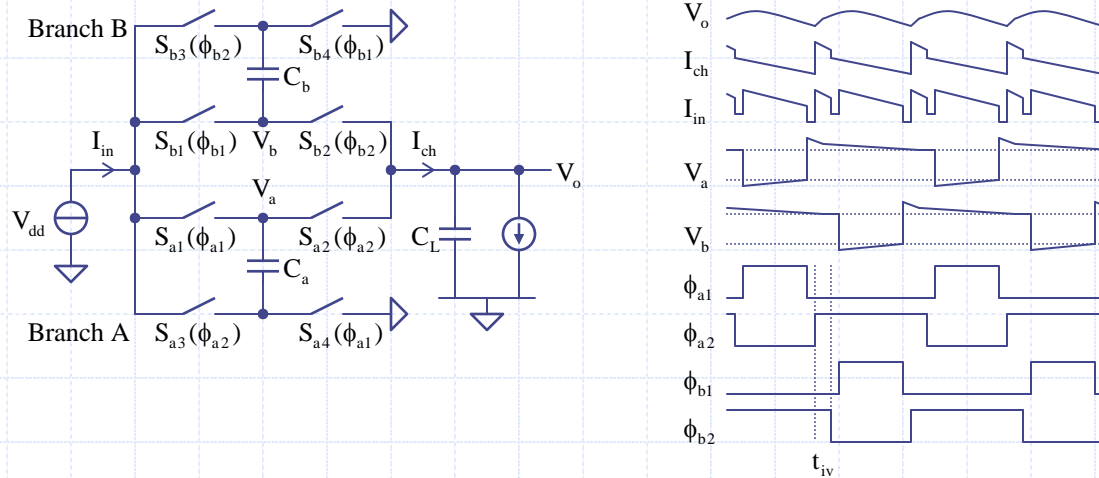
# RQP with Continuous Output Regulation (1)


To achieve (in-phase) continuous output regulation, a 4-phase clock with interleaving control is proposed [Su 09].

Voltage doubler with 4-phase interleaving clock:




# RQP with Continuous Output Regulation (2)

The interleaving scenario:

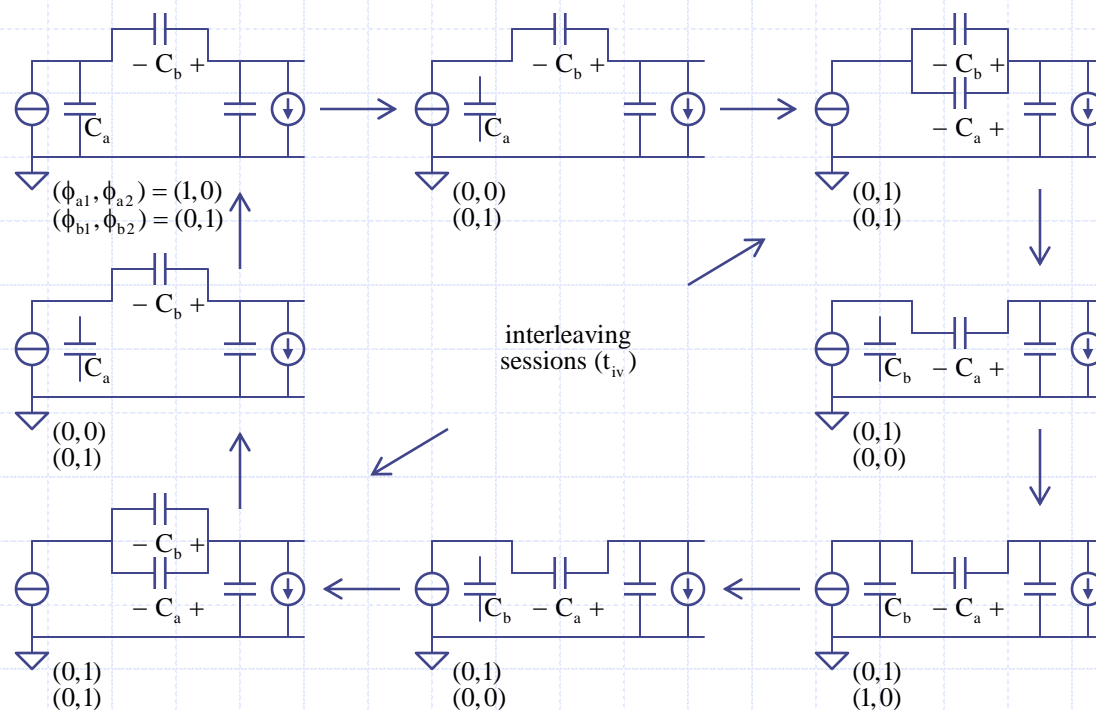

# RQP with Continuous Output Regulation (3)

The LDR architecture:

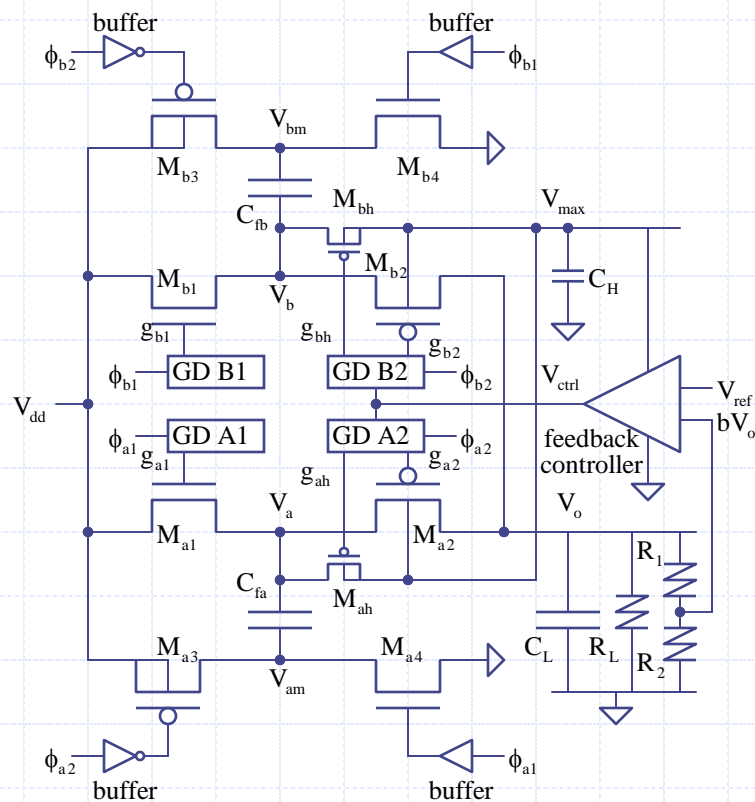



## Remarks

A systematic study of charge pumps should cover **analysis**, **topology**, **gate control** and **regulation**. This talk only covers snapshots on topology, gate control and regulation.

The talk centered on the research activities at HKUST. The attached reference section only mentions those papers (in chronological order) that are directly useful for the discussion:

[BLUE] Papers from other institutions

[RED] HKUST papers (Ki's research group)

[PINK] HKUST papers (Mok's and Tsui's research groups)

The reference section tabulates all publications since the setup of the **Integrated Power Electronics Lab**. in 1995 up to Sept. 2009, and topics such as analysis, AC-DC charge pumps, energy harvesting applications, etc., are not covered in this talk due to limited time.

# References: Analysis, Gate Control

## Analysis

- [Dickson 76] J. Dickson, "On-chip high-voltage generation in MNOS integrated circuits using an improved voltage multiplier technique," IEEE J. of Solid State Circ., pp.374-378, June 1976.
- [Makowski 97] M. S. Makowski, "Realizability conditions and bounds on synthesis of switched-capacitor dc-dc voltage multiplier circuits," IEEE Trans. on Circ. & Syst. I, pp. 684-691, Aug. 1997.
- [Ki 05] W. H. Ki, F. Su and C. Y. Tsui, "Charge redistribution loss consideration in optimal charge pump design," IEEE Int'l. Symp. on Circ. & Syst., pp.1895-1898, May 2005.

## Gate Control

- [Cheng 03] K. H. Cheng, C. Y. Chang and C. H. Wei, "A CMOS charge pump for sub-2.0V operation," IEEE Int'l Symp. on Circ. & Syst., pp.V-89 – V-92, 2003.
- [Lee 05] H. Lee and P. Mok, "Switching noise and shoot-through current reduction techniques for switched-capacitor voltage doubler," IEEE J. of Solid-State Circ., pp.1136–1146, May 2005.
- [Su 05] F. Su, W. H. Ki and C.Y. Tsui, "Gate control strategies for high efficiency charge pumps", IEEE Int'l. Symp. on Circ. & Syst., pp.1907-1910, May 2005.
- [Su 06] F. Su, W. H. Ki and C. Y. Tsui, "High efficiency cross-coupled doubler with no reversion loss," IEEE Int'l. Symp. on Ckts. & Sys., pp.2761-2764, May 2006.

# References: Topology (1)

- [Dickson 76] J. Dickson, "On-chip high-voltage generation in MNOS integrated circuits using an improved voltage multiplier technique," IEEE J. of Solid State Circ., pp.374-378, June 1976.
- [Nakagome 91] Y. Nakagome et al., "An experimental 1.5-V 64-Mb DRAM," IEEE J. of Solid-States Circ., pp. 465-472, March 1991.
- [Ueno 91] F. Ueno et. al., "Emergency power supply for small computer systems," IEEE Int. Symp. Circ. & Syst., 1991, pp. 1065–1068.
- [Mihara 95] M. Mihara, Y. Terada and M. Yamada, "Negative heap pump for low voltage operation flash memory," IEEE VLSI Symp. on Circ., 1995, pp. 75–76.
- [Favrat 98] P. Favrat, P. Deval and M. J. Declercq, "A high efficiency CMOS voltage doubler," IEEE J. of Solid-States Circ., March 1998, pp.410-416.
- [Starzyk 01] J. A. Starzyk, Y. W. Jan and F. Qiu, "A DC-DC charge pump design based on voltage doublers," IEEE Trans. on Circ. & Syst., pp.350-359, March 2001.
- [Ying 02] T. R. Ying, W. H. Ki and M. Chan, "Area-efficient CMOS integrated charge pumps," IEEE Int'l. Symp. on Circ. & Syst., Scottsdale, USA, pp.III.831-III.834, May, 2002.
- [Cheng 03] K. H. Cheng, C. Y. Chang and C. H. Wei, "A CMOS charge pump for sub-2.0V operation," IEEE Int'l Symp. on Circ. & Syst., pp.V-89 – V-92, 2003.

## References: Topology (2)

- [Pelliconi 03] R. Pelliconi et. al., "Power efficient charge pump in deep submicron standard CMOS technology," IEEE J. Solid-State Circ., pp. 1068–1071, Jun. 2003.
- [Ying 03] T. R. Ying, W. H. Ki and M. Chan, "Area-efficient CMOS charge pumps for LCD drivers," IEEE J. of Solid-State Circ., pp.1721-1725, Oct. 2003.
- [Chang 04] L. K. Chang and C. H. Hu, "An exponential-folds design of a charge pump styled DC/DC converter," IEEE Power Elec. Specialists Conf., pp.516-520, June 2004.
- [Ki 05] W. H. Ki, F. Su and C. Y. Tsui, "Charge redistribution loss consideration in optimal charge pump design," IEEE Int'l. Symp. on Circ. & Syst., pp.1895-1898, May 2005.
- [Su 07] F. Su and W. H. Ki, "Design strategy for step-up charge pumps with variable integer conversion ratios," IEEE Trans. on Circ. & Syst. II, pp.417-421, May 2007.
- [Ki 08] W. H. Ki, F. Su, Y. H. Lam and C. Y. Tsui, "N-stage exponential charge pumps, charging stages therefor and methods of operation therefor," US Patent 7,397,299, July 8, 2008.
- [Su 08c] F. Su and W. H. Ki, "An integrated reconfigurable SC power converter with hybrid gate control scheme for mobile display driver applications," IEEE Asian Solid-State Circ. Conf., pp.169-172, Nov. 2008.

# References: Regulated Charge Pumps

- [Chung 98] H. Chung, "Design and analysis of quasi-switched-capacitor step-up DC/DC converter," *IEEE Int'l. Symp. on Circ. & Syst.*, pp.IV-438 – IV-441, 1998.
- [Chen 01] W. Chen, W. H. Ki, P. Mok and M. Chan, "Switched-capacitor power converters with integrated low dropout regulators," *IEEE Int'l. Symp. on Circ. & Syst.*, pp.III-293 - III-296, May 2001.
- [Chan 02] C. S. Chan, W. H. Ki and C. Y. Tsui, "Bi-directional integrated charge pumps," *IEEE Int'l. Symp. on Circ. & Syst.*, pp.III.827-III.830, May, 2002.
- [Lee 05] H. Lee and P. Mok, "A SC DC-DC converter with pseudo-continuous output regulation using a three-stage switchable opamp," *IEEE Int'l Solid-State Circ. Conf.*, pp.288-289+599, Feb. 2005.
- [Lam 06a] Y. H. Lam, W. H. Ki and C. Y. Tsui, "An integrated 1.8V to 3.3V regulated voltage doubler using active diodes and dual-loop voltage follower for switch-capacitive load," *IEEE VLSI Symp. on Tech. & Circ.*, pp.104-105, June 2006.
- [Lee 07] H. Lee and P. Mok, "An SC voltage doubler with pseudo-continuous output regulation using a three-stage switchable opamp," *IEEE J. of Solid-State Circ.*, pp. 1216-1229, June 2007.
- [Su 08a] F. Su, W. H. Ki and C. Y. Tsui, "An SC voltage regulator with novel area-efficient continuous output regulation by a dual-branch interleaving control scheme," *IEEE VLSI Symp. on Tech. & Circ.*, pp.136-137, June, 2008.
- [Su 09] F. Su and W. H. Ki, "Regulated switched-capacitor doubler with interleaving control for continuous output regulation," *IEEE J. of Solid-State Circ.*, pp. 1112-1120, Apr. 2009.

# References: M-Phase, AC-DC, Energy Harvesting QPs

## Multi-Phase Charge Pumps

- [Su 08b] F. Su and W. H. Ki, "Component-efficient multi-phase switched capacitor DC-DC converter with configurable conversion ratios for LCD driver applications," IEEE Trans. on Circ. & Syst. II, pp.753-757, Aug. 2008.

## AC-DC Charge Pumps

- [Lam 06b] Y. H. Lam, W. H. Ki and C. Y. Tsui, "Integrated low-loss CMOS active rectifier for wirelessly powered devices," IEEE Trans. on Circ. & Syst. II, pp.1378-1382, Dec. 2006.
- [Yi 07] J. Yi, W. H. Ki and C. Y. Tsui, "Analysis and design strategy of UHF micro-power CMOS rectifiers for micro-sensor and RFID applications," IEEE Trans. on Circ. & Syst. I, pp.153-166, Jan. 2007.

## Energy Harvesting Charge Pumps

- [Tsui 05] C. Y. Tsui, H. Shao, W. H. Ki and F. Su, "Ultra-low voltage power management and computation methodology for energy harvesting applications," IEEE VLSI Symp. on Tech. & Circ., pp.316-319, June 2005.
- [Tsui 06] C. Y. Tsui, H. Shao, W. H. Ki and F. Su, "Ultra-low voltage power management and computation methodology for energy harvesting applications," Asia South Pacific Design Automation Conf., LSI University Design Contest, pp.96-97, Jan. 2006.



# References: Charge Pumps for Energy Harvesting

- [Shao 06] H. Shao, C. Y. Tsui and W. H. Ki, "A novel charge based computation system and control strategy for energy harvesting applications," IEEE Int'l. Symp. on Circ. & Syst., pp.2933-2936, May 2006.
- [Shao 07a] H. Shao, C. Y. Tsui and W. H. Ki, "An inductor-less micro solar power management system design for energy harvesting applications," IEEE Int'l. Symp. on Circ. & Syst., pp.1353-1356, May 2007.
- [Shao 07b] H. Shao, C. Y. Tsui and W. H. Ki, "A micro power management system and maximum output power control for solar energy harvesting applications", IEEE Int'l Symp. on Low Power Elec. Devices, pp.298-303, Aug. 2007.
- [Yi 08] J. Yi, F. Su, Y. H. Lam, W. H. Ki and C. Y. Tsui, "An energy-adaptive MPPT power management unit for micro-power vibration energy harvesting," IEEE Int'l. Symp. on Circ. & Syst., May 2008, pp.2570-2573.
- [Shao 09a] H. Shao, C. Y. Tsui and W. H. Ki, "An inductor-less MPPT design for light energy harvesting systems," Asia South Pacific Design Automation Conf., LSI University Design Contest, pp.101-102, Jan. 2009.
- [Shao 09b] H. Shao, C. Y. Tsui and W. H. Ki, "The design of a micro power management system for applications using photovoltaic cells with the maximum output power control," IEEE Trans. on VLSI Syst., pp.1138-1142, Aug. 2009.

**BLANK**



# **IC Design of Power Management Circuits (VI)**

**Wing-Hung Ki**

**Integrated Power Electronics Laboratory**

**ECE Dept., HKUST**

**Clear Water Bay, Hong Kong**

**[www.ee.ust.hk/~eeki](http://www.ee.ust.hk/~eeki)**

**International Symposium on Integrated Circuits  
Singapore, Dec. 14, 2009**



## **Part VI**

# **Introduction to Low Dropout Regulators**

# Content




Generic Linear Regulator

Low Dropout Regulator

Simple Low Dropout Regulator
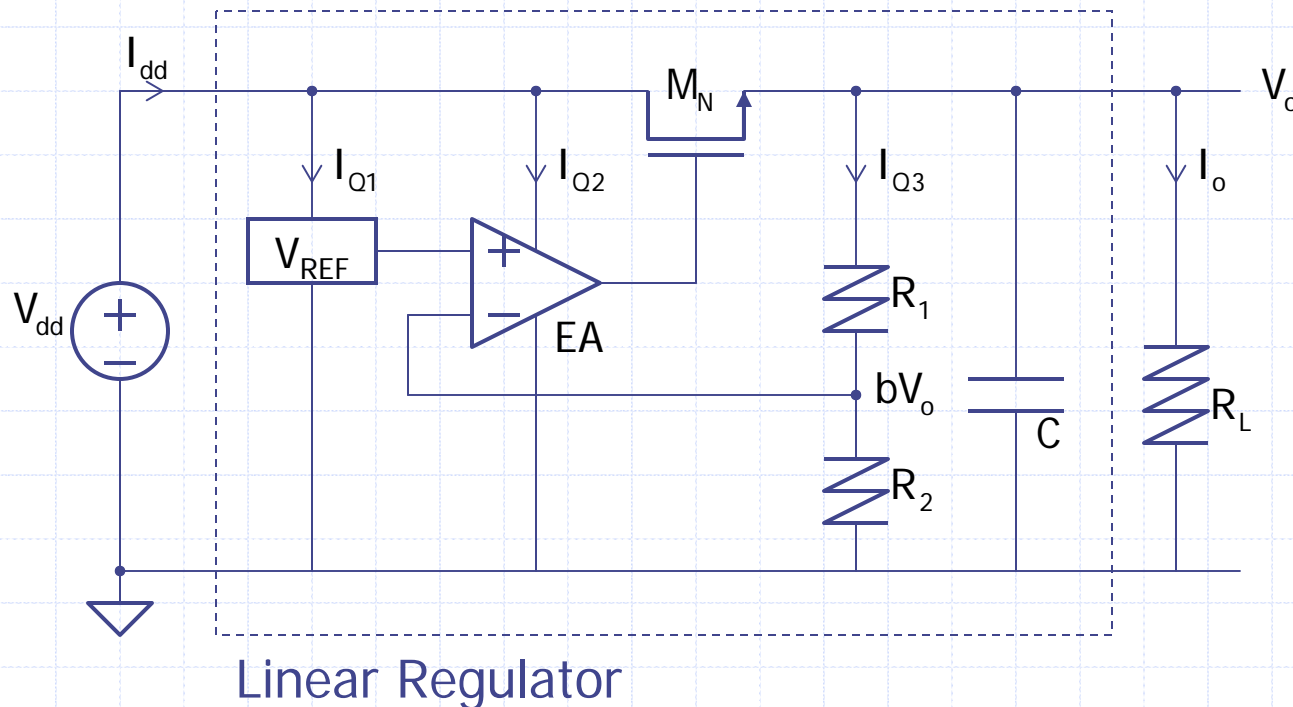
# Generic Linear Regulator

A **linear regulator** consists of a **pass transistor** inserted between the input supply voltage  $V_{dd}$  and the required output voltage  $V_o$ , and a **feedback circuit** for controlling the voltage drop across the pass transistor such that  $V_o$  is kept constant. In CMOS design, the pass transistor could be an NMOS or a PMOS transistor.



# Dropout Voltage of Linear Regulator

One important parameter of a linear regulator is the **dropout voltage** ( $V_{DO}$ ) that is defined as the minimum voltage difference between  $V_{dd}$  and  $V_o$  such that the regulator still performs satisfactorily as a linear regulator:

$$V_{DO} = \min[V_{dd} - V_o]$$

As  $V_o$  is usually fixed, we have

$$V_{DO} = V_{ddmin} - V_o$$

For the linear regulator in the previous page, the high output swing of the error amplifier EA is  $V_{dd} - V_{ov}$ , and  $V_{gsN} = V_{tn} + V_{ov}$  ( $V_{ov}$  is the gate overdrive voltage of all transistors), and  $V_{ddmin}$  is computed as

$$\begin{aligned} V_{ddmin} &= V_o + V_{gsN} + V_{ov} \\ &= V_o + V_{tn} + 2V_{ov} \end{aligned}$$

# Efficiency of Linear Regulator

Another important parameter is the **efficiency** that is obtained as

$$\eta = \frac{P_o}{P_{in}} = \frac{V_o I_o}{V_{dd} I_{dd}} = \frac{V_o}{V_{dd}} \frac{I_o}{I_o + I_Q} \approx \frac{V_o}{V_{dd}}$$

and

$$\eta_{max} \approx \frac{V_o}{V_{ddmin}} = \frac{V_o}{V_o + V_{tn} + 2V_{ov}}$$


For example, if  $V_o=1.8V$ ,  $V_{tn}=0.8V$ ,  $V_{ov}=0.2V$ , then the maximum efficiency is only 60%.

It is desirable to have a low  $V_{DO}$  such that the efficiency is still satisfactory even when the battery is drained very low.
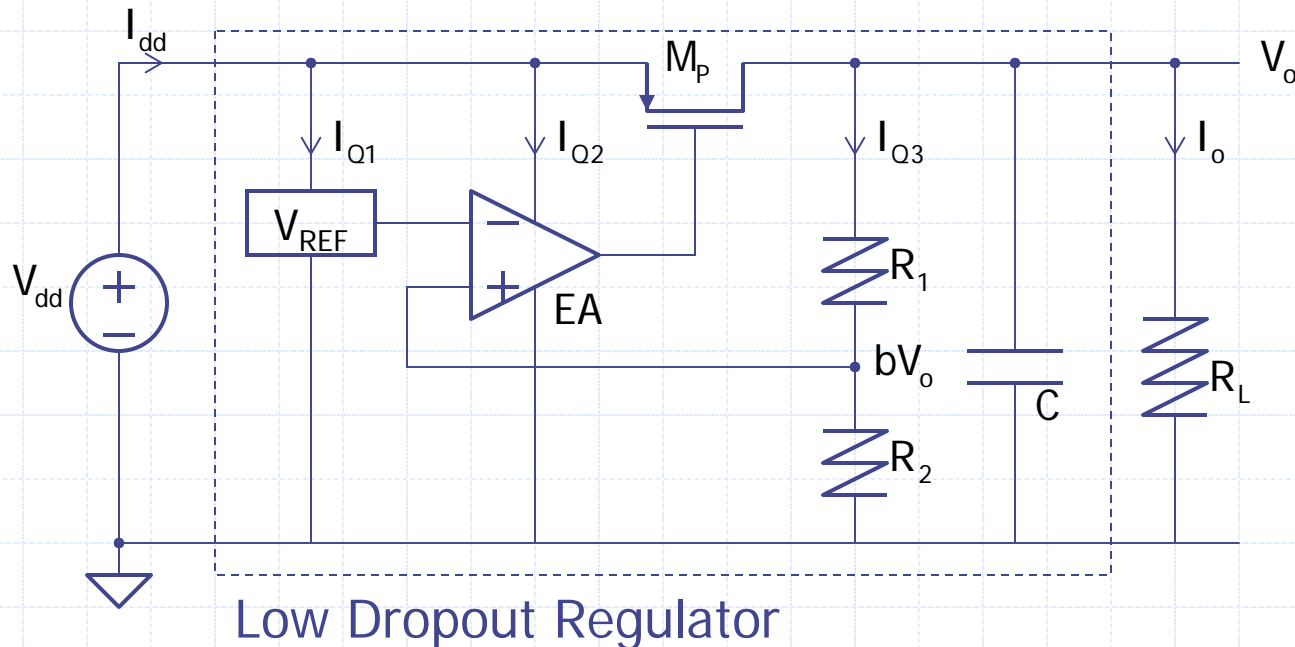
# Low Dropout Regulator


Low dropout regulators (LDRs) could be achieved by using a higher supply voltage for EA through using an **on-chip charge pump**. Yet, a popular method is to use a **PMOS pass transistor**, ( $V_+$  and  $V_-$  have to be swapped), and  $V_{ddmin} = V_o + V_{ov}$ , giving

$$\eta_{max} \approx \frac{V_o}{V_{ddmin}} = \frac{V_o}{V_o + V_{ov}} \quad (\eta_{max} = 90\% \text{ with the previous parameters})$$



# Simple Low Dropout Regulator

A simple LDR could be obtained by using a differential pair to drive the PMOS pass transistor. For  $V_{tn}=0.55V$ ,  $|V_{tp}|=0.7V$ , and  $V_{ov}=0.2V$ , it is feasible to use  $V_{ref}=1.25V$  to bias  $M_0$  to  $M_2$ . Also, let  $V_o=2.5V$  and  $V_{DO}=0.2V$ , then  $V_{ddmin}=2.7V$ . Clearly, the voltage swing of  $V_a$  (with  $V_{ref}=1.25V$ ) is from  $0.7V$  to  $2.5V$ .

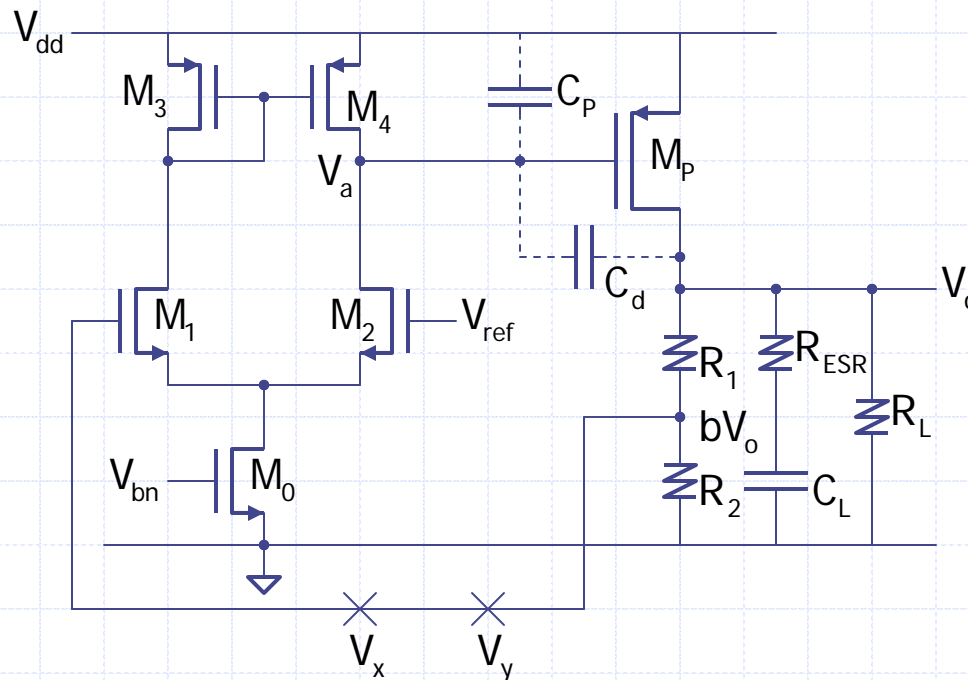




# Complications in LDR Analysis

Although the simple LDR resembles a 2-stage amplifier of which the analysis is well-known, there are complications.

1. In many analyses, only the gate capacitance of the pass transistor  $C_{gp}$  ( $=C_p$ ) is considered; but in fact the gate-drain overlap capacitance  $C_{gdoP}$  ( $=C_d$ ) is quite large and should not be omitted.
2. The output current could change by 5 orders of magnitudes (say, from  $10\mu\text{A}$  to  $100\text{mA}$ ), and the pass transistor will transit from the sub-threshold region to the active region.
3. For aggressive design in using a smaller pass transistor, it will operate in the triode region at high currents.
4. Both  $C_p$  and  $C_d$  depends on the load current.
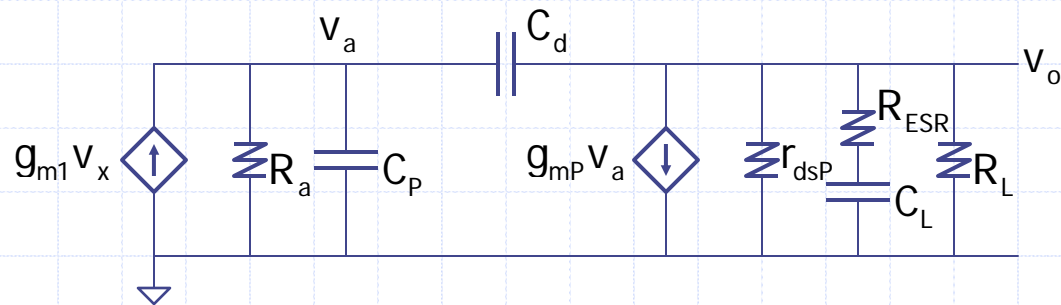
# Simple LDR: Small Signal Model

$C_p$  and  $C_d$  are parasitic capacitors and are shown by dotted lines in pg. 8. By absorbing  $R_1 + R_2$  into  $R_L$ , the small signal model is



$$T(s) = \frac{-v_y}{v_x} = \frac{-bv_o}{v_x} = \frac{T_o (1 + sC_L R_{ESR})(1 - sC_d/g_{mP})}{(1 + as + bs^2)}$$

with  $T_o = bg_{ma}g_{mP}R_aR_o$        $R_a = r_{ds2} || r_{ds4}$        $R_o = R_L || r_{dsP}$

$$a = [C_p + (1 + g_{mP}R_o)C_d]R_a + (C_d + C_L)R_o$$

$$b = (C_pC_d + C_pC_L + C_dC_L)R_aR_o$$

# Simple LDR: Loop Gain Function

Note that  $C_L \gg C_p, C_d$ , we have

$$a \approx C_L R_o = C_L (R_L || r_{dsP})$$

$$b \approx (C_p + C_d) C_L R_a R_o$$

and  $g_{mp}/C_d \gg z_{ESR}$ , then the loop gain function is given by

with

$$T(s) = \frac{T_o (1 + s/z_{ESR})}{(1 + s/p_o)(1 + s/p_a)}$$

$$T_o = b g_{ma} g_{mp} (r_{ds2} || r_{ds4}) (R_L || r_{dsP})$$

$$z_{ESR} = \frac{1}{C_L R_{ESR}}$$

$$p_o = \frac{1}{C_L (R_L || r_{dsP})}$$

$$p_a = \frac{1}{(C_p + C_d) (r_{ds2} || r_{ds4})}$$

# Simple LDR: Numerical Example

The simple LDR is designed using a  $0.35\mu\text{m}$  CMOS process:

$$\mu_n C_{ox} = 110\mu\text{A}/\text{V}^2, \mu_p C_{ox} = 35\mu\text{A}/\text{V}^2, V_{tn} = 0.55\text{V}, |V_{tp}| = 0.7\text{V}, \\ \lambda_n = 0.1/\text{V}@L=0.5\mu\text{m}, |\lambda_p| = 0.1/\text{V}@L=1\mu\text{m}$$

$$V_{dd} = 2.7\text{V}, V_o = 2.5\text{V}, V_{ref} = 1.25\text{V}, b = 0.5, C_L = 10\mu\text{F}, \\ I_{1,2} = 50\mu\text{A}, I_{o\text{max}} = 100\text{mA}$$

At  $I_o = I_{o\text{max}}$ ,  $M_p$  is at the edge of active region, and

$$\left(\frac{W}{L}\right)_p = \frac{2 \times 100\text{m}}{35\mu \times 0.2^2} = \frac{50,000\mu\text{m}}{0.35\mu\text{m}}$$

The gate capacitance  $C_p$  and gate-drain overlap capacitance  $C_{gdoP}$  ( $=C_d$ ) depends on the load current  $I_o$ :

$I_o$	$C_p$	$C_d$
0.1mA	9.5pF	10pF
1mA	12.5pF	10pF
10mA	50pF	13pF
100mA	50pF	13pF

## Simple LDR: Diff Pair Parameters

Consider the pass transistor to operate at  $I_{o\max}=100\text{mA}$  first.  
To achieve  $\lambda_n=|\lambda_p|=0.1/\text{V}$ ,  $L_n=0.5\mu\text{m}$ , and  $L_p=1\mu\text{m}$ , and

$$\left(\frac{W}{L}\right)_{1,2} = \frac{2 \times 50\mu}{110\mu \times 0.2^2} \approx \frac{12\mu\text{m}}{0.5\mu\text{m}}$$

$$\left(\frac{W}{L}\right)_{3,4} = 3 \left(\frac{W}{L}\right)_{1,2} \approx \frac{67.5\mu\text{m}}{1\mu\text{m}}$$

$$g_{m1,2} = \frac{2 \times 50\mu}{0.2} = 500\mu \text{ A/V}$$

$$r_{ds2,4} = \frac{1}{0.1 \times 50\mu} = 200\text{k}\Omega$$

$$A_1 = 500\mu \times 100\text{k} = 50 \text{ V/V} \quad (34\text{dB})$$

$$p_a = \frac{1}{63\text{p} \times 100\text{k}} = 160\text{k rad/s}$$

# Simple LDR: Output Stage Parameters

Consider  $I_{\text{omax}}=100\text{mA}$  and  $R_{\text{ESR}}=100\text{m}\Omega$ :

$$g_{\text{mP}} = \frac{2 \times 100\text{m}}{200\text{m}} = 1\text{A} / \text{V}$$

$$r_{\text{dsP}} = \frac{1}{0.25 \times 100\text{m}} = 40\Omega$$

(L of  $M_{\text{p}}$  is  $0.35\mu\text{m}$ ,  
and  $|\lambda_{\text{p}}|=0.25/\text{V}$ )

$$R_{\text{L}} = \frac{2.5}{100\text{m}} = 25\Omega$$

$$A_2 = 1 \times 15.4 = 15.4 \text{ V/V} \quad (23.7\text{dB})$$

$$z_{\text{ESR}} = \frac{1}{10\mu \times 100\text{m}} = 1\text{M rad/s}$$

$$p_o = \frac{1}{10\mu \times 15.4} = 6.5\text{k rad/s}$$

and

$$T(s) = \frac{385(1 + s/1\text{M})}{(1 + s/6.5\text{k})(1 + s/160\text{k})}$$

# Simple LDR: T(s) at Lower Currents

The output stage is affected by  $I_o$ . Let  $I_o = f \times I_{o\max}$ , and

$$g_{mP}' = \sqrt{2I_o \mu_p C_{ox} (W/L)_P} = \sqrt{f} \times g_{mP}$$


$$R_o' = (R_L' || r_{dsP}') = R_o / f$$

The loop gain function is then given by

$$T'(s) = \frac{(T_o / \sqrt{f})(1 + s/z_{ESR})}{[1 + s/(f \times p_o)](1 + s/p_a)}$$

$I_o$	$T(s)$
1mA	$\frac{3850(1 + s/1M)}{(1 + s/65)(1 + s/160k)}$
10mA	$\frac{1217(1 + s/1M)}{(1 + s/650)(1 + s/160k)}$
100mA	$\frac{385(1 + s/1M)}{(1 + s/6.5k)(1 + s/160k)}$

# Simple LDR: Bode Plots of $T(s)$

 



# Simple LDR: Computation vs Simulation

Computation:

$I_o$	$T_o$	UGF	$\phi_m$
1mA*	71.5dB	32kHz	55°
10mA	61.5dB	57kHz	55°
100mA	51.5dB	100kHz	55°

Simulation:

$I_o$	$T_o$	UGF	$\phi_m$
1mA*	57.1dB	13kHz	70°
10mA	56.2dB	46kHz	40°
100mA	45.8dB	94kHz	42°

\* At 1mA  $M_p$  is in sub-threshold and resulted in large discrepancy.

## Simple LDR: Remarks

- (1) To maintain stability, a relatively large output capacitor  $C_L$  is used.
- (2) A relatively large ESR ( $100\text{m}\Omega$ ) is needed to achieve a marginal phase margin (around  $45^\circ$ ).
- (3) The gate-drain overlap capacitance  $C_d$  is miller multiplied by the gain of the output stage, but the gain is too low to affect the dominant pole  $p_o$ . However, the pole  $p_a$  should be modified to  $1/(C_p + C_d)R_a$  for better accuracy.
- (4) For low output current, the pass transistor enters sub-threshold region. A more accurate small signal model should take this into account.