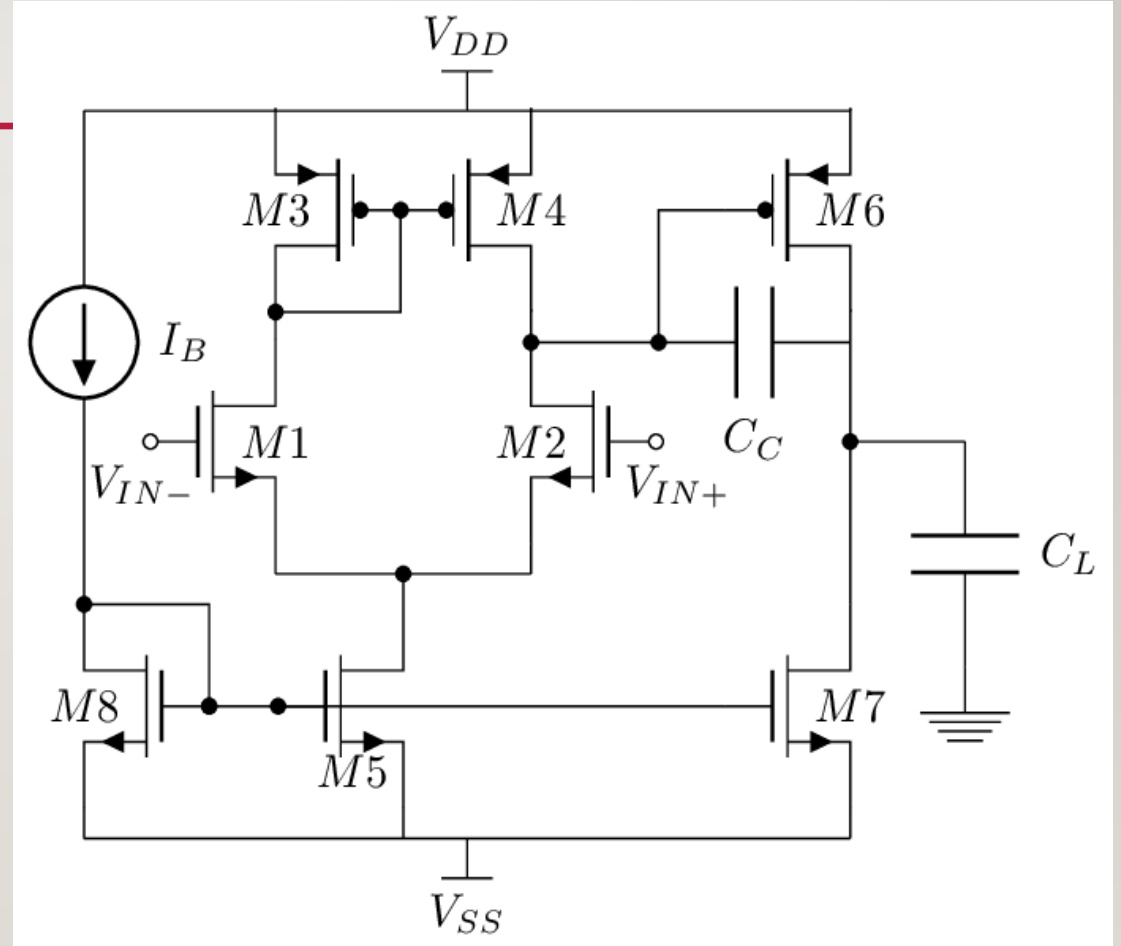


OTA REPORT



OTA DESIGN

- I designed Miller OTA.
- Required Specs: -
- 1- DC gain ≥ 60 dB
 - 2- GBW ≥ 30 MHz
 - 3- PM > 60 deg
 - 4- Slew rate = 20V / 1 μ sec
 - 5- ICMR(+) = 1.6V , ICMR(-) = 0.8V
 - 6- Power < 1 mW



OTA DESIGN STEPS

- I used $V_{DD}=1.8\text{v}$, $C_I=2\text{pf}$ and skywater130nm technology
- 1- To have phase margin $\geq 60^\circ$, C_c should be $\geq 0.22 C_I$ so $C_c \geq 440 \text{ fF}$
 - 2- From slew rate equation we got the Current value , $I = SR \cdot C_c$ so $I \geq 8.8 \text{ uA}$
 - 3- From GBW equation we got $g_{m1,2} = GBW \cdot 2 \cdot \pi \cdot C_c$ then $W/L)_{1,2}$
 - 4- From $ICMR^+$ equation we got $W/L)_{3,4}$ and from $ICMR^-$ equation we got $W/L)_{5,8}$
 $ICMR^+ \leq V_{DD} - V_{sg3} + V_{th1}$
 $ICMR^- \geq V_{gs1} + V_{ov5}$
 - 5- For $PM \geq 60^\circ$ $g_{m6} \geq 10 \cdot g_{m1}$ then from $W/L)_{6,7} / W/L)_{4,5} = g_{m6}/g_{m4}$ we got $W/L)_{6,7}$
 - 6- From equation: $W/L)_{6,7} / W/L)_{4,5} = I_6 / I_4$ we got I_6
 - 7- Finally from equation: $W/L)_{7,8} / W/L)_{5,8} = I_7 / I_5$ we got $W/L)_{7,8}$


OTA CALCULATED PARAMETERS

Parameter	Value
Iref	20uA
W/L)1,2	25u/0.5u
W/L)3,4	7u/0.5u
W/L)5,8	12u/1u
W/L)6	90u/0.5u
W/L)7	75u/1u
Cc	2pf

OTA SIMULATIONS


1. DC analysis to check the DC operating point and ensure that all transistors are in sat.

2.AC analysis:- a) Differential gain

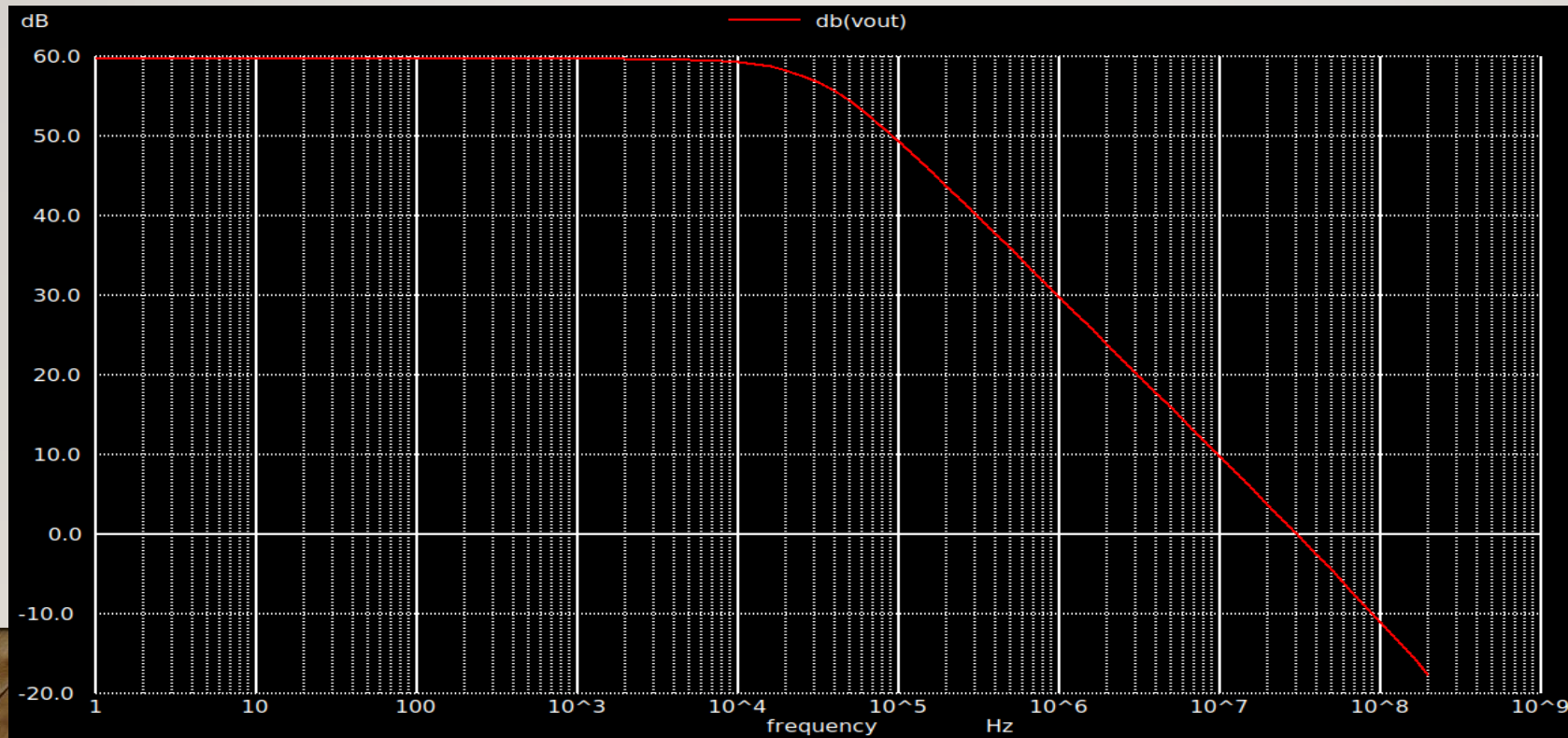


OTA SIMULATIONS

2- AC analysis b) Common mode gain

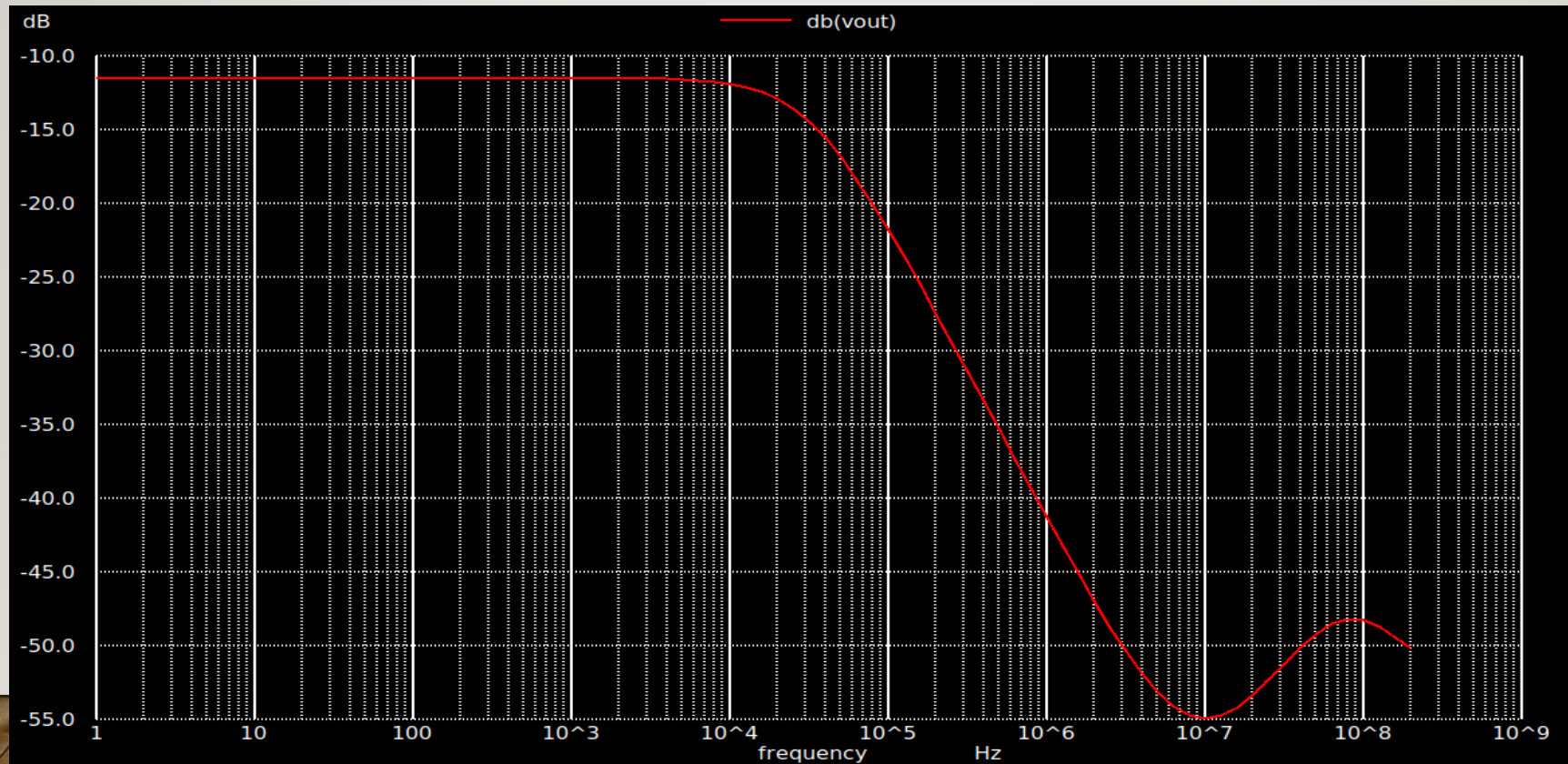


OTA SIMULATIONS

2- AC analysis c) PSRR

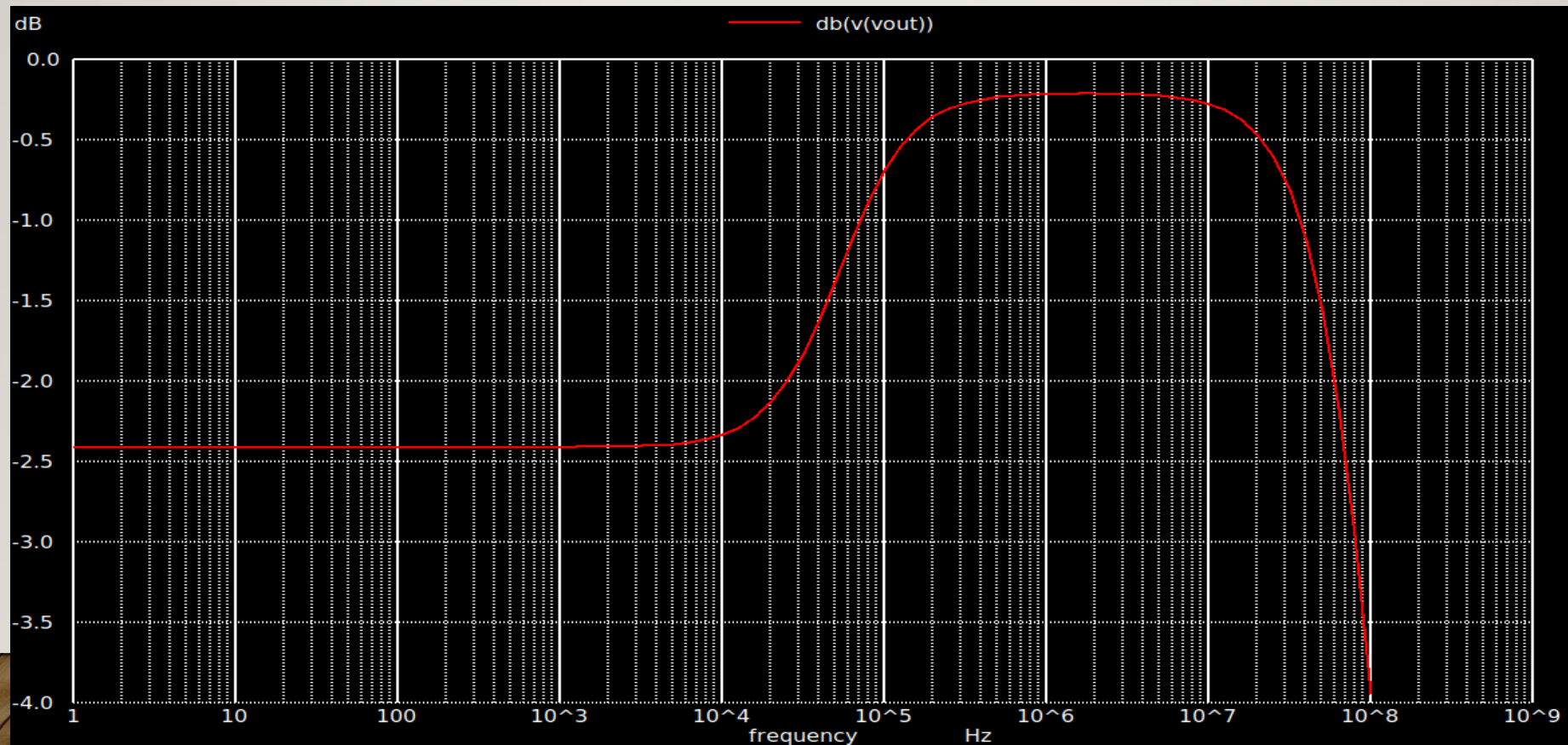


OTA SIMULATIONS

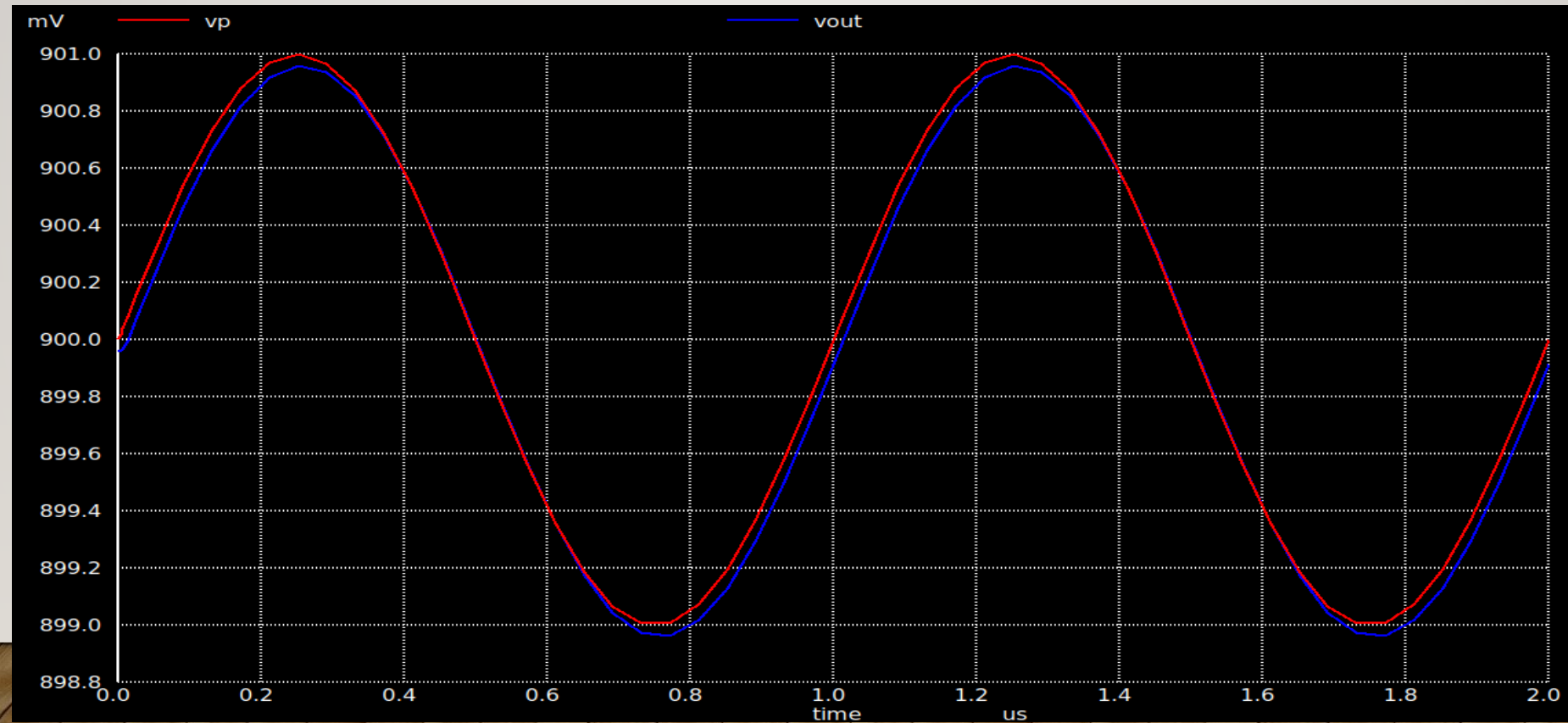3- Transient analysis (The OTA as buffer)



OTA SIMULATIONS

4- Noise analysis (Input referred noise)

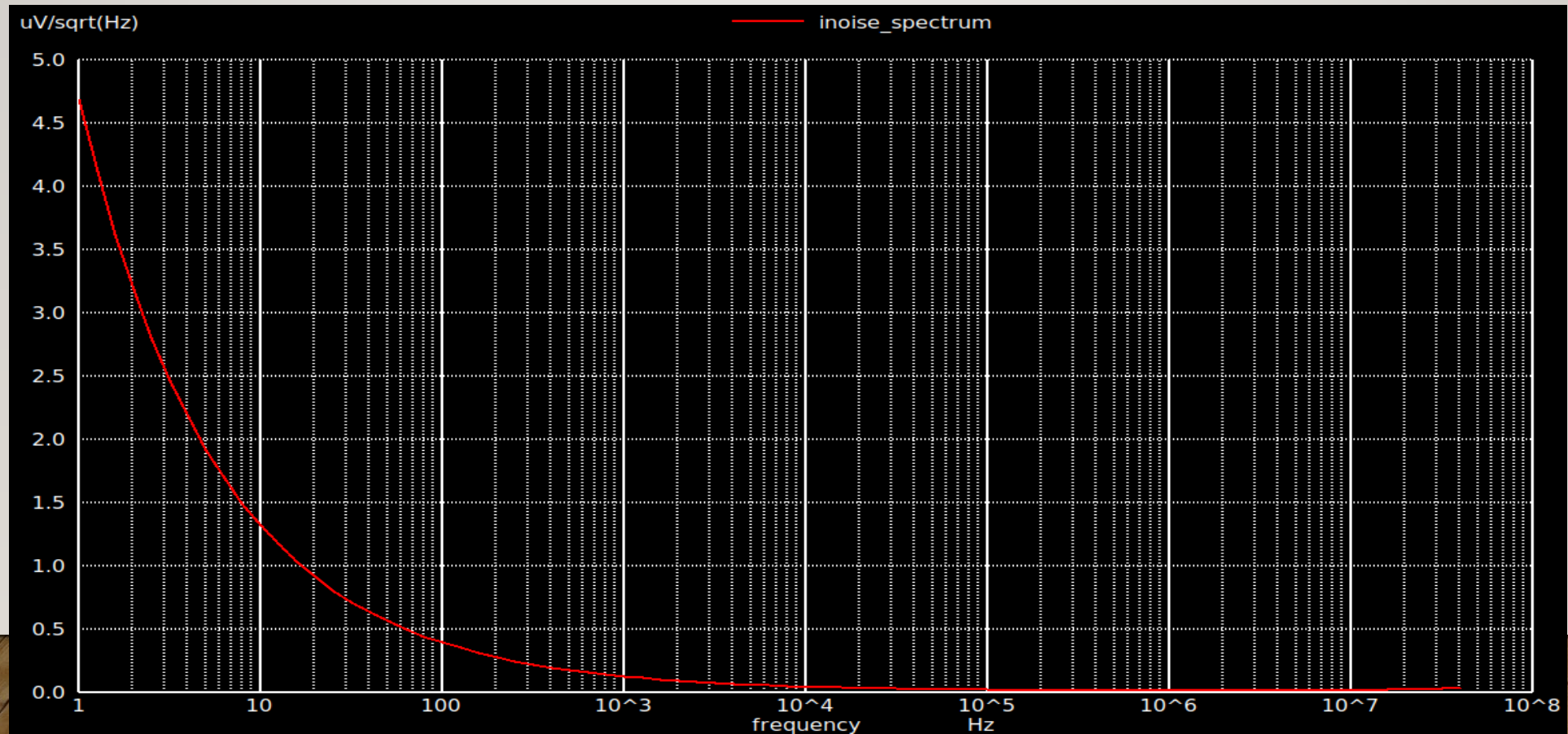

OTA ACHIEVED SPECS

spec	value
Av	60 dB
Acm	-11.5 dB
CMRR	71.5 dB
PSRR	57 dB
GBW	30MHz
PM	52 deg
Power	318 uW