


# LDO REPORT

---


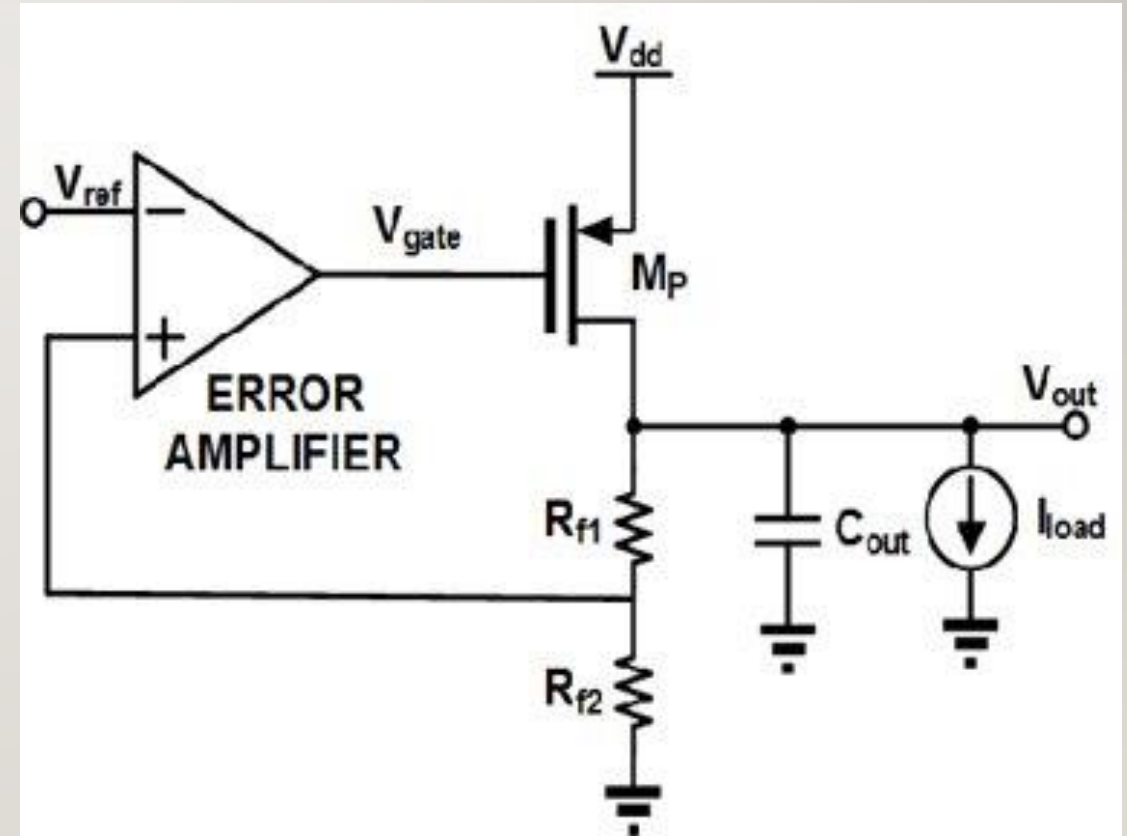
# LDO DESIGN

- I designed the conventional LDO for:-
  - 1- Output voltage of 1.8v.
  - 2- Input voltage from 1.8v to 2.2v.
  - 3- Reference voltage of 1v.
  - 4- Dropout voltage  $\leq 0.1\text{v}$
  - 5- Maximum output current of 17mA.
  - 6- Quiescent current of 12  $\mu\text{A}$ .



# LDO DESIGN STEPS


1- Feedback resistors design:

$$V_{out} = V_{ref} (1 + R_{f1}/R_{f2})$$

$$V_{out} = 1.8\text{v and } V_{ref} = 1\text{v}$$

$$\text{so } R_{f1}/R_{f2} = 0.8$$
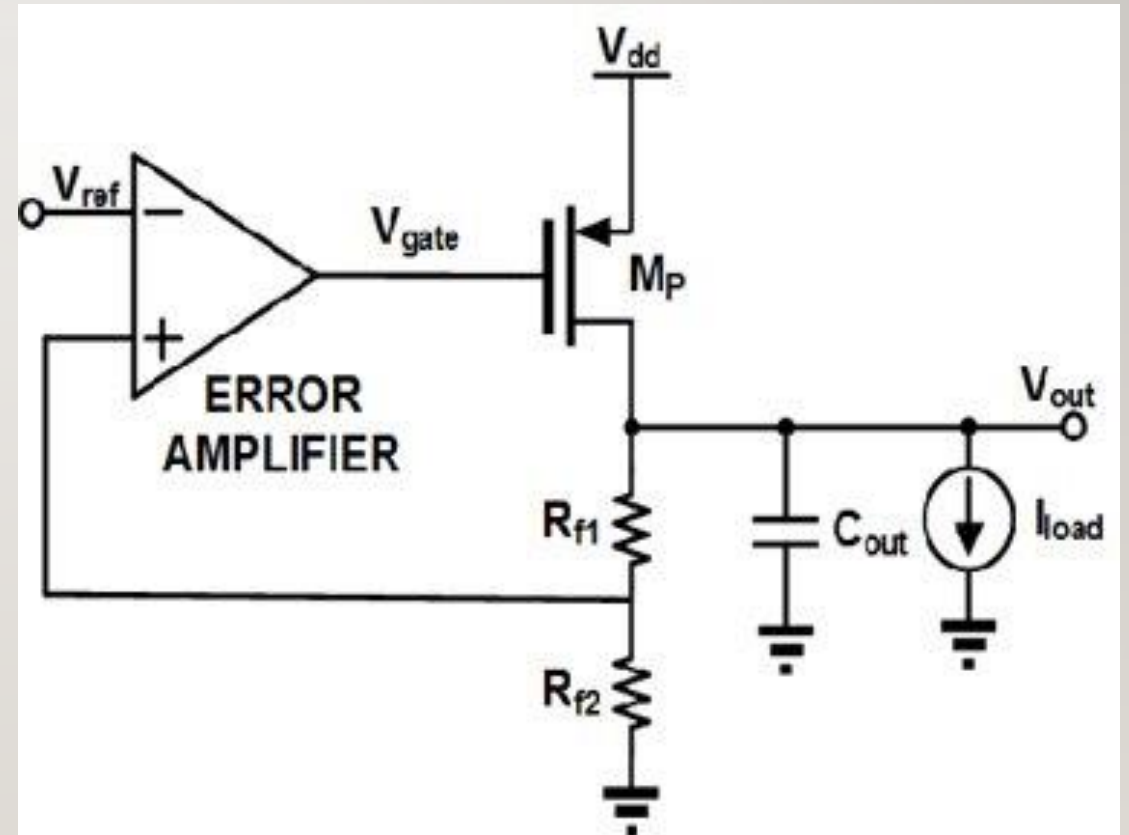
$$\text{Let } R_{f1} = 80\text{k and } R_{f2} = 100\text{k}$$



# LDO DESIGN STEPS

---

2- Pass transistor design: -

$$I_D = \frac{1}{2} \mu C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})^2 \Rightarrow \frac{W}{L} = \frac{I_D}{\frac{1}{2} \mu C_{ox} \cdot (V_{GS} - V_{TH})^2}$$

$I_{D \max} = 17\text{mA}$  ,  $V_{DO} = 0.1$  and  $\mu_p C_{ox} = 42 \text{ u}$

So  $W/L)_p = 40000$

Let  $W = 20\text{u}$  ,  $L = 0.5\text{u}$  and  $M = 1000$

# LDO DESIGN STEPS

---

3- Error amplifier design:-

I used Two stage miller OTA.


4- Vref design:-

I used the Bandgap design to generate Vref.



# LDO STABILITY


## Approximate Pole Zero Locations

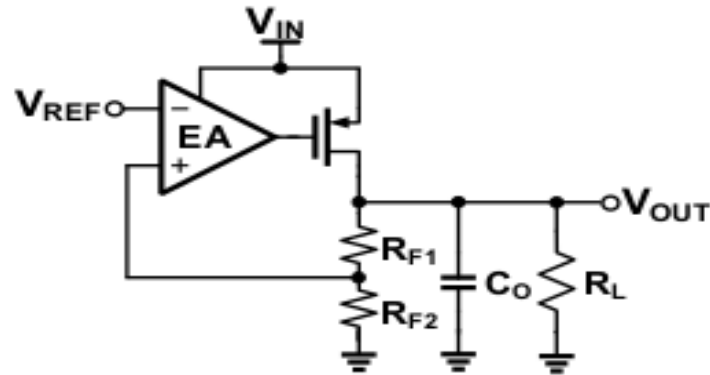

$$\omega_{PL} \approx \frac{1}{R_{OUT} \cdot C_O}$$

$$\omega_{PH} \approx \frac{1}{R_{OEA} \cdot [C_1 + g_{mp} \cdot R_{OUT} \cdot C_{gdp}]}$$

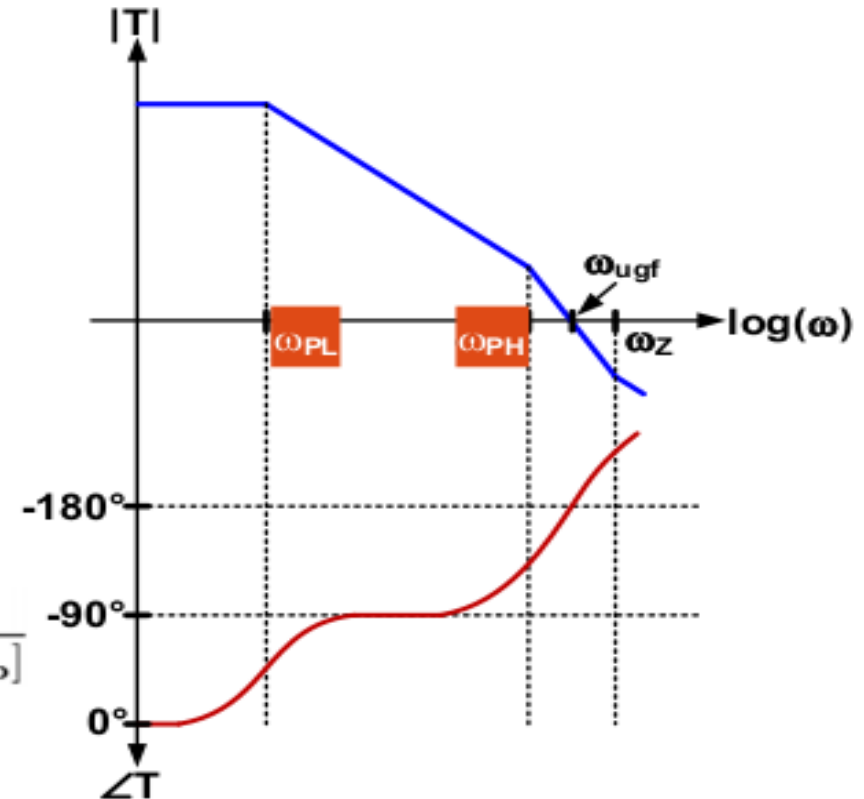
$$\omega_Z \approx \frac{g_{mp}}{C_{gdp}}$$



# LDO STABILITY
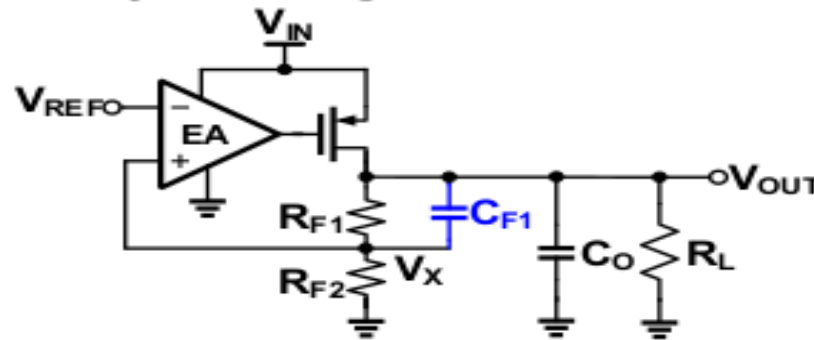
## Frequency Compensation - II [2]

- Introduce zero by adding feed-forward capacitor



$$\frac{V_X(s)}{V_{OUT}(s)} = \left( \frac{R_{F2}}{R_{F1} + R_{F2}} \right) \cdot \left( \frac{1 + sC_{F1}R_{F1}}{1 + sC_{F1}(R_{F1} || R_{F2})} \right)$$

$$\omega_{ZF} = \frac{1}{R_{F1}C_{F1}}$$

$$\omega_{PF} = \frac{1}{(R_{F1} || R_{F2})C_{F1}}$$


$$\frac{\omega_{PF}}{\omega_{ZF}} = 1 + \frac{R_{F1}}{R_{F2}} = \frac{V_{OUT}}{V_{REF}}$$

# LDO SIMULATIONS

---

## 1- Dropout Voltage

$V_{do}$  achieved = 60mV

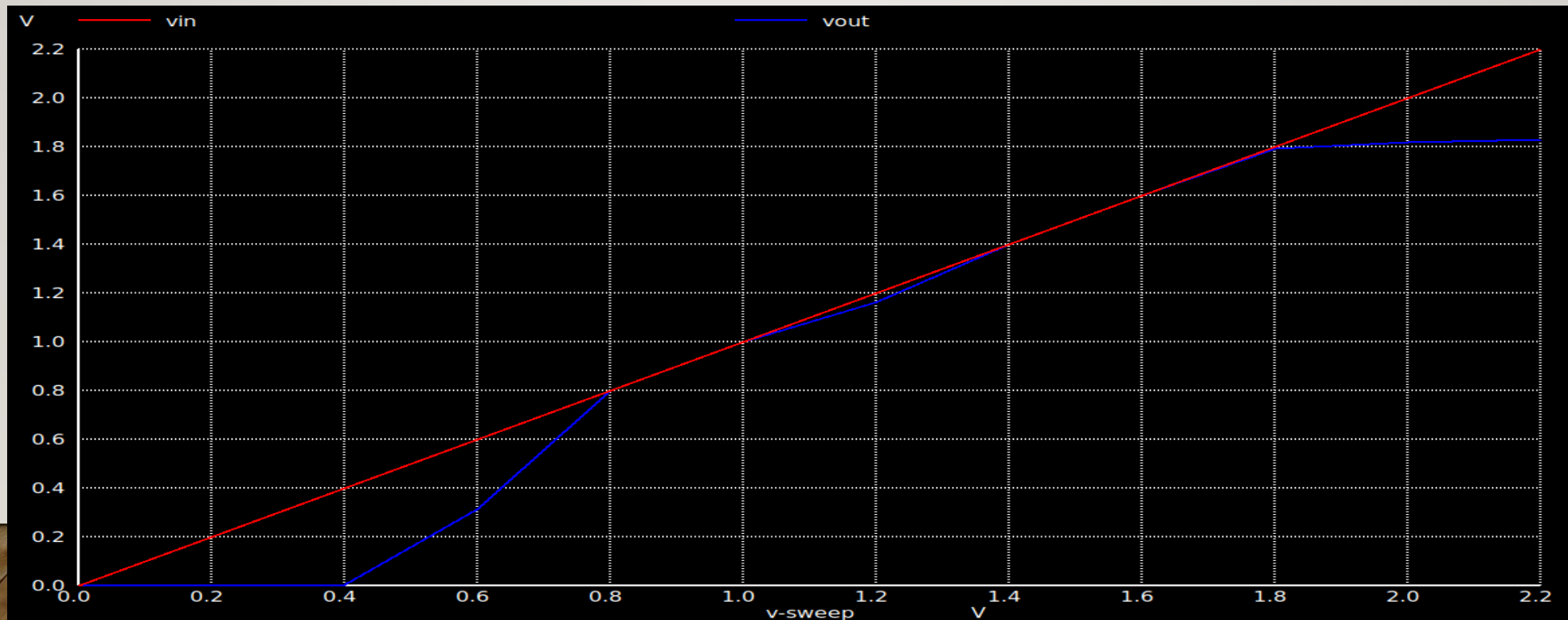




# LDO SIMULATION


---

2- Line regulation = 90 mV/V

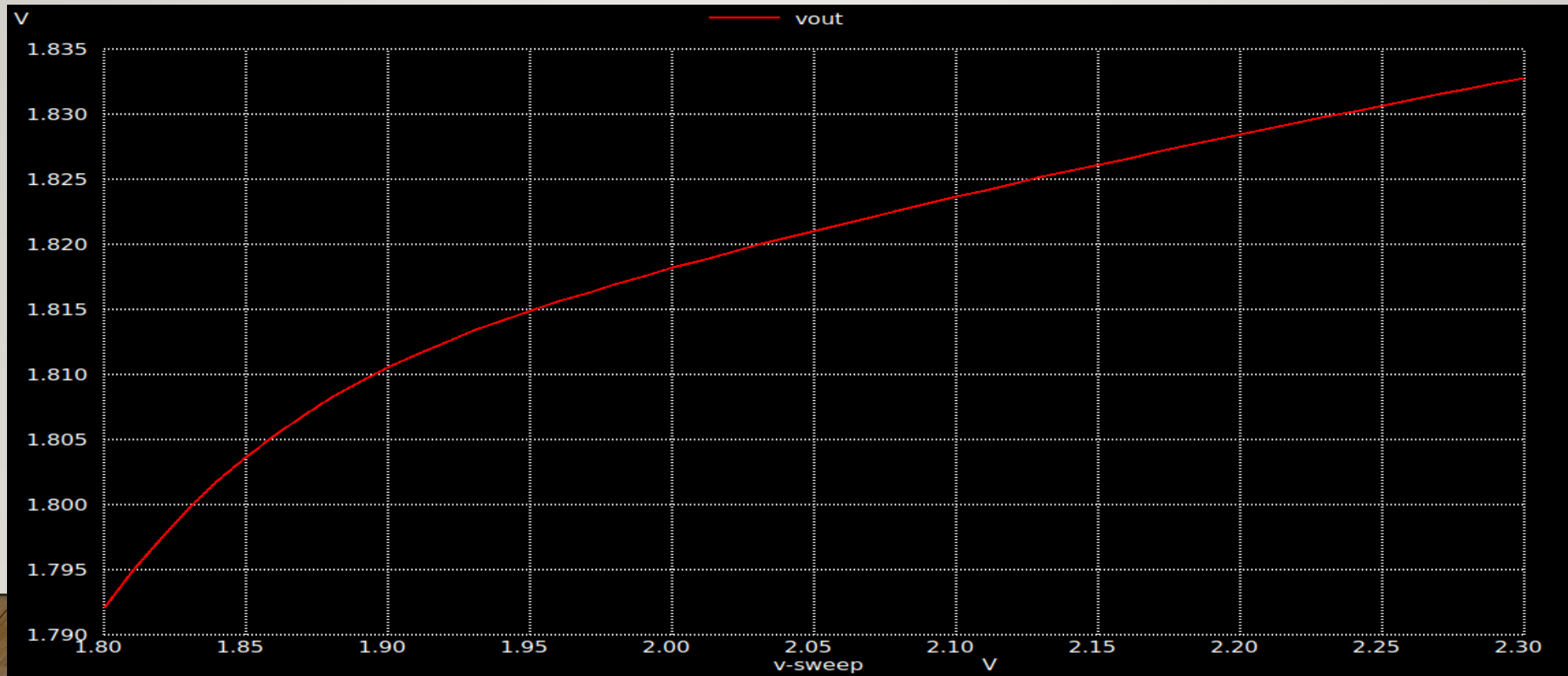
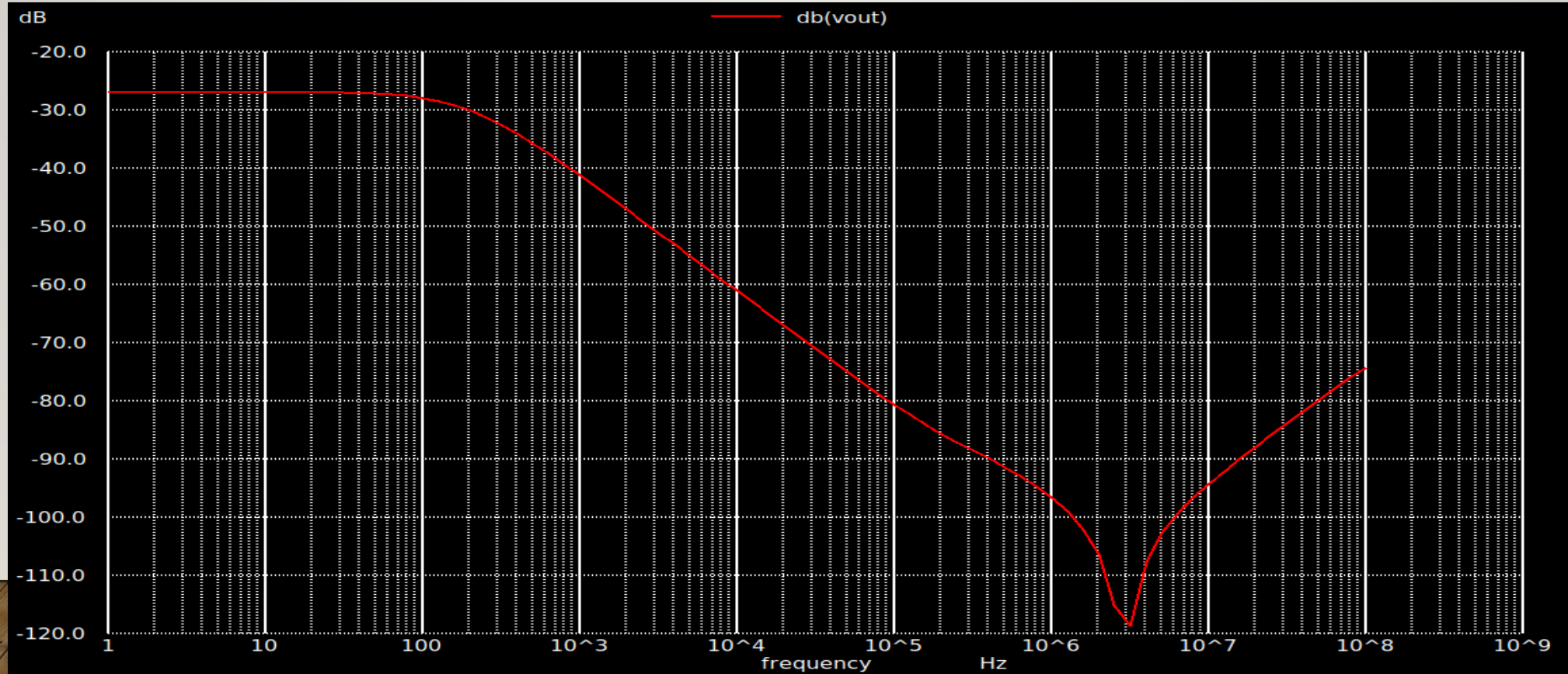
# LDO SIMULATIONS

3- PSRR @ 1KHz = 41 dB , PSRR @ 1MHz = 97 dB



# LDO SIMULATIONS

## 4- Line transient

